



# Lectures of Electrical Engineering Department

**S**ubject Title: Electrical Networks

**C**lass: 2<sup>nd</sup> Stage

Lecture Contents	Lecture sequences:	1 <sup>st</sup> lecture	Instructor Name: Omer Sharaf Aldeen Ali Abbawi
	<b>The major contents:</b>		
	<b>1- Transient Response of RL /RC Circuit</b>		

## Chapter 1

### Transient Response of RL/RC Circuit

**Inductor:**

$$w_L = \frac{1}{2} L i_L^2 \quad v_L = \frac{1}{2} L \frac{d i_L}{dt}$$

$$i_L = \frac{1}{L} \int v_L dt$$

**Capacitor:**

$$w_C = \frac{1}{2} C v_C^2 \quad v_C = \frac{1}{C} \int i_C dt$$

$$i_C = C \frac{d v_C}{dt}$$

- The inductor and capacitor are energy storage elements.
- The stored energy does not change promptly (in zero time) as this needs infinite power transfer ( $w = dp/dt$ )
- $i_L$  and  $v_C$  are associated with the energy stored in the inductor and capacitor respectively; and therefore, they also do not change instantly.
- This chapter studies the time function of  $i_L$  and  $v_C$  as they change in RL and RC circuits.

This chapter is divided into three parts:

**Natural Response** (Week#1):  $i_L$  and  $v_C$  result by discharging energy stored in L or C in a resistive network.

**Step Response** (Week#2):  $i_L$  and  $v_C$  when the energy is being stored in an initially uncharged L and C.

**General Response** (Week #3): analysis of RL and RC circuits that applied to find the response of a circuit with any initial charge and subjected to any change(s) in DC voltage (or current) source.

---

#### 1. Natural Response of RL Circuit

Consider the circuit shown in Fig. 1 where the switch has been closed for a long time and opens at  $t=0$ .

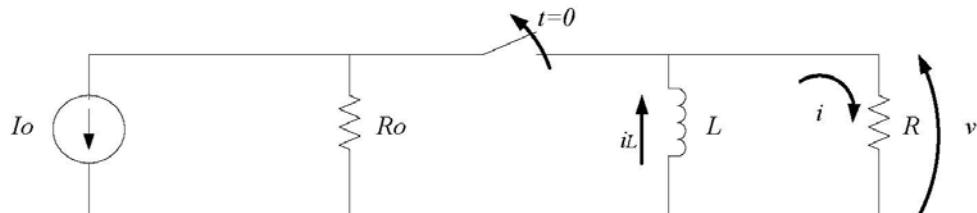


Fig.1

Before opening the switch (say at  $t = 0^-$ ), the circuit is at steady state, and therefore  $v_L = L \frac{di}{dt} = 0$ , so the inductor is acting as a short circuit and  $i_L(t = 0^-) = I_o$ .

After opening the switch, the current source and  $R_o$  are isolated and the inductor circuit becomes as in Fig. 2

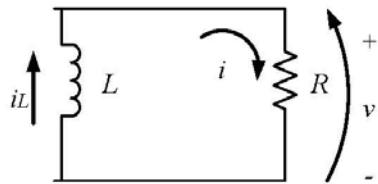


Fig. 2

Just after opening the switch (at  $t = 0^+$ ), the inductor current is still  $I_0$ , but this makes  $v(t = 0^+) = I_0R$  and this voltage will appear across the inductors and cause the inductor current to change. The following analysis describes the variation of the circuit current and voltage after ( $t=0$ ),

For  $t > 0$

The loop voltage equation...

$$L \frac{di}{dt} + iR = 0 \quad (1)$$

Eq. (1) is a 1<sup>st</sup> order Differential Equation (DE) usually solved by integration; However we will apply alternative method here:

Assume:

$$i = Ae^{st} \quad (2)$$

$$\frac{di}{dt} = Ase^{st} \quad (3)$$

Substitute (2) and (3) into (1):

$$LAse^{st} + RAe^{st} = 0$$

$$Ae^{st}(Ls + R) = 0 \quad (4)$$

Eq. (4) implies that either:  $Ae^{st} = 0$ , (i.e.  $i = 0$ ), this solution has no significance and usually referred to as trivial solution or:  $(Ls + R = 0)$  which is the interesting case, so:

$$s = -\frac{R}{L} \quad (5)$$

In order to fully define the current ( $i$ ), we must determine  $A$  in Eq. (1). Consider the Initial condition  $i(0) = I_0$

$$i = Ae^{-\frac{R}{L}t} \quad (6)$$

At ( $t = 0$ ),  $i = I_0$

$$I_0 = Ae^{-\frac{R}{L}\times 0} = A \quad (7)$$

Therefore:

$$i = I_0 e^{-\frac{R}{L}t} \quad (8)$$

It can be shown that  $L/R$  has the unit of time (sec), and (8) can be re-written as:

$$i(t) = I_0 e^{-\frac{t}{L/R}}, \quad (t \geq 0) \quad (8)$$

A plot of  $i(t)$  according to Eq. (8) is shown in Fig. (3) for three values of  $L/R$ .

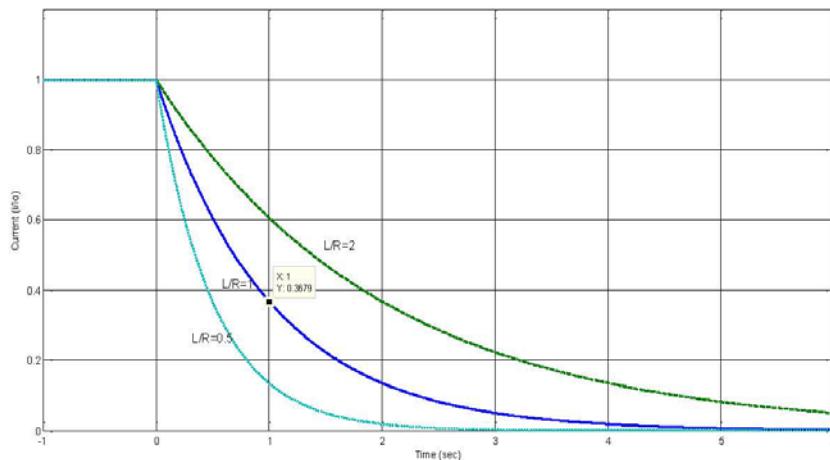


Fig. (3)

It can be noticed that  $L/R$  determines how fast the inductor current discharges and this parameter is defined as the RL circuit **time constant**, and denoted by  $\tau$  (تaw).

$$\text{Time constant, } \tau \triangleq \frac{L}{R} \quad (9)$$

Table 1 mitigates the discharge rate seen in Fig. 3

Table 1						
Time	0	$\tau$	$2\tau$	$3\tau$	$4\tau$	$5\tau$
$\frac{i}{I_0}$	1.00	0.3679	0.1353	0.0498	0.0183	0.0067
Approximation of $\frac{i}{I_0}$	1.00	$\approx 0.37$		<5%		<1%

Most of the time transient is considered over for any time  $>5\tau$ ; and any time  $>10\tau$  can be described as **long time**.

The inductor voltage:

$$v_L = L \frac{di}{dt} = L \frac{d(I_0 e^{-\frac{t}{\tau}})}{dt} = -\frac{L}{\tau} I_0 e^{-\frac{t}{\tau}} = -\frac{L}{L/R} I_0 e^{-\frac{t}{\tau}}$$

$$v_L = -RI_0 e^{-\frac{t}{\tau}} \quad t \geq 0^+ \quad (10)$$

**Example 1:** The switch in the circuit shown in Fig. 4 has been open for long time. The switch is closed at  $t=0$ , determine  $i(t)$ , ( $t \geq 0$ ) and  $v(t)$ ,  $t > 0$

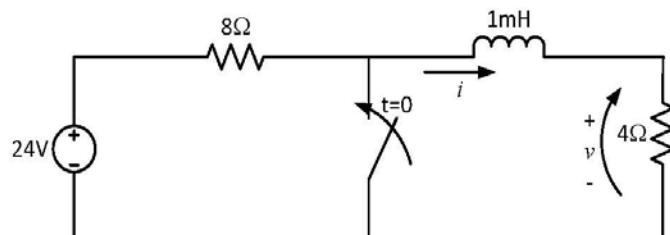


Fig. 4

Answer:

//The three solution steps are:		
(1) Determine $I_0$ ( $i(0^-)$ ) (by studying the circuit before transient starts)	For $t=0^-$ : $I_0 = \frac{24V}{(8+4)\Omega} = 2A$	
(2) Determine $\tau$ by determining $R_{eq}$ for $(t>0)$	For $t>0$ , $R_{eq} = 4\Omega$ $\tau = \frac{L}{R} = \frac{1mH}{4\Omega} = 0.25 \times 10^{-3} sec$	
(3) write $i_L$ according to Eq. (8)	$i(t) = I_0 e^{-\frac{t}{\tau}}$ $i(t) = 2e^{-\frac{t}{0.25 \times 10^{-3}}} = 2e^{-4000t} (A), \text{ for } t \geq 0$	
(4) Other requirements://	$v(t) = i(t) \times R$ $v(t) = 8e^{-4000t} (V)$	

**Example 2:** The switch in the circuit shown in Fig. 5 has been closed for a long time before it is opened at  $t=0$ . Find:

- a)  $i_L(t)$  for  $t \geq 0$ ;
- b)  $i_o(t)$  for  $t \geq 0^+$ ;
- c)  $v_o(t)$  for  $t \geq 0$ , and:
- d) The percentage of total energy dissipated in the  $10\Omega$  resistor

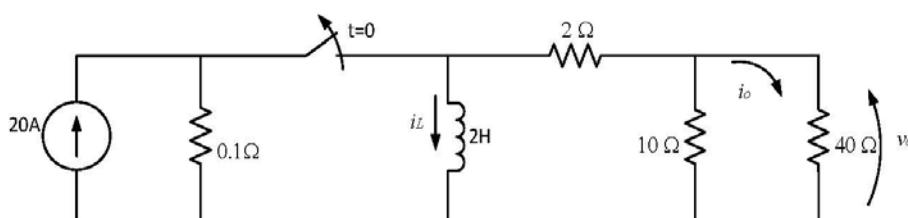


Fig. 5

Answer:

a)

- Initial value of inductor current,  $i_L(t = 0) = 20A$  (usually denoted by  $(i_0)$ )
- $R_{eq} = 2 + (40//10) = 10\Omega$
- $\tau = \frac{2H}{10\Omega} = 0.2sec$
- $i_L(t) = 20e^{-5t}(A), (t \geq 0)$

b)

$$i_0 = -i_L \frac{10\Omega}{(10 + 40)\Omega} = -0.2i_L$$

$$i_o = -4e^{-5t}(A) \quad (t \geq 0^+)$$

c)

$$v_o = 40i_o = -160e^{-5t}(V) \quad (t \geq 0^+)$$

d)

- $W_L = \frac{1}{2}LI_0^2 = \frac{1}{2} \times 2 \times 20^2 = 400J$
- $p_{10\Omega}(t) = \frac{v_o^2}{10} = 2560e^{-10t}(W) \quad (t \geq 0^+)$

$$W_{10\Omega} = \int_{t=0}^{\infty} p_{10\Omega}(t)dt = \int_{t=0}^{\infty} 2560e^{-10t}dt = \frac{2560}{-10}[e^{-10t}]_0^{\infty} = 256[1 - 0]$$

$$W_{10\Omega} = 256J$$

- Percentage energy dissipated in  $10\Omega$  resistor  $= \frac{256}{400} \times 100\% = 64\%$

-Practice: show that the energy dissipated in the three resistors for  $(t > 0)$  in Example 2 is equivalent to the energy initially stored in the inductor)

-Related book examples: 8.2, 8.3, 8.4

A graphical method to find  $(\tau)$  can be applied if the circuit parameters are unknown.

The line tangent to  $i_L$  at  $t=0$  (the switching instant) intersects the  $t$  axis at  $t=\tau$ .

Proof:


$$\frac{di}{dt} = -\frac{1}{\tau}I_o e^{-\frac{t}{\tau}}; \frac{di}{dt}|_{t=0} = -\frac{1}{\tau}I_o \text{ (slope)}$$

The line equation...

$$y = I_0 - \frac{I_o}{\tau}t = I_0 \left(1 - \frac{t}{\tau}\right)$$

At  $t=\tau$ ,  $y=0$ .

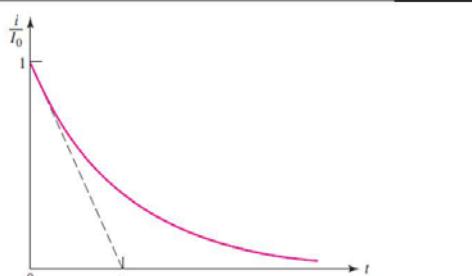//(This method used in the lab to determine  $\tau$ )//




Related Book Problems:

Chapter 8 problems (1-13)


**Homework** (to be handed in the tutorial session This week)

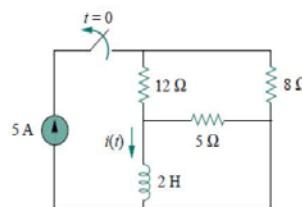- 1- For the circuit in Fig. , find  $i(t)$  for  $t > 0$ .



2- At  $t=0$ , the make-before-break switch moves from position a to position b.

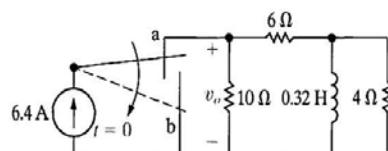- Calculate  $v_o(t), t \geq 0^+$
- What percentage of the initial energy stored in the inductor is dissipated in the  $4\Omega$  resistor.



## 2. Natural Response of RC Circuit

Consider the circuit shown in Fig. 6, the switch has been in position (a) for long time and at  $t=0$ , the switch is moved to position (b). The following analysis shows the variation of the capacitor voltage after the switch is moved.

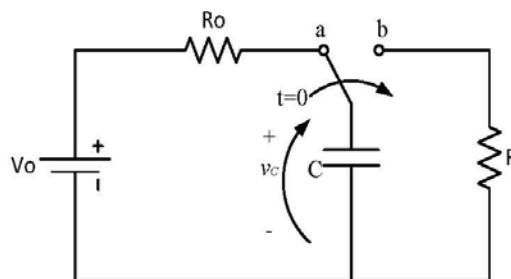


Fig. 6

- Before the switch moves to position (b), (at  $t=0^-$ ), the capacitor is charged by the DC source to  $V_o$ .
- For  $t>0$ , the supply is removed and the capacitor equivalent circuit is as shown in Fig. 7

Applying the “node current” principle:

$$i_C + i_R = 0$$

$$C \frac{dv_c}{dt} + \frac{v_c}{R} = 0 \quad (11)$$

(Eq. (11) is similar to Eq. (1)), Assume:

$$v_c = Ae^{st} \text{ and } \frac{dv_c}{dt} = As e^{st} \quad (12a \text{ and } 12b)$$

Substitute (12) into (11)

$$As e^{st} \left( Cs + \frac{1}{R} \right) = 0 \quad (13)$$

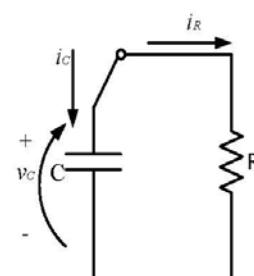


Fig. 7

Either:  $Ae^{st} = 0$ , (i.e.  $v_{c=0}$ ) trivial solution (ignore).

$$\text{Or: } \left( Cs + \frac{1}{R} \right) = 0 \Rightarrow s = -\frac{1}{RC} \quad (14)$$

$$\text{At } t=0, v_c(t = 0) = V_0 \quad (15)$$

Substitute (15) into (12a)

$$v_c(t = 0) = V_0 = Ae^{sx_0} = A,$$

$$A = V_0 \quad (16)$$

Substitute (14) and (16) into (12a)

$$v_c(t) = V_0 e^{-\frac{t}{RC}} \quad (V), \text{ for } (t \geq 0) \quad (17)$$

It can be shown that RC has the unit of sec. defining the circuit time constant,  $\tau$  as:

$$\tau \triangleq RC \quad (18)$$

Substitute (18) into (17)

$$v_c(t) = V_0 e^{-\frac{t}{\tau}} \quad (V), \text{ for } (t \geq 0) \quad (19)$$

Eq. (19) describes the capacitor discharge in resistive circuit, and Fig. 8 shows the *natural response* of an RC circuit.

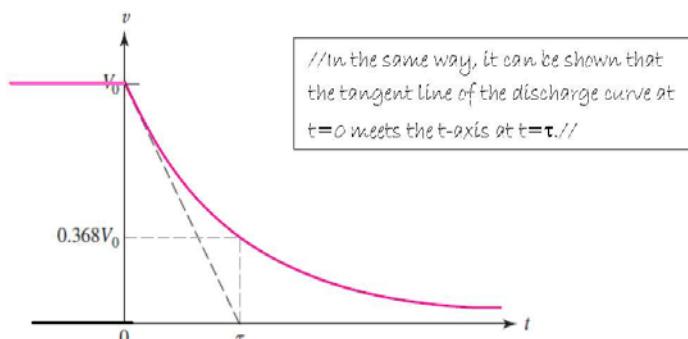


Fig. 8

**Example 3:** The switch in the circuit shown in Fig. 9 has been in position (x) for a long time. At  $t=0$  the switch moves to position (y). Find

- $v_c(t), t \geq 0$
- $v_o(t), t \geq 0^+$
- $i_o(t), t > 0$
- The total energy dissipated in the  $60\text{k}\Omega$  resistor

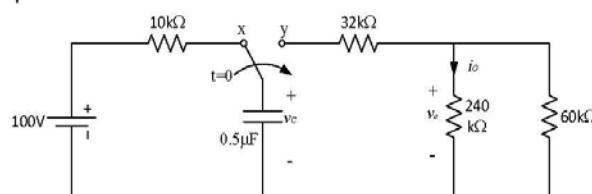


Fig. 9

Answer:

(a)

<p>From the circuit condition for <math>t &lt; 0</math>.</p> <ul style="list-style-type: none"> <li>The initial value of the capacitor voltage,  <math>v_o = v_c(t=0) = 100V</math></li> </ul>	
<p>From the circuit condition for <math>t &lt; 0</math>.</p> <ul style="list-style-type: none"> <li>The equivalent resistance:  <math>R_{eq} = \left( \frac{240 \times 60}{240 + 60} \right) k\Omega</math>  <math>R_{eq} = 80 k\Omega</math></li> <li>The time constant:  <math>\tau = R_{eq}C = 80 \times 10^3 \times 0.5 \times 10^{-6}</math>  <math>\tau = 40 \text{ msec.}</math></li> <li>The capacitor voltage (from Eq.19)  <math>v_c(t) = 100e^{-25t} (V), t \geq 0</math></li> </ul>	

(b)

//We can find  $v_o$  by: (1) dividing the voltage  $v_o$  between the  $32k\Omega$  and the parallel combination. OR (2) by determining  $i_o$  as follows://

$$i_C = C \frac{dv_C}{dt} = 0.5 \times 10^{-6} (-25 \times 100 e^{-25t})$$

$$i_C = -1.25 \times 10^{-3} e^{-25t} (A), t > 0$$

$$v_o = -i_C \times (240/(60) k\Omega) // \text{the parallel sign is reversed as the correct one } // \text{turns fraction in Ms equation } \otimes //$$

$$v_o = -(-1.25 \times 10^{-3} \times e^{-25t}) \times \left( \frac{240 \times 60}{240 + 60} \right) \times 10^3$$

$$v_o = 60e^{-25t} (V), t > 0$$

(c)

$$i_o = \frac{v_o}{60k}$$

$$i_o = e^{-25t} (mA), (t > 0)$$

$$(d) W_{60k} = \int_{t=0}^{\infty} i_o^2 R dt = \int_{t=0}^{\infty} (e^{-25t} \times 10^{-3})^2 240 dt = \int_{t=0}^{\infty} e^{-50t} \times 10^{-6} \times 60 \times 10^3 dt$$

$$W_{60k} = 1.2mJ$$

**Example 4:** The initial voltage of the capacitors  $C_1$  and  $C_2$  are as indicated. The switch is closed at  $t=0$ .

- Find  $v_1(t)$ ,  $v_2(t)$  and  $v(t)$  for  $t \geq 0$ , and  $i(t)$  for  $t \geq 0^+$ .
- Calculate the initial energy stored in  $C_1$  and  $C_2$ .
- Determine how much energy stored in the capacitors as  $t \rightarrow \infty$ .
- Show that the total energy delivered to the resistor is the difference between the results of (b) and (c).

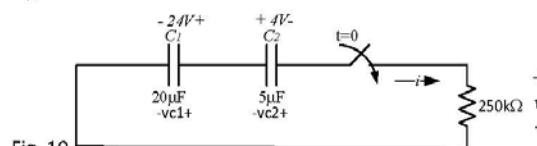


Fig. 10

Answer:

(a)

- Find  $C_{eq}$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \left(\frac{1}{20} + \frac{1}{5}\right) \frac{1}{\mu F} \rightarrow C_{eq} = 4\mu F$$

- Find  $\tau$

$$\tau = RC_{eq} = 250 \times 10^3 \times 4 \times 10^{-6} = 1 \text{ sec.}$$

- Find initial voltage of  $C_{eq}$

$$v(t=0) = 24 - 4 = 20V$$

- Find  $v(t)$ :

$$v(t) = 20e^{-t}(V), t > 0$$

$$i(t) = \frac{v(t)}{R} = 80e^{-t}\mu A, (t > 0)$$

$$v_{C1}(t) = \frac{1}{C} \int_0^t -i(x) dx + v_{C1}(0)$$

$$v_{C1}(t) = -\frac{10^6}{5} \int_0^t 80 \times 10^{-6} e^{-x} dx - 4$$

$$v_{C1}(t) = 16e^{-t} - 20 (V), t \geq 0$$

Similarly,

$$v_{C2}(t) = \frac{1}{C_2} \int_0^t -i(x) dx + v_{C2}(0)$$

$$v_{C2}(t) = -\frac{10^6}{20} \int_0^t 80 \times 10^{-6} e^{-x} dx + 24$$

$$v_{C2}(t) = 4e^{-t} + 20 (V), t \geq 0$$

(b)

The initial energy stored in  $C_1$  and  $C_2$

$$W_{1,0} = \frac{1}{2}(5\mu)(4^2) = 40\mu J$$

$$W_{2,0} = \frac{1}{2}(25\mu)(24^2) = 5760\mu J$$

The total initial energy:

$$W_0 = W_{1,0} + W_{2,0} = 5800\mu J$$

(c)

As  $t \rightarrow \infty$ :  $v_1 \rightarrow -20V$  and  $v_2 \rightarrow 20V$

And the energy in the two capacitors as  $t \rightarrow \infty$

$$W_{1,\infty} = \frac{1}{2}(5\mu)(-20^2) = 1000\mu J$$

$$W_{2,\infty} = \frac{1}{2}(20\mu)(20^2) = 4000\mu J$$

The total final energy=

$$W_\infty = W_{1,\infty} + W_{2,\infty} = 5000\mu J$$

(d) The total energy dissipated in the resistor:

$$W_{250} = \int_{t=0}^{\infty} i^2 R dt = \int_{t=0}^{\infty} (80e^{-t} \times 10^{-6})^2 \times 250 \times 10^3 dt = 800 \mu J$$

The power dissipated in the resistor is the difference between the initial power and the final value.

$$800 \mu J = 5800 \mu J - 5000 \mu J$$

#### Practice

- 8.6 Find values of  $v_C$  and  $v_o$  in the circuit of Fig. 8.23 at  $t$  equal to  
(a)  $0^-$ ; (b)  $0^+$ ; (c) 1.3 ms.

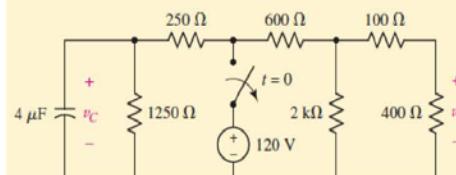



FIGURE 8.23

Ans: 100 V, 38.4 V; 100 V, 25.6 V; 59.5 V, 15.22 V.

Related book Problems 16-40

Homework (to be handed in the tutorial session this week)

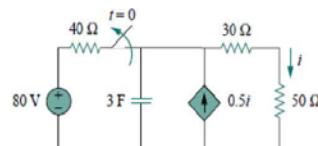3- For the circuit shown. Find  $i(t)$  for  $t < 0$  and  $t > 0$ .





# Lectures of Electrical Engineering Department

**S**ubject Title: Electrical Networks

**C**lass: 2<sup>nd</sup> Stage

Lecture Contents	Lecture sequences:	2 <sup>nd</sup> lecture	Instructor Name: Omer Sharaf Aldeen Ali Abbawi
	<b>The major contents:</b> <b>Natural Response</b>		
	<b>The detailed contents:</b> <b>1- Natural Response of RC circuits</b> <b>2- Step Response in RC circuits</b>		

## Chapter 1

### Transient Response of RL /RC Circuit

This second lecture of chapter 1 deals with the step response. It presents the analysis of RL /RC circuit subjected to sudden application of dc voltage or current supply.

#### Definition:

The unit-step function  $u(t)$ : a function of time which is ZERO for all values of its argument less than zero and which is ONE for all positive values of its argument as shown in Fig. 11.:

$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases} \quad (1)$$

More generally;

$$u(t - t_0) = \begin{cases} 0 & t < t_0 \\ 1 & t > t_0 \end{cases} \quad (2)$$

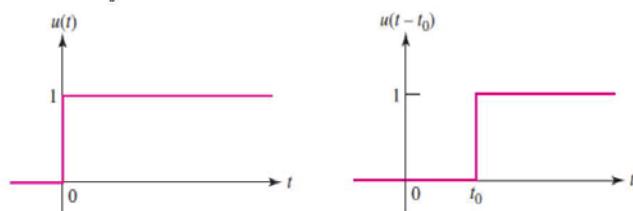


Fig. 11

Initially, we will use this function to activate some sources other applications will be indicated later. Fig. 12 shows two identical arrangements, the second uses unit step function to activate the current source.

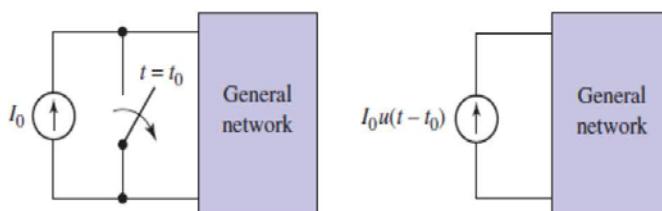


Fig. 12

#### 3. Step Response of RL Circuit

Consider the circuit shown in Fig. 13, where the voltage supply is applied to the RL circuit at  $t=0$ .

Assume that the initial value of the inductor current  $i_L(t = 0) = I_0$  (the source of  $I_0$  is not shown in Fig. 13)

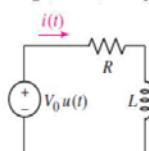


Fig.13

For  $t \geq 0$ , the loop equation:

$$V_s = R_i + L \frac{di}{dt} \quad (3)$$

Assume the solution of Eq. (3) has the following form:

$$i(t) = Ae^{st} + K \quad (4)$$

$$\frac{di}{dt} = Ase^{st} \quad (5)$$

Substitute (4) and (5) into (3):

$$V_s = R(Ae^{st} + K) + LAsse^{st}$$

$$V_s = RAe^{st} + RK + LAsse^{st} \quad (6)$$

By separating the constant and variable parts of Eq (6), we obtain two equations:

$$V_s = RK \Rightarrow K = \frac{V_s}{R} \quad (7)$$

$$0 = RAe^{st} + LAsse^{st}$$

$$Ae^{st}(R + sL) = 0 \rightarrow s = -\frac{R}{L} \quad (8)$$

As in section 1, define  $\tau \equiv \frac{L}{R}$

$$\text{Eq. (8) becomes } s = -\frac{1}{\tau} \quad (8)$$

At  $t=0, i = I_o$ , substitute into (4)

$$i(t=0) = I_o = A + \frac{V_s}{R} \rightarrow A = (I_o - \frac{V_s}{R}) \quad (9)$$

Substitute (7), (8) and (9) into (4)

$$i(t) = \frac{V_s}{R} + \left( I_o - \frac{V_s}{R} \right) e^{-\frac{t}{\tau}}, t \geq 0 \quad (10)$$

Eq. (10) is a general equation, notice the following special cases:

-If we have no source ( $V_s=0$ ), Eq. (10) becomes identical to the natural response equation

$$(\text{Eq. (8)}\_ \text{Lect. #1}). i(t) = I_o e^{-\frac{t}{\tau}}$$

- If the initial current is zero ( $I_o=0$ ), Eq. (10) becomes  $i(t) = \frac{V_s}{R} - \frac{V_s}{R} e^{-\frac{t}{\tau}}$  similar to Eq. [24] in the textbook.

Fig. 14 clarifies the inductor current variation with time, it is shown that:

- At  $t=\tau$ , the inductor current changes by 63.2% of the total variation ( $\frac{V_s}{R} - I_o$ ). Where  $63.2\% = (1 - e^{-1})$ .
- At  $t=3\tau$  and  $5\tau$  the change of the inductor current is 95% and 99.3% of the total change respectively.

Note that  $\frac{V_s}{R}$  represents the inductor current as the time  $\rightarrow \infty$ , sometimes denoted by  $I_F$

// No problem to have  $I_o > V_s/R$ . In that case the current will decrease during transient time //

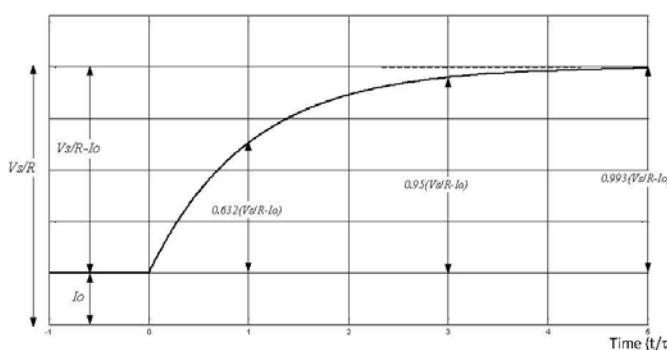


Fig. 14

**Example 1:** For the circuit shown in Fig. 15, determine  $i(t)$ ,  $t \geq 0$ .


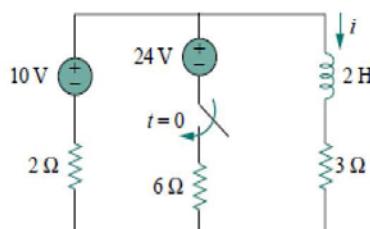


Fig. 15

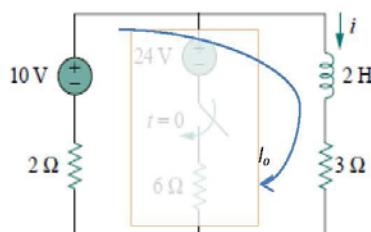
$$\text{For } t < 0 \\ I_o = \frac{10V}{5\Omega} = 2A$$




For  $t > 0$

Vth:
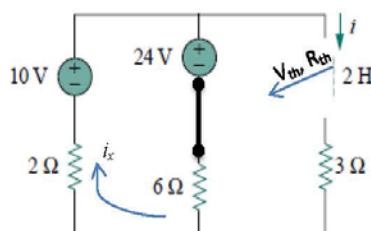
$$24 + 8i_x - 10 = 0 \rightarrow i_x = -\frac{14}{8} \\ V_{th} = 24 + i_x \times 6 = 24 - \frac{14}{8} \times 6 = 13.5V \\ R_{th} = 3 + (2 \parallel 6) = 4.5\Omega \\ \tau = \frac{L}{R_{th}} = \frac{2}{4.5} \text{ sec.}$$


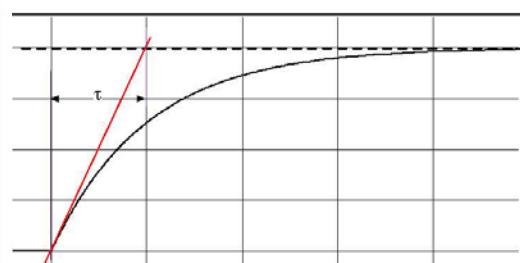
$$i(t) = \frac{V_s}{R} + \left( I_o - \frac{V_s}{R} \right) e^{-\frac{t}{\tau}} \\ i(t) = \frac{13.5}{4.5} + \left( 2 - \frac{13.5}{4.5} \right) e^{-\frac{t}{4.5}} \\ i(t) = 3 - e^{-2.25t} A, t \geq 0$$




**Exercise:** show that the tangent line of the transient curve at  $t=0$ , reaches the final value of the transient at  $t=\tau$ .

As in the natural response case, this method can be used to measure  $\tau$ , if the circuit parameters are unknown.


Related textbook Example 8.8, practice exercises 8.10, 8.11, and problems: 47-54.

H.W. submit in tutorial session

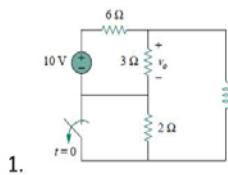Find  $v_o(t)$  for  $t > 0$  in the circuit of Fig.



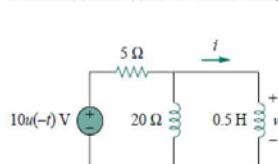Obtain  $v(t)$  and  $i(t)$  in the circuit of Fig.



#### 4. Step Response in RC Circuit

The capacitor shown in Fig. 16 is initially charged to a voltage,  $V_0$  ( $v_c(t < 0) = V_0$ ). At  $t=0$  the switch is closed; we want to determine  $v(t)$ , ( $t \geq 0$ ).

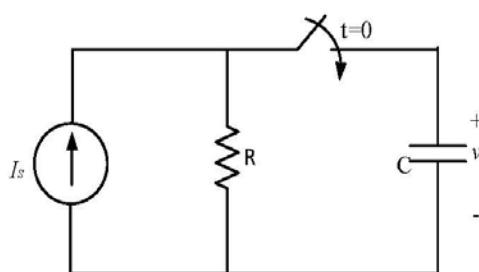


Fig. 16

For  $t \geq 0$ , the node currents equation:

$$I_s = \frac{v}{R} + C \frac{dv}{dt} \quad (11)$$

Following steps similar to those written to derive equation (10), we can show that the solution of (11) is

$$v(t) = I_s R + (V_0 - I_s R) e^{-\frac{t}{RC}}, \quad t \geq 0 \quad (12)$$

Where  $\tau = RC$

What has been indicated about Eq. (10), is also applicable to Eq. (12) for being:

- A general equation and zero forced voltage ( $I_s R$ ), or zero initial voltage can be taken as special cases.
- The plot of  $v$  against time for  $t \geq 0$  is similar to that shown in Fig. 14.

**Example 2:** The switch in the circuit shown in Fig. 17 has been in position (a) for a long time. At  $t=0$  the switch is moved to position (b).

- What is the initial value of  $v_c$ ?
- What is the final value of  $v_c$ ?
- What is the time constant of the circuit when the switch is in position (b)?
- What is the expression of  $v_c(t)$  when  $t \geq 0$ ?
- What is the expression of  $i(t)$  when  $t \geq 0$ ?

(f) How long after the switch is in position (b) does the capacitor voltage equal zero?

(g) Plot  $v_c(t)$  and  $i(t)$  versus t.


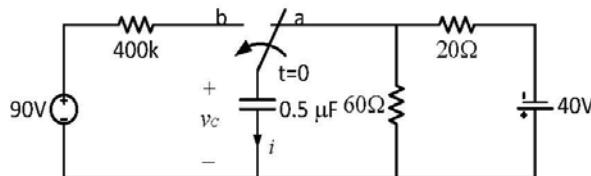


Fig. 17

Sol.

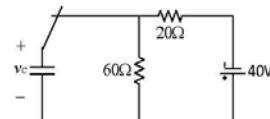(a)  $t < 0$

$$v_c(t = 0^-) = V_0 = \frac{-40}{20 + 60} 60 = -30V$$



(b)  $v_c(t = \infty) = V_F = 90V$

$$(c) \tau = RC = (400 \times 10^3)(0.5 \times 10^{-6}) = 0.2sec$$


$$(d) v(t) = I_s R + (V_o - I_s R) e^{-\frac{t}{\tau}}$$

$$v(t) = 90 + (-30 - 90)e^{-5t}$$

$$v(t) = 90 - 120e^{-5t}, t \geq 0$$

//We have used Thevenin's  $\leftrightarrow$  Norton's transfer to replace  $6\Omega$ . However we can always substitute  $6\Omega$  by the final value of the capacitor voltage //

$$(d) 0 = 90 - 120e^{-5t_z}$$

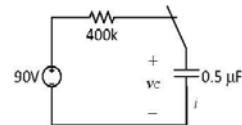


$$\ln\left(\frac{-90}{-120}\right) = -5t_z$$

$$t_z = 57.54ms$$

$$(e) i_C = C \frac{dv_C}{dt} = 0.5 \times 10^{-6} \times ((-5)(-120e^{-5t}))$$

$$i_C = 0.3e^{-5t} (mA), t > 0$$


(f)

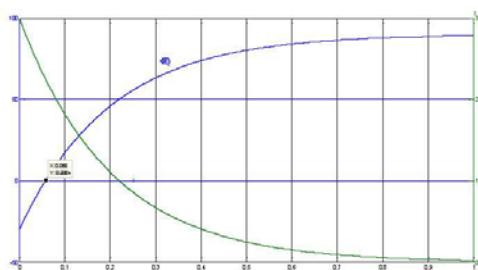


Related Book Examples 8.10 and 8.11; Book Practice 8.12 ; problems: 59-64

H.W. submit in tutorial session

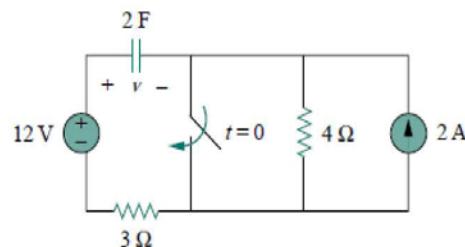
3. Calculate the capacitor voltage and current for  $t \geq 0$  in the circuit shown:



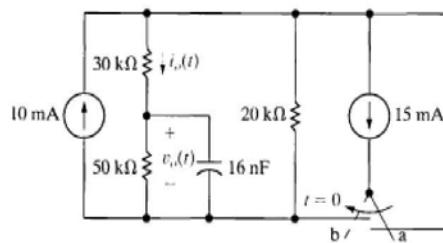4. The switch in the circuit shown has been in position (a) for a long time. At  $t=0$  the switch moves to position (b). Find  $v_o(t), t \geq 0$



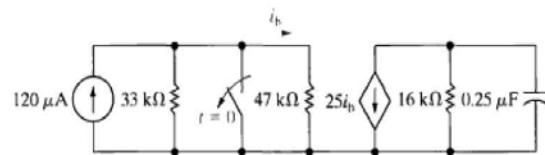5. The switch has been closed for a long time and it is opened at  $t=0>$ . How many milliseconds after the switch opens is the energy stored in the capacitor 25% of its final value?





## Lectures of Electrical Engineering Department

**S**ubject Title: Electrical Networks

**C**lass: 2<sup>nd</sup> Stage

Lecture Contents	Lecture sequences:	3 <sup>rd</sup> lecture	Instructor Name: Omer Sharaf Aldeen Ali Abbawi
	<b>The major contents:</b> <b>Transient Response of RL /RC Circuit</b>		
<b>The detailed contents:</b> <b>1- General Response of RL/RC circuits</b> <b>2- Sequential Switches</b>			

## Chapter 1

## Transient Response of RL /RC Circuit

This third (and last) lecture of Chapter 1 deals with the general response which includes:

- Analysis of RL /RC circuit subjected to application of new dc supply at any instant ( $t_0$ ), and
- Analysis of circuit subjected to sequence of application (or removal) of dc supplies.

**1. General Response of RL/RC Circuit**

To deal with the transient that start at any time ( $t_0$ ) which is not necessarily zero, we can imagine a new shifted time axis (say  $t'$ -axis) with a zero at ( $t_0$ ) as shown in Fig. 18.

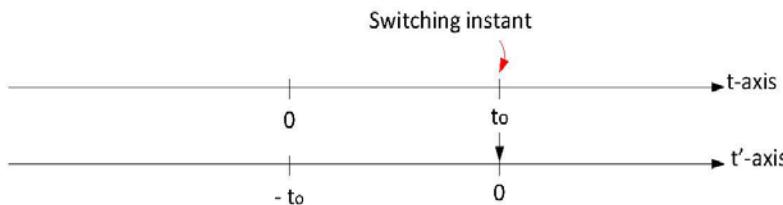


Fig. 18

If we write the general response equation as a function of  $t'$ , we will follow the method presented last week exactly. i.e.

$$x(t') = X_F + (X_o - X_F)e^{-\frac{t'}{\tau}} \quad (1)$$

Where:

$x$  is the inductor current for RL circuit or the capacitor voltage for RC circuit.

$X_F$  is the steady state value of ( $x(t' = \infty)$ )

$X_o$  is the initial condition ( $x(t' = 0)$ )

From Fig. 18 it can be noted that the relationship between  $t$  and  $t'$  is:

$$t' = t - t_0 \quad (2)$$

If (2) substituted in (1), we will get the circuit response as a function of the  $t$ , as follows:

$$x(t) = X_F + (X_o - X_F)e^{-\frac{(t-t_0)}{\tau}} \quad (3)$$

**Example 1:** Refer to the circuit of Fig. 19, which contains a voltage-controlled dependent voltage source in addition to two resistors. (a) Compute the circuit time constant. (b) Obtain an expression for  $v_x$  valid for all  $t$ . (c) Plot the power dissipated in the  $4\Omega$  resistor over the range of 6 time constants. (d) Repeat parts (a) to (c) if the dependent source is installed in the circuit upside down.

(e) Are both circuit configurations "stable"? Explain.

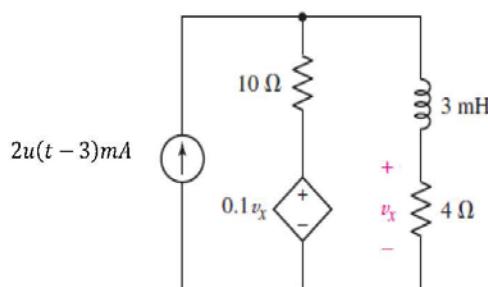


Fig. 19

// one last time I will recite the typical "solution steps":

1. Identify  $x$ : (usually the inductor current or capacitor voltage)
  2. Find the initial condition  $x_0 = x(t=t_0^-)$
  3. Determine  $R_{th}$  and  $\tau$
  4. Calculate  $X_F$
  5. Sub stutue into Eq. (3)
- //

Sol.

(a) To find the time constant ( $\tau$ ), we need consider the circuit for  $t > t_0$ .

To find  $R_{th}$  looking from the inductor terminals, we will use the following

$$R_{th} = \frac{V_{oc}}{I_{sc}}$$


To find  $V_{oc}$ :

$$\begin{aligned} V_{oc} &= 2 \times 10^{-3} \times 10 + 0.1v_x \\ v_x &= 0 \times (4\Omega) = 0V \\ V_{oc} &= 0.02V \end{aligned}$$

To find  $I_{sc}$ : (node current equation)

$$\begin{aligned} 2 \times 10^{-3} &= \frac{v_x - 0.1v_x}{10} + \frac{v_x}{4} \\ v_x &= \frac{80}{13.6} \times 10^{-3} \\ I_{sc} &= \frac{v_x}{4} = \frac{0.02}{13.6} A \\ R_{th} &= \frac{V_{oc}}{I_{sc}} = \frac{0.02}{0.02/13.6} = 13.6\Omega \end{aligned}$$
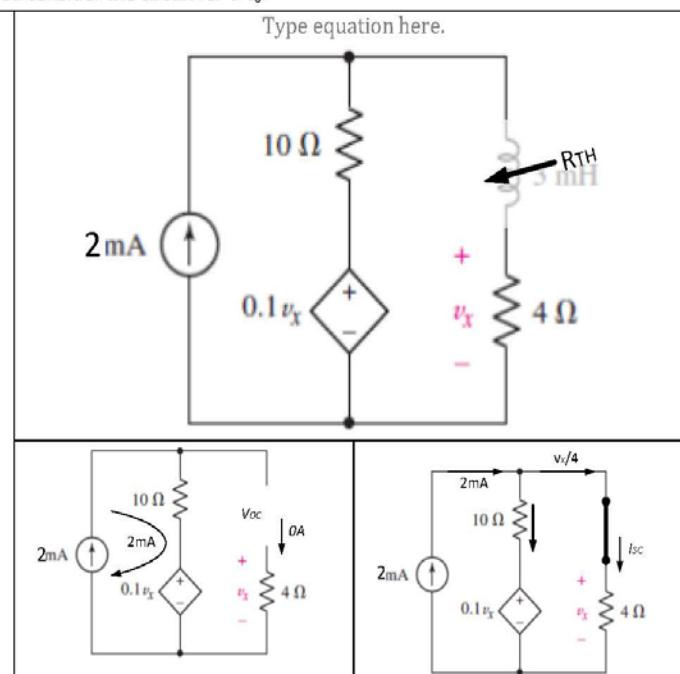
$$\begin{aligned} L &= 3 \times 10^{-3} \\ \tau &= \frac{L}{R} = \frac{3 \times 10^{-3}}{13.6} \\ \tau &= 0.22 \text{msec} \end{aligned}$$



(b) Find: (1)  $i_L$  before introducing the supply ( $t < 3$ ), and this represents the initial condition ( $i_o$ ) and (2)  $i_L$  as ( $t \rightarrow \infty$ ), and this represents the forced solution ( $i_f$ )

$t < 3$	$\begin{aligned} \frac{v_x}{4} &= \frac{v_x - 0.1v_x}{10} \\ 10v_x &= 3.6v_x \\ v_x &= 0 \\ i_o &= 0A \end{aligned}$	
$t \rightarrow \infty$	$I_f = \frac{0.02}{13.6} A$ <p>// Calculated in (a) as the short circuit current ...no need to repeat!//</p>	

Now we can write the expression of  $i_L(t)$

$$i_L(t) = \begin{cases} 0 & t \leq 3 \\ 1.47 \times 10^{-3} (1 - e^{-\frac{(t-3)}{0.22 \times 10^{-3}}}) & t \geq 3 \end{cases}$$


Since  $v_x = 4 \times i_L$

$$v_x(t) = \begin{cases} 0 & t \leq 3 \\ 5.88 \times 10^{-3} (1 - e^{-4545(t-3)}) & t \geq 3 \end{cases}$$

(c)

To plot obtain some points on p-curve

t	$i_L(t)$ (mA)	$p(t) = i_L^2 \times 4$ ( $\mu W$ )
3	0	0
$3+\tau$	0.929	3.454
$3+2\tau$	1.27	6.462
$3+3\tau$	1.397	7.804
$3+4\tau$	1.443	8.33
$3+5\tau$	1.46	8.528
$3+6\tau$	1.467	8.6

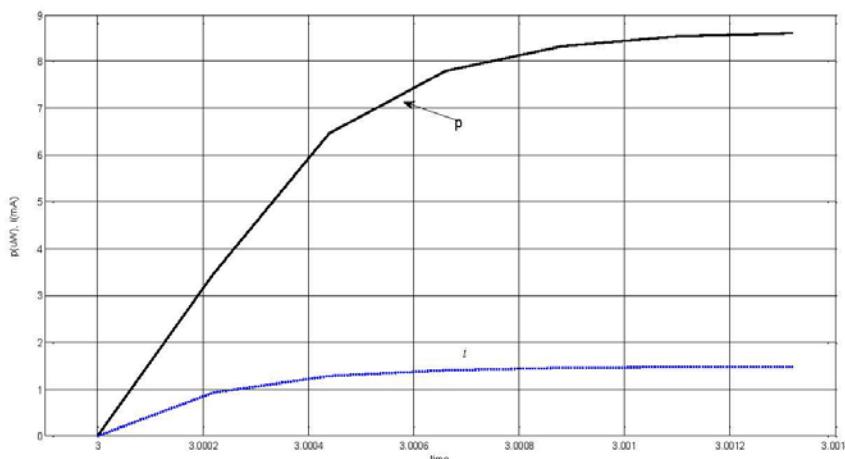

% the current saturates faster than the power!! (wow)

(d) and (e) are left for practice. (the circuit will be unstable if you have  $R_{th} \leq 0$ )

- Related book example: 8.7
- Book practice 8.9
-


### 2-Sequential Switching

- We have sequential switching if the switching occurs in the circuit more than one time.
- In the analysis of circuits with sequential switching we consider that the circuit transient is not necessarily ended between the subsequent switching actions. (the time between the subsequent switching is possibly a short time ( $<3\tau$ ))
- We use the solution of an earlier state to determine the initial condition of the following state.

**Example-2:** The voltage source in the circuit shown in Fig.20 has “internal” sequential switching. Before  $t=0$  there is no energy stored in the capacitor.

(a) Derive the expressions of  $v_o(t)$  for the intervals (i)  $t < 0$ ; (ii)  $0 \leq t \leq 4ms$ ; (iii)  $4ms \leq t \leq 8ms$ ; and  $8ms \leq t < \infty$ .

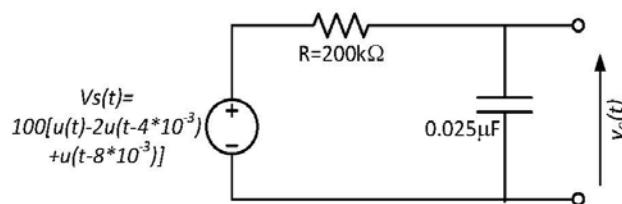
(b) Sketch  $v_s(t)$  and  $v_o(t)$  on the same coordinate axes.



Sol.

//simple circuit but complicated source! The following figure mitigates the supply and shows the shape of its voltage.

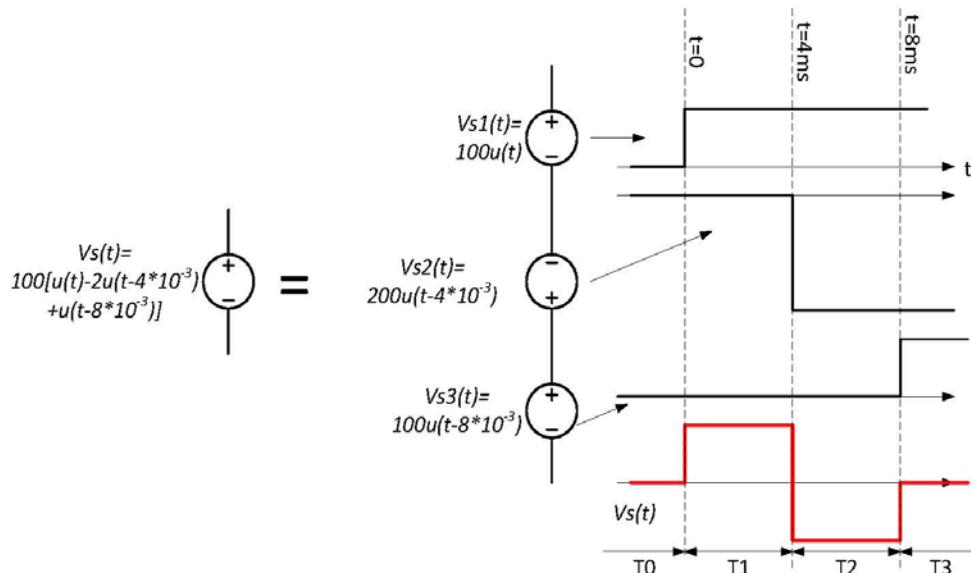
Some more, we have divided the time into 4 intervals  $T_0-T_3$  //



The RC circuit time constant,  $\tau = RC = 200 \times 10^3 \times 0.025 \times 10^{-6} = 5 \times 10^{-3} s$ .

Interval	Initial condition $V_0$	Forced Sol. $V_F = v_s$	$v_c(t) = V_F + (V_o - V_F)e^{-\frac{(t-t_0)}{\tau}}$	$V_c(\text{end of interval})$
T0 ( $-\infty < t \leq 0$ )	0	0	0	0
T1 ( $0 < t \leq 4ms$ )	0	100	$100 - 100e^{-200t}$	$100 - 100e^{-200 \times 4 \times 10^{-3}} = 55.1V$
T2 ( $4ms < t \leq 8ms$ )	55.1	-100V	$-100 + 155.1e^{-200(t-0.004)}$	$-100 + 155.1e^{-200(0.008-0.004)} = -30.31V$
T3 ( $8ms < t < \infty$ )	-30.31	0	$-30.13e^{-200(t-0.008)}$	0


(b)

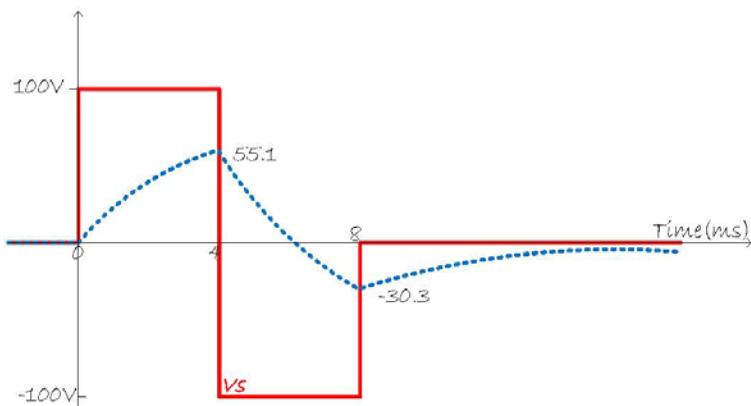


- Related Book Example: 8.9
- Related Book Practice 8.14
- Related Book Problems 41-45

Homework: Book Problem 35, 55

### The Operational Amplifier

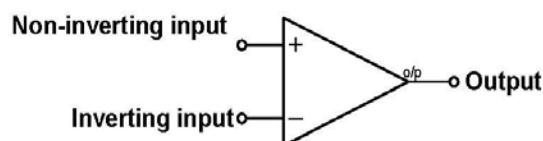


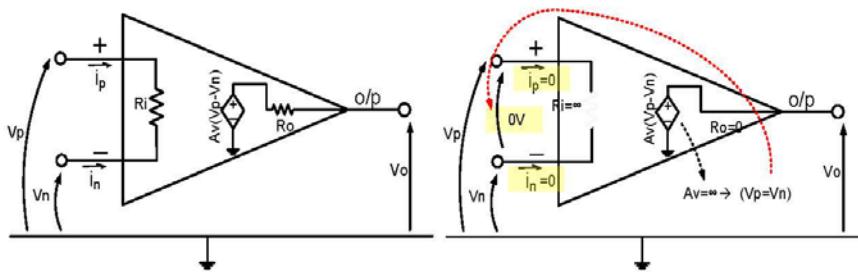

The ideal OPAMP:

- $R_i=0\Omega$
- $A_v=\infty$
- $R_o=0\Omega$

- Calculate  $V_o$  in the circuit shown

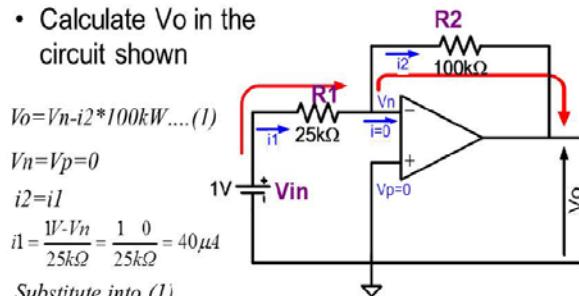

$$Substitute \text{ into (1)} \\ Vo = 0 - 40\mu A * 100k\Omega$$

Answer:  $Vo=-4V$

65. Obtain an expression for the voltage  $v_x$  as labeled in the op amp circuit of Fig. 8.94.


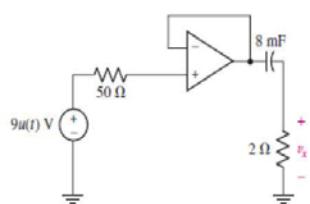


FIGURE 8.94

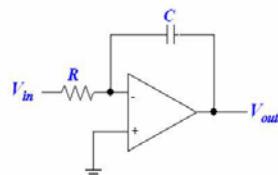Homework: Assuming an ideal OPAMP, show that  $v_{out} = -\frac{1}{RC} \int_{t_0}^t v_{in} dt + v_c(0)$





## Lectures of Electrical Engineering Department

**S**ubject Title: Electrical Networks

**C**lass: 2<sup>nd</sup> Stage

Lecture Contents	Lecture sequences:	4 <sup>nd</sup> lecture	Instructor Name: Omer Sharaf Aldeen Ali Abbawi
	<b>The major contents:</b>	<b>Transient Response of RLC Circuit</b>	
	<b>The detailed contents:</b>	<b>1-Natural Response of Parallel of RLC Circuit</b> <b>2- Analysis of Over-damped RLC Circuits</b> <b>3- Analysis of Critically-damped RLC Circuits</b> <b>4- Analysis of Under-damped RLC Circuits</b>	

**Chapter 2****Transient Response of RLC Circuit**

- The response of the “second-order” RLC circuit is very different than that of the “first order” RL or RC system studied in Chapter 1.
- This chapter presents the natural and step response of parallel and series RLC circuits.

**1. Natural response of Parallel RLC circuit**

To find the natural response of a parallel RLC circuit, assume the circuit shown in Fig. 1 has been initiated at  $t = 0$ , with initial capacitor voltage  $v_C(0^+) = V_0$  and initial inductor current,  $i_L(0^+) = I_0$ .

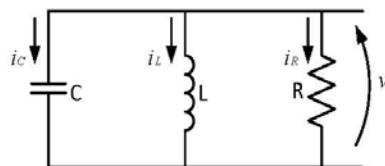


Fig. 1

The node current equation:

$$i_C + i_L + i_R = 0$$

Which can be written in terms of one variable, the parallel circuit voltage ( $v$ ):

$$C \frac{dv}{dt} + \frac{1}{L} \int_0^t v dt + \frac{v}{R} = 0 \quad (1)$$

To eliminate the integration in Eq. (1), we differentiate with respect to  $t$ :

$$C \frac{d^2v}{dt^2} + \frac{1}{L} v + \frac{1}{R} \frac{dv}{dt} = 0 \quad (2)$$

$$\frac{d^2v}{dt^2} + \frac{1}{LC} v + \frac{1}{RC} \frac{dv}{dt} = 0 \quad (3)$$

Eq. (3) is a second order DE, its solution has the form  $v = f(t)$  and represents the circuit behavior for  $t > 0$ .

In order to solve (3), assume:

$$v = A e^{rt} \quad (4)$$

Substituting (4) into (3) and simplify gives:



$$Ae^{st} \left( s^2 + \frac{s}{RC} + \frac{1}{LC} \right) = 0 \quad (5)$$

For the reason indicated in Chapter 1, we ignore the case in which the first term is zero, giving:

$$s^2 + \frac{s}{RC} + \frac{1}{LC} = 0 \quad (6)$$

- Eq. (6) determines the characters of  $v(t)$  and therefore it is known as the “**Characteristics Equation**”.
- Eq (6) is a quadric equation has 2 roots, usually defined as follows:

$$\begin{aligned} S_1 &= -\alpha + \sqrt{\alpha^2 - \omega_0^2} \\ S_2 &= -\alpha - \sqrt{\alpha^2 - \omega_0^2} \end{aligned} \quad (7)$$

Where:

$$\alpha = \frac{1}{2RC} \quad (8)$$

$\alpha$  is known as the **exponential damping coefficient or neper frequency**. And:

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (9)$$

$\omega_0$  is known as the **resonant frequency**.

Both  $s_1$  and  $s_2$  given in Eq. (7) gives solutions of Eq. (3) if substituted in (4); however the general solution is formed as follows:

$$v = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (10)$$

The polarity of the term under the root of Eq. (7) determines the nature of  $v$ . This term ( $\alpha^2 - \omega_0^2$ ) gives three distinctive forms of  $v$  when being positive, zero or negative, as follows:

- if  $\alpha > \omega_0$  gives two real roots and **Overdamped response**
- if  $\alpha = \omega_0$  gives two real and equal roots and **Critical response**
- if  $\alpha < \omega_0$  gives two complex conjugates roots and **Underdamped response**

The three forms will be discussed individually after the example.

**Example 1:** Consider a parallel RLC circuit having an inductance of 10 mH and a capacitance of 100  $\mu\text{F}$ . Determine the resistor values that would lead to overdamped and underdamped responses.

**Ans.:**

$$\text{From (9)} \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-2} \times 10^{-4}}} = 10^3 \text{ rad/sec}$$

For overdamped response:

$$\alpha > \omega_0$$

$$\frac{1}{2RC} > 1000$$

$$R < \frac{1}{2 \times 1000 \times 10^{-4}}$$

$$R < 5\Omega$$

For over damped response  $R > 5\Omega$

---

→ Book Practice 9.1

## 2. Analysis of Overdamped RLC circuit

The voltage of the overdamped circuit is in the form of Eq. (10)

$$v = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (10)$$

Where,  $s_1$  and  $s_2$  are given in terms of circuit parameters in equations (7)-(9).

Now to determine  $A_1$  and  $A_2$ , consider:

The initial capacitor voltage:

$$V_o = A_1 + A_2 \quad (11)$$

Take the differentiation of (10) at  $t=0^+$

$$\frac{dv(0^+)}{dt} = s_1 A_1 + s_2 A_2 \quad (12)$$

$$\text{Given: } i_C(0^+) = C \frac{dv(0^+)}{dt}$$

$$\text{Or} \quad \frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} \quad (13)$$

$i_C(0^+)$  can be determined by applying KCL in terms of the inductor and resistor current:

$$i_C(0^+) = -i_L(0^+) - i_R(0^+)$$

$$i_C(0^+) = -I_o - \frac{V_o}{R} \quad (14)$$

Now we can substitute (13) and (14) into (12) to form the second equation to determine  $A_1$  and  $A_2$ . However, closed form of this equation will not be given as it is difficult to memorize.

Usually the calculations procedure is given by the following sequence of applications:

- Given RLC,  $V_0$ ,  $I_0$
- Calculate  $\alpha$  and  $\omega_0$
- Calculate  $s_1$  and  $s_2$
- Eq. (14)
- Eq. (13)
- Eq. (12)
- Eq. (11) // alternatively this step can be done b4 Eq. (14) //
- Solve the simultaneous equations (11) and (12) obtain  $A_1$  and  $A_2$
- Write the expression of  $v$  Eq. (10)

**Example 2:** A source-free parallel RLC circuit is formed by  $200\Omega$ ,  $50mH$ , and  $0.2\mu F$ . At  $t=0$ , the capacitor voltage  $v_c(0) = 12V$  and the inductor current  $i_L(0) = 30mA$ .

- Find the expression of  $v(t)$ ,  $t > 0$
- Plot  $v(t)$ ,  $t > 0$

Ans.

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 200 \times 0.2 \times 10^{-6}} = 12.5 \times 10^3 \text{ rad/sec}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{50 \times 10^{-3} \times 0.2 \times 10^{-6}}} = 10^4 \text{ rad/sec}$$

Since  $\alpha > \omega_0$  the response is overdamped

$$s_{1,2} = -12.5 \times 10^3 \pm \sqrt{1.5625 \times 10^8 - 10^8} = (-1.25 \pm .75) \times 10^4$$

$$s_1 = -5000 \text{ and } s_2 = -20000$$

$$V_o = A_1 + A_2 = 12 \quad (1)$$

At  $t=0^+$ ,

$$i_L(0^+) = I_0 = 30 \times 10^{-3} A$$

$$i_R(0^+) = \frac{v(0^+)}{R} = \frac{12}{200} = 60 \times 10^{-3} A$$

$$i_C(0^+) = -i_L(0^+) - i_R(0^+) = -90 \times 10^{-3} A$$

$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = \frac{-0.09}{0.2 \times 10^{-6}} = -45 \times 10^4$$

$$\frac{dv(0^+)}{dt} = s_1 A_1 + s_2 A_2$$


$$-45 \times 10^4 = -0.5 \times 10^4 A_1 - 2 \times 10^4 A_2$$

$90 = A_1 + 4A_2$  (2)

(2)-(1)

$78 = 3A_2 \rightarrow A_2 = 26$ ,  $A_1 = -14$

$$v(t) = -14e^{-5000t} + 26e^{-20000t}$$

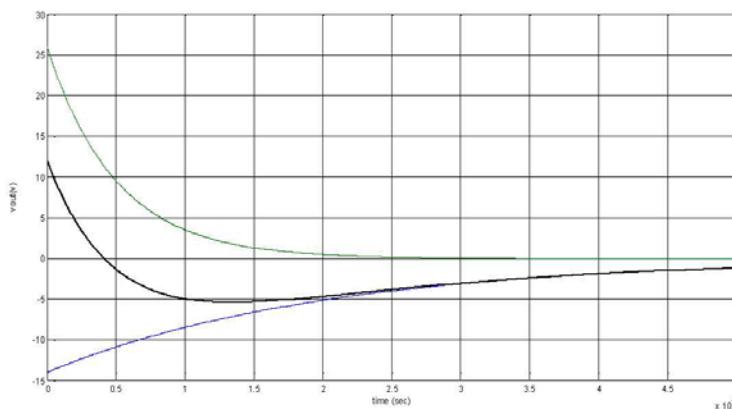

Related Book Example 9.2, 9.3, 9.4

Practice 9.2, 9.3, 9.4

### 3. Analysis of Underdamped RLC circuit

If  $\omega_0 > \alpha$ , the roots of the characteristics equation described in Eq. (7) become complex.

$$s_{1,2} = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2} \quad (15)$$

The second term usually denoted by  $\omega_d$ , where:

The damped radian frequency,  $\omega_d \triangleq \sqrt{\omega_0^2 - \alpha^2}$

So

$$s_{1,2} = -\alpha \pm j\omega_d \quad (16)$$

// the reasons for this name will be explained in the lecture //

Substitute in Eq. (10)

$$v = A_1 e^{(-\alpha+j\omega_d)t} + A_2 e^{(-\alpha-j\omega_d)t}$$

$$v = A_1 e^{-\alpha t} e^{j\omega_d t} + A_2 e^{-\alpha t} e^{-j\omega_d t}$$

$$v = e^{-\alpha t} (A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t})$$

Use Euler's identity ( $e^{jx} = \cos x + j\sin x$ )

$$v = e^{-\alpha t} (A_1 (\cos(\omega_d t) + j \sin(\omega_d t)) + A_2 (\cos(\omega_d t) - j \sin(\omega_d t)))$$

$$v = e^{-\alpha t} ((A_1 + A_2) \cos(\omega_d t) + j(A_1 - A_2) \sin(\omega_d t))$$

Choose a different notation for the constants

$$v = e^{-\alpha t} (B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t)) \quad (17)$$

Where  $B_1 = (A_1 + A_2)$  and  $B_2 = j(A_1 - A_2)$

Now we use the initial conditions to determine the constant  $B_1$  and  $B_2$  as follows:

$$v(0^+) = V_0 = B_1$$

and

$$\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = -\alpha B_1 + \omega_d B_2$$

**Example 3:** A source-free parallel RLC circuit is formed by  $20k\Omega$ ,  $8H$ , and  $0.125\mu F$ . At  $t=0$ , the capacitor voltage  $v_c(0) = 0V$  and the inductor current  $i_L(0) = -12.25mA$ .

- Find the expression of  $v(t), t > 0$
- Plot  $v(t), t > 0$

Ans.

$$\alpha = \frac{1}{2RC} = 200 \text{ rad/sec}$$

$$\omega_o = \frac{1}{\sqrt{LC}} = 10^3 \text{ rad/sec}$$

Since  $\alpha < \omega_o$  the response is underdamped

$$\omega_d = \sqrt{10^6 - 4 \times 10^4} = 400\sqrt{6}$$

$$s_{1,2} = -200 \pm j400\sqrt{6}$$

Since  $V_o=0$ ,

$B_1=0$

Also  $i_R(0^+) = 0$


$$i_C(0^+) = -i_L(0^+) = 12.25mA$$

$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = 98 \times 10^3 V/s$$

$$98 \times 10^3 = -\alpha B_1 + \omega_d B_2$$

$$B_2 = \frac{98 \times 10^3}{400\sqrt{6}} \cong 100V$$

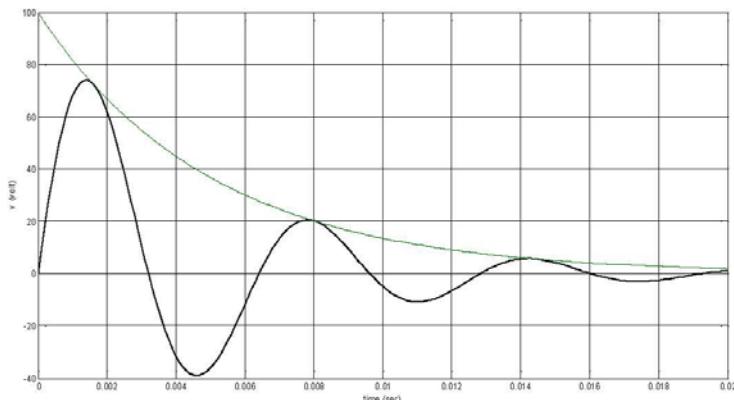Gives:  $v(t) = 100e^{-200t} \sin 979.8t V$ , for  $t \geq 0$



Related Book Example 9.6

Book Practice 9.6

Home work : Book Problem 31 P366

#### 4. Analysis of Critically-damped RLC circuit

If  $\alpha = \omega_0$ , the solution, the two roots of the DE will be identical

$$s_1 = s_2 = -\alpha \quad (18)$$

- If we carry on in the same way we will say that the solution will be similar to that of the 1<sup>st</sup> order DE given in chapter 1 ( $Ae^{-\alpha t}$ ).
- This solution however cannot handle two different initial conditions. So there is a problem with this solution. Indeed the reason of that is due to the assumption proposed in Eq. 10. This form is not valid when the two root identical.
- In critical damping case the solution has the following form:

$$v(t) = D_1 te^{-\alpha t} + D_2 e^{-\alpha t} \quad (19)$$

And the two arbitrary constant can be determined from initial conditions as follows:

$$V_o = D_2 \quad (20)$$

$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = D_1 - \alpha D_2 \quad (21)$$

**Example4: (book problem 23)** A critically damped parallel RLC circuit is constructed from component values  $40 \Omega$ ,  $8 \text{ nF}$ , and  $51.2 \mu\text{H}$ , respectively.

- Verify that the circuit is indeed critically damped.
- Explain why, in practice, the circuit once fabricated is unlikely to be truly critically damped.
- The inductor initially stores  $1 \text{ mJ}$  of energy while the capacitor is initially discharged. Determine the magnitude of the capacitor voltage at  $t = 500 \text{ ns}$ , the maximum absolute capacitor voltage, and the settling time.

Ans.

$$(a) \alpha = \frac{1}{2RC} = \frac{10^9}{2*40*8} = 1.5625 \times 10^6$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{51.2 * 8 * 10^{-15}}} = 1.5625 \times 10^6$$

$\therefore \alpha = \omega_0$  critical damping

(b) In practice it is unusual to obtain components that are closer than 1 percent of their specified values. Thus, obtaining critical damping case not very likely. The model ignores the stray elements such as connection leads, the effect of temperature.

(c) determine  $v(t)$

$$D_2 = V_o = 0$$

$$I_o = \sqrt{\frac{2W_L}{L}} = \sqrt{\frac{2 * 10^{-3}}{51.2 * 10^{-6}}} = 6.25A$$

$$i_C(0^+) = -i_L(0^+) - i_R(0^+) = -6.25A$$

$$\frac{dv_C(0^+)}{dt} = \frac{i_C(0^+)}{C} = \frac{-6.25}{8 * 10^{-9}} = -0.78125 \times 10^9 V/s$$

$$-0.78125 \times 10^9 = D_1 - \alpha D_2 = D_1$$

$$v(t) = -0.78125 \times 10^9 t e^{-1.5625 \times 10^6 t}$$

$$v(500ns) = -0.78125 \times 10^9 (500 \times 10^{-9}) e^{-1.5625 \times 10^6 (500 \times 10^{-9})}$$

$$v(500ns) = -178.8V$$

$$\frac{dv(t)}{dt} = -0.78125 \times 10^9 (t * -1.5625 \times 10^6 e^{-1.5625 \times 10^6 t} + e^{-1.5625 \times 10^6 t})$$

Denote the peak voltage time by  $tp$ :

$$0 = -0.78125 \times 10^9 (tp * -1.5625 \times 10^6 e^{-1.5625 \times 10^6 tp} + e^{-1.5625 \times 10^6 tp})$$

$$tp = \frac{-1}{-1.5625 \times 10^6} = 0.64 \mu sec$$

$$vp = -0.78125 \times 10^9 (0.64 * 10^{-6}) e^{-1.5625 \times 10^6 (0.64 * 10^{-6})}$$

$$vp = -184V$$

Settling time ( $ts$ ) is the time at which the voltage drop to 5% of its peak

$$0.04(-184) = -0.78125 \times 10^9 t s e^{-1.5625 \times 10^6 t s} = -9.2V$$

$$t s e^{-1.5625 \times 10^6 t s} = 11.776 \times 10^{-9}$$

This nonlinear equation can be solved by iteration  $ts=3.676 \mu sec$ .

Related Book Example 9.5

Practice 9.5

Homework

The natural voltage response of the circuit in Fig. 8.1 is

$$v(t) = 75e^{-800t}(\cos 6000t - 4 \sin 6000t) V, \quad t \geq 0,$$

when the inductor is 400 mH. Find (a)  $C$ ; (b)  $R$ ; (c)  $V_0$ ; (d)  $I_0$ ; and (e)  $i_L(t)$ .

Find the response  $v_R(t)$  for  $t > 0$  in the circuit in Fig. 8.102. Let  $R = 3 \Omega$ ,  $L = 2 \text{ H}$ , and  $C = 1/18 \text{ F}$ .

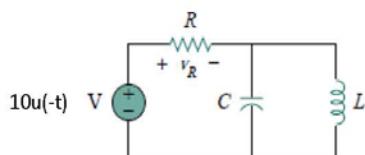


Figure 8.102 For Prob. 8.54.



## Lectures of Electrical Engineering Department

**S**ubject Title: Electrical Networks

**C**lass: 2<sup>nd</sup> Stage

Lecture Contents	Lecture sequences:	5 <sup>nd</sup> lecture	Instructor Name: Omer Sharaf Aldeen Ali Abbawi
	<b>The major contents:</b>	<b>Transient Response of RLC Circuit</b>	
	<b>The detailed contents:</b>	<b>1- The Complete Response pf Parallel RLC Circuits</b> <b>2-Derivation of Step Response Equations</b>	

**Chapter 2****THE COMPLETE RESPONSE OF THE PARALLEL RLC CIRCUIT**

In this lecture we will consider a parallel RLC with any initial conditions (inductor current and capacitor voltage) and we will determine the transient response after applying a DC current source at  $t=0$ . Unlike natural response case, the presence of the DC source causes non-discharged final conditions.

**1. Derivation of Step Response Equations**

Fig. 1 shows a parallel RLC circuit with initial capacitor voltage  $v_C(0^+) = V_0$  and initial inductor current,  $i_L(0^+) = I_o$ ; and a current source that is applied at  $t=0$ .

Notice: that the DC voltage source cannot be applied as the inductor will short circuit it!!

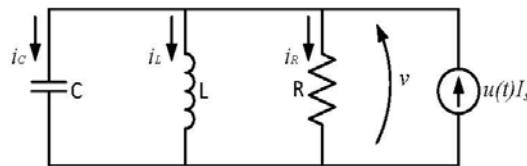


Fig. 1

The node current equation:

$$i_C + i_L + i_R = I \quad (1)$$

By following steps similar to those used in last lecture, leads to:

$$\frac{d^2v}{dt^2} + \frac{1}{LC}v + \frac{1}{RC}\frac{dv}{dt} = 0 \quad (2)$$

Eq. (2) is identical to the natural response equation and leads to the same results obtained, which are:

- Over damping:  $v = A_1 e^{s_1 t} + A_2 e^{s_2 t}$  (3)

- Under damping:  $v = e^{-\alpha t}(B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t))$  (4)

- Critical damping:  $v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$  (5)

The only difference in this case is that the effect of the supply must be taken into account (i.e.

$$i_C(t = 0^+) = I_s - I_o - \frac{V_0}{R}$$

The evaluation of  $v$  of the parallel branches, however, is not sufficient to reveal full analysis as the expression of  $v$ , which approaches 0 at  $t \rightarrow \infty$  does not reflect the end value of the inductor current. On the other hand if we have the inductor current we can find  $v$  easily! Therefore in the analysis of DC supplied parallel RLC circuit we will solve for  $i_L(t)$  rather than  $v$ .

Before explaining the procedure by examples, let's look at the general expression of  $i_L(t)$  as follows:


$$i_L(t) = I_f + i_n = I_s + (\text{natural response function Eq. (3,4 or 5)}) \quad (6)$$

The arbitrary constants of the natural response equation are determined from the initial conditions:

$$i_L(t = 0^+) = I_0 \text{ and } \frac{di_L(t = 0^+)}{dt} = \frac{1}{L} V_o$$

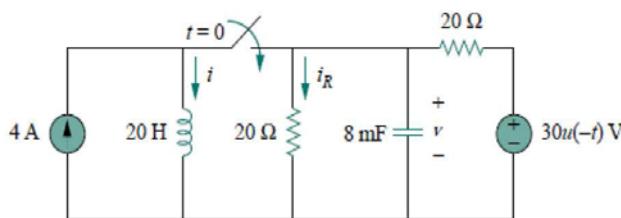Example 1:

In the circuit in Fig. 8.23, find  $i(t)$  and  $i_R(t)$  for  $t > 0$ .



Sol.

$$I_o = 4A; V_o = 15V; v_L(0^+) = 15V; I_f = 4A$$

$$\alpha = \frac{1}{2R_{eq}C} = \frac{1000}{2 * 10 * 8} = 6.25 \frac{\text{rad}}{\text{sec}}; \omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 * 0.008}} = 2.5 \text{ rad/sec}$$

Notice that the parallel RLC circuit has two branches of resistors with  $20\Omega$  each. Therefore the equivalent resistor is  $10\Omega$

$\alpha > \omega_o$  Overdamping response:

$$S_1 = -\alpha + \sqrt{\alpha^2 - \omega_o^2} = -6.25 + 5.73 = -0.522; S_2 = -6.25 - 5.73 = -11.98$$

$$i = I_f + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$i = 4 + A_1 e^{-0.522t} + A_2 e^{-11.98t}$$

At  $t=0$ ,  $i=I_0$ , gives

$$A_1 + A_2 = 0$$

$$\frac{di(t=0^+)}{dt} = \frac{v_L(t=0^+)}{L} = A_1 S_1 + A_2 S_2$$

$$\frac{15}{20} = -0.522A_1 - 11.98A_2$$

$$0.75 = -0.522A_1 + 11.98A_2; A_1 = 0.0655; A_2 = 0.0655$$

$$i = 4 + 0.0655e^{-0.522t} - 0.0655e^{-11.98t}$$

$$v_L = L \frac{di}{dt} = 20[-0.0342e^{-0.522t} + 0.7847e^{-11.98t}]$$

$$i_R = \frac{v_L}{20} = [-0.0342e^{-0.522t} + 0.7847e^{-11.98t}]$$

**Practice:** show that the energy dissipated in the resistors is equivalent to the energy supplied by the current source plus the energy initially stored in the capacitor.

Homework:

The switch in Fig. 8.4 was open for a long time but closed at  $t = 0$ . Determine: (a)  $i(0^+)$ ,  $v(0^+)$ , (b)  $di(0^+)/dt$ ,  $dv(0^+)/dt$ , (c)  $i(\infty)$ ,  $v(\infty)$ .


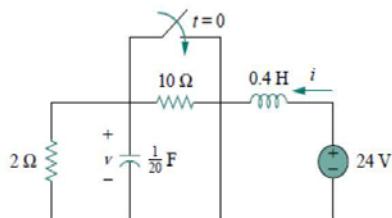



Figure 8.4 For Practice Prob. 8.1.

In the circuit of Fig. 8.5, calculate: (a)  $i_L(0^+)$ ,  $v_C(0^+)$ ,  $v_R(0^+)$ , (b)  $di_L(0^+)/dt$ ,  $dv_C(0^+)/dt$ ,  $dv_R(0^+)/dt$ , (c)  $i_L(\infty)$ ,  $v_C(\infty)$ ,  $v_R(\infty)$ .

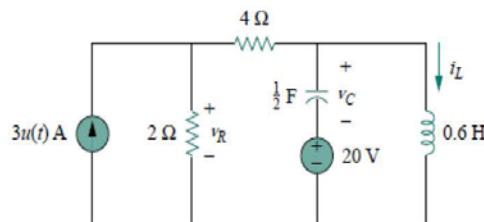

**Example 2: (Book Problem 52)**

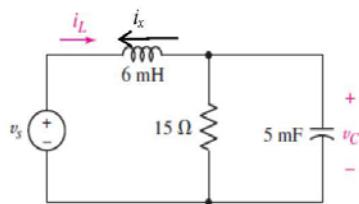52. Consider the circuit depicted in Fig. 9.52. If  $v_s(t) = -8 + 2u(t)$  V, determine  
 (a)  $v_c(0^+)$ ; (b)  $i_L(0^+)$ ; (c)  $v_c(\infty)$ ; (d)  $v_c(t = 150 \text{ ms})$ .



Sol:

$$(a) v_c(0^+) = V_0 = -8V$$

$$(b) i_L(0^+) = I_0 = -\frac{8}{15}A$$

$$(c) v_c(\infty) = -6V$$

// the direction of  $i_L$  marked in the fig accompanying the question is opposite to that taken into consideration so just treat  $i_x$  as  $(-i_L)$  //

// solution plan: find  $i_x \rightarrow$  find  $v_L \rightarrow$  then  $v_c = v_L + v_s \oplus$  //

// 1-) determination of the type of response://

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 15 \times 5 \times 10^{-3}} = 6.67 \text{ rad/sec}$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{10^3}{\sqrt{6 \times 5}} = 182.6 \text{ rad/sec}$$

$$\omega_o > \alpha \text{ Underdamping response } \omega_d = \sqrt{\frac{10^6}{30} - \frac{10^6}{22500}} \cong 182.45 \text{ rad/sec}$$

// 2-) Initial and forced conditions //

$$I_0 = \frac{8}{15} = 0.533A, V_0 = -8V, v_L(t = 0^+) = v_c - v_s = -8 - (-6) = -2V, I_f = \frac{6}{15} = 0.4A$$

// write the equation and find the constants for  $i_L$  //

$$i_X = I_f + e^{-\alpha t} (B_1' \cos(\omega_d t) + B_2' \sin(\omega_d t))$$

$$\text{At } t=0^+ \quad 0.533 = 0.4 + B_1; B_1 = 0.133$$

$$\frac{di_x(t=0^+)}{dt} = -\frac{2}{0.006} = \omega_d B'_2 - \alpha B'_1$$

$$B_2 = \frac{-333.3 + 6.67 \times 0.133}{182.45} = -1.822$$

$$i_L = 0.4 + e^{-6.7t} (0.133 \cos(182.45t) - 1.822 \sin(182.45t))$$

$$v_L = 0.006 [e^{-6.7t} (-0.133 \times \omega_d \sin(\omega_d t) - 1.822 \omega_d \cos(\omega_d t)) + (0.133 \cos(\omega_d t) - 1.822 \sin(\omega_d t))(-6.7e^{-6.7t})]$$


$$v_L = e^{-6.7t} (-2 \cos(\omega_d t) - 0.072 \sin(\omega_d t))$$

$$v_L(t = 150ms) = e^{-6.7 \times 0.15} (-2 \cos(182.45 * 0.15) - 0.072 \sin(182.45 * 0.15))$$

$$v_L(t = 150ms) = 0.433V$$


$$v_C = v_S + v_L = -6 + 0.4325 = -5.567V$$


---

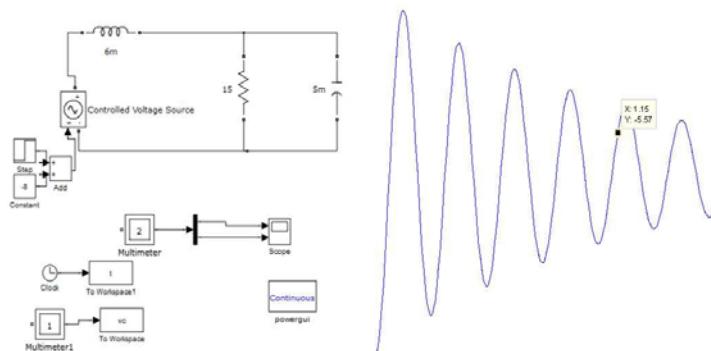

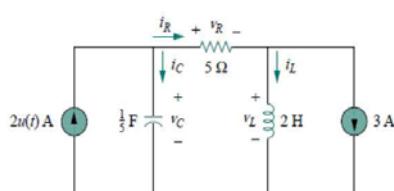**Practice:**

For the circuit in Fig. 8.7, find: (a)  $i_L(0^+)$ ,  $v_C(0^+)$ ,  $v_R(0^+)$ ,  
 (b)  $di_L(0^+)/dt$ ,  $dv_C(0^+)/dt$ ,  $dv_R(0^+)/dt$ , (c)  $i_L(\infty)$ ,  $v_C(\infty)$ ,  $v_R(\infty)$ .





## Lectures of Electrical Engineering Department

**S**ubject Title: Electrical Networks

**C**lass: 2<sup>nd</sup> Stage

Lecture Contents	Lecture sequences:	6 <sup>th</sup> lecture	Instructor Name: Omer Sharaf Aldeen Ali Abbawi
	<b>The major contents:</b> <b>Transient Response of RLC Circuit</b>		
	<b>The detailed contents:</b> <b>1- Natural Response of Series RLC Circuits</b> <b>2- Step Response of Series RLC Circuits</b>		

**Chapter 2****Transient Response of Series RLC Circuit**

The procedure of natural and step response analysis for the series RLC circuit is similar to that of the parallel circuit. The only difference is in the definition of the damping ratio,  $\alpha$ .

Your selection of the most appropriate variable for solution will also differ as you will see shortly.

**1. Natural response of series RLC circuit**

Assume the circuit shown in Fig. 1 is initiated at  $t = 0$ , with initial capacitor voltage  $v_C(0^+) = V_0$  and initial inductor current,  $i_L(0^+) = I_0$ .

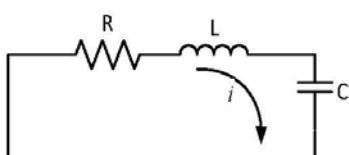


Fig. 1

The loop voltage equation:

$$v_R + v_L + v_C = 0$$

write the equation in terms of one variable, the current ( $i$ ):

$$iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0 \quad (1)$$

Differentiate with respect to  $t$ , rearrange and divide by L:

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0 \quad (2)$$

Eq. (2) is similar to the parallel voltage equation of the parallel RLC circuit [Eq. (3) week#4]. Therefore, without repeating the derivation, we are going to state the characteristics equation and the current equations for the three cases. (The bold marks the difference compared to parallel voltage case):

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad (3)$$

$$S_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad (4)$$

Where:  $\alpha = \frac{R}{2L}$  (Rad/sec) (5)

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (\text{Rad/sec}) \quad (6)$$

The current equation depends on the value under the root square in Eq. (4)

- if  $\alpha > \omega_0$  Overdamping :  $i = A_1 e^{s_1 t} + A_2 e^{s_2 t}$  (7)

- if  $\alpha < \omega_0$  Underdamping  $i = e^{-\alpha t}(B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t))$  (8)

where  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$  (9)

- if  $\alpha = \omega_0$  Critical damping :  $i = D_1 t e^{\alpha t} + D_2 e^{\alpha t}$  (10)

In case of natural response it is a good choice to solve for the current, ( $i$ ) especially if need to calculate more than one quantity (for example  $i$  and  $v_L$ ) because the current of the three elements is equal.

**Example 1** The  $0.1 \mu F$  capacitor in the circuit shown in Fig 2 is charged to  $100 V$ . At  $t = 0$  the capacitor is discharged through a series combination of a  $560 \Omega$  resistor and  $100 mH$  inductor.

- Find  $i(t)$  for  $t > 0$ .
- Find  $v_C(t)$  for  $t > 0$ .

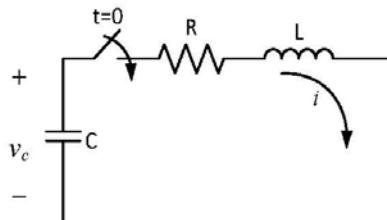


Fig. 2

**Sol:**

$$\alpha = \frac{R}{2L} = \frac{560}{2 \times 0.1} = 2800 \text{ rad/sec}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.1 \times 10^{-7}}} = 10^4 \text{ rad/sec}$$

((Underdamping ))

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{10^8 - 2800^2} = 9600 \text{ rad/sec}$$

$$i = e^{-\alpha t}(B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t))$$

$$i(0^+) = B_1 = 0$$

$$\frac{di(0^+)}{dt} = \frac{v_L(0^+)}{L}$$

$$-v_C(0^+) + i(0^+)R + v_L(0^+) = 0 \text{ gives } v_L(0^+) = 100V$$

$$\frac{di(0^+)}{dt} = 1000A/sec = \omega_d B_2 - \alpha B_1 \text{ gives } B_2 = \frac{1000}{9600} \approx 0.1042A$$

$$i = 0.1042e^{-2800t} \sin(9600t) \quad t > 0$$

$$v_c = \frac{1}{C} \int i dt \quad // \text{can be solved as } \int u dv \dots \text{but let's look for alternative} //$$

OR  $v_c(t) = iR + v_L = iR + L \frac{di}{dt}$

$$v_c = 560 \times \frac{10}{96} e^{-2800t} \sin(9600t)$$

$$+ 0.1 \left( \frac{10}{96} \right) [e^{-2800t} (9600 \cos 9600t) + \sin(9600t) (-2800e^{-2800t})]$$

$$v_c = e^{-2800t} [100 \cos 9600t - 29.17 \sin 9600t]$$

// what will be the case if we determined  $v_C$  first ...??? ....try //

**Practice:** For the circuit in example 1,

- draw the variation of the capacitor voltage against time,
- determine the settling time, and
- show the all the energy initially stored in the inductors is dissipated in R.

## 2. Step response of series RLC circuit

In this case a DC source will be present in the circuit after the switching, this leads to  $v_C(t = \infty) = V_F$  as seen in Fig. 3.

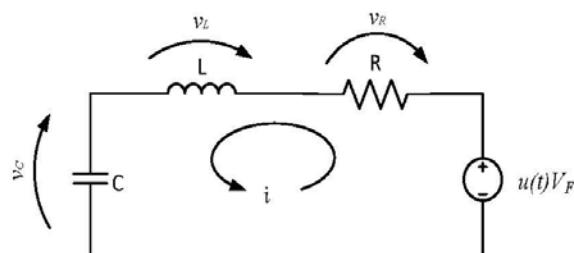


Fig. 3

In case of step response, the capacitor voltage is usually a good choice because it is the only variable which has a non-zero forced part (Solving for other variables is also possible). The forced response expressions for  $i_c$  for the three types of response are as follows:

- Overdamping :  $v_C = V_F + A_1 e^{s_1 t} + A_2 e^{s_2 t}$  (11)

- Underdamping  $v_C = V_F + e^{-\alpha t} (B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t))$  (12)

- Critical damping :  $v_C = V_F + D_1 t e^{st} + D_2 e^{st}$  (13)

**Example 2:** In the circuit shown in Fig. 4, switch 1 has been in position (a) and switch two has been closed for a long time. At  $t=0$  switch 1 moves to position (b) and switch 2 opens simultaneously. Find  $v_C(t)$  for  $t>0$ .

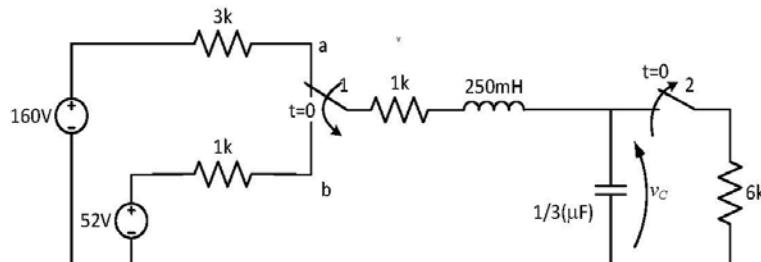


Fig. 4

**Sol:**

Initial and Forced Quantities:

$$V_0 = v_C(0^-) = \frac{160}{3k + 1k + 6k} 6k = 96V$$


$$V_F = v_C(\infty) = 52V$$

$$I_0 = i_L(0^-) = \frac{160}{10k} = 16mA$$

$$I_F = i_L(\infty) = 0$$

Type of response:

The circuit for  $t>0$

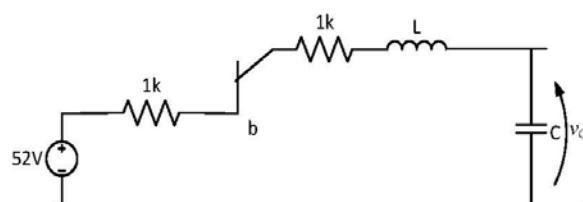

$$\alpha = \frac{R}{2L} = \frac{2000}{2 \times 0.25} = 4000 \text{ rad/sec}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{4} \times \frac{1}{3} \times 10^{-6}}} = 2000\sqrt{3} \text{ rad/sec}$$

$\alpha > \omega_0$  overdamping response

$$S_{1,2} = -4000 \pm 1000\sqrt{16 - 12} = -4000 \pm 2000$$

$$S_1 = -2000; S_2 = -6000 \text{ (rad/sec)}$$

$$v_C = V_F + A_1 e^{-2000t} + A_2 e^{-6000t}$$

At  $t=0^+$

$$96 = 52 + A_1 + A_2$$

$$A_1 + A_2 = 44V \quad \dots \dots (1)$$

$$\frac{dv_C(0^+)}{dt} = \frac{I_o}{C} = \frac{16 \times 10^{-3}}{\frac{1}{3} \times 10^{-6}} = 48 \times 10^3 V/\text{sec}$$

$$48 \times 10^3 = -2000A_1 - 6000A_2$$

$$24 = -A_1 - 3A_2 \quad \dots \dots (2)$$

Add (1) and (2)


$68 = -2A_2 \dots \dots \text{gives } A_2 = -34$

$$A_1 = 78$$

$$v_C = 52 + 78e^{-2000t} - 34e^{-6000t}V, \quad t>0$$

### Example 3 (with dependent source)

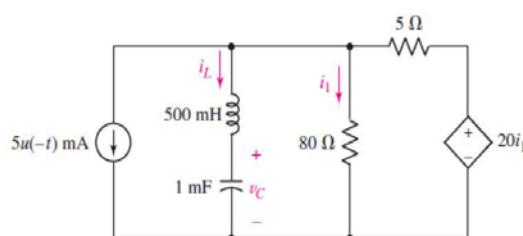49. Obtain an expression for  $i_L$  as labeled in Fig. 9.49 which is valid for all  $t > 0$ .




■ FIGURE 9.49

Sol.

Determination of initial conditions

Consider the circuit with  $t < 0$

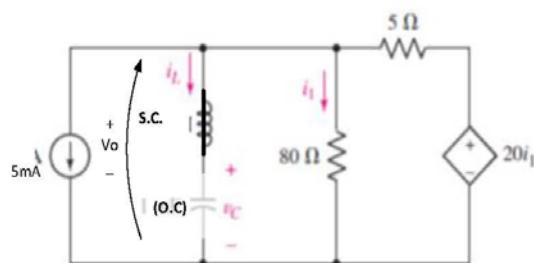

Write the node currents equation:

$$5 \times 10^{-3} + \frac{V_o}{80} + \frac{V_o - 20i_1}{5} = 0$$

$$5 \times 10^{-3} + \frac{V_o}{80} + \frac{V_o - 20 \left( \frac{V_o}{80} \right)}{5} = 0$$


$$5 \times 10^{-3} + \frac{V_o}{80} + \frac{V_o}{5} - \frac{V_o}{20} = 0$$

$$0.4 + V_o + 16V_o - 4V_o = 0$$

$$V_o = -\frac{0.4}{13}; \text{ and } I_o = 0$$

For  $t > 0$

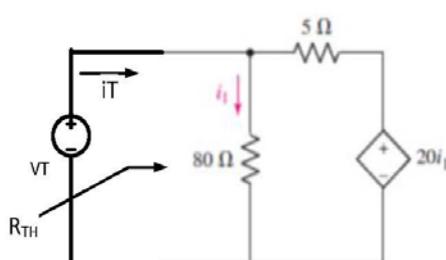Determine the equivalent resistor ( $R_{TH}$ ).



By applying a test voltage source ( $V_T$ ), the resultant current is ( $I_T$ ) and  $R_{TH} = \frac{V_T}{I_T}$

$$I_T = \frac{V_T}{80} + \frac{V_T - 20 \left( \frac{V_T}{80} \right)}{5} = \frac{V_T}{80} + \frac{V_T}{5} - \frac{V_T}{20}$$

$$80I_T = V_T + 16V_T - 4V_T \text{ gives } R_{TH} = \frac{V_T}{I_T} = \frac{80}{13} \Omega$$

#### Determination of type of response

$$\alpha = \frac{R}{2L} = \frac{80}{13} = 6.153 \text{ (rad/sec)}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.5 \cdot 10^{-3}}} = \frac{100}{\sqrt{5}} \approx 44.72 \text{ (Rad/sec)}$$

Under damping response:

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \approx 44.3 \text{ rad/sec}$$

$$i = e^{-\alpha t} (B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t))$$

At  $t=0^+$ ,  $i(0+)=0$  gives  $B_1=0$

$$i = e^{-\alpha t} (B_2 \sin(\omega_d t))$$

$$\frac{di}{dt} = \frac{v_L(0^+)}{L} = \frac{-V_o - I_o R}{0.5} = -2 \left( -\frac{0.4}{13} + 0 \right)$$

$$\frac{di(t=0^+)}{dt} = \frac{0.8}{13} = \omega_d B_2$$

$$B_2 \approx 1.39mA$$

$$i = 1.39e^{-6.153t} \sin(44.3t)$$

---


$$i_1 = -i = -1.39e^{-6.153t} \sin(44.3t)$$

H.W.

Book Problem (Chapter 9) 56 Parts (a) and (b) only. And Book Problem 57



# Lectures of Electrical Engineering Department

**S**ubject Title: Electrical Networks

**C**lass: 2<sup>nd</sup> Stage

Lecture Contents	Lecture sequences:	7 <sup>th</sup> lecture	Instructor Name: Omer Sharaf Aldeen Ali Abbawi
	<p><b>The major contents:</b></p> <p><b>Balanced Three-Phase Circuits</b></p> <p><b>The detailed contents:</b></p> <p><b>1- The Three Phase Y- connected Source</b></p> <p><b>2- Balanced Three-Phase System</b></p> <p><b>3- The Three Phase Delta - connected Source</b></p>		

### Chapter 3

#### Balanced Three-Phase Circuits

The electric energy is generated, transmitted and distributed using three-phase systems for economical reason. Large loads, such as industrial apparatus, are three-phase loads. This chapter introduces the three-phase systems and its basic analysis<sup>1</sup>.

This lecture defines the basic elements, connections and circuits of the three-phase system.

##### 1. The three-phase Y-connected source

Consider the three ac supplies shown in Fig. 1. The three sources represent a balanced three-phase supply if the voltages of the three supplies have the following form (in various representations)

##### 1-Instantaneous representation:

$$\begin{array}{ll} v_{an} = V_{ph} \sin(2\pi ft + \phi) & v_{an} = V_{ph} \sin(2\pi ft + \phi) \\ v_{bn} = V_{ph} \sin(2\pi ft + \phi - 120^\circ) & v_{bn} = V_{ph} \sin(2\pi ft + \phi + 120^\circ) \\ v_{cn} = V_{ph} \sin(2\pi ft + \phi - 240^\circ) & OR \quad v_{cn} = V_{ph} \sin(2\pi ft + \phi + 240^\circ) \\ \dots(1) & \dots(2) \end{array}$$

##### 2-Vector representation:

$$\begin{array}{ll} V_{an} = V_{ph} \angle \phi & V_{bn} = V_{ph} \angle \phi \\ V_{bn} = V_{ph} \angle \phi - 120^\circ & V_{bn} = V_{ph} \angle \phi + 120^\circ \\ V_{cn} = V_{ph} \angle \phi - 240^\circ & V_{cn} = V_{ph} \angle \phi + 120^\circ \\ \dots(3) & \dots(4) \end{array}$$

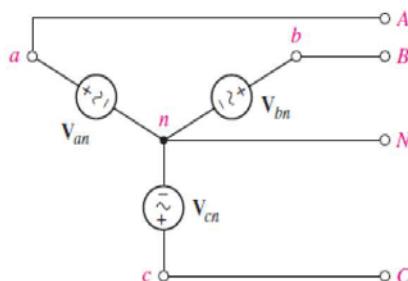


Fig. 1

##### Positive and negative sequence:

In equations (1) and (3), we can think of the voltage  $v_{an}$  as "leading"  $v_{bn}$  by  $120^\circ$ ; and the voltage  $v_{bn}$  as leading  $v_{cn}$  by  $120^\circ$ . So the voltages are arranged as  $v_{an} - v_{bn} - v_{cn}$  as the time progresses. This sequence is known as the **positive sequence** of voltages.

<sup>1</sup> The material of this chapter is covered in chapter 12 of the textbook

In contrast, for the voltages represented in equations (2) and (4), the voltage  $v_{an}$  as "lagging"  $v_{bn}$  by  $120^\circ$ ; and  $v_{bn}$  lags  $v_{cn}$  by  $120^\circ$ . So the voltages are arranged as  $v_{an} - v_{cn} - v_{bn}$  as the time progresses. This sequence is known as the **negative sequence** of voltages.

To emphasize the above Fig. 2 shows the three voltages represented in Eq. (1) and Fig. 3 shows the vectors represented in Eq. (3). In Fig. 2 and Fig. 3 the,  $\phi$  is considered to be zero and this is common practice.

In summary, we can say that the three-phase voltage system is composed of three ac voltages of:

- Identical frequency,
- Equal amplitudes, and
- Phase shift of  $120^\circ$  between the three sources

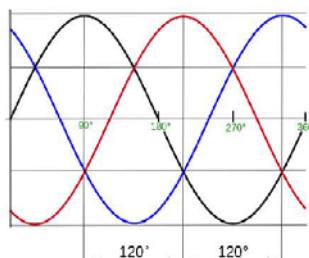


Fig. 2

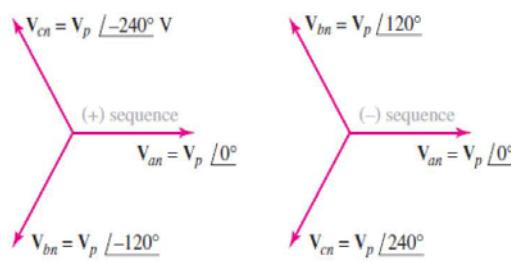


Fig. 3

(a)

(b)

To explain the practical implementation of three-phase source; The electricity is generated in bulk by a three-phase generator with rotating magnet that induces the voltage in three identical stator windings which are displaced by  $120^\circ$  in space as shown in Fig. 4. This maintains identical frequency and phase constant  $120^\circ$ -phase displacement of the three sources representing the voltages induced in the three windings.

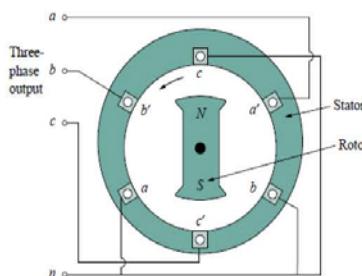


Fig. 4

### The "a" operator

We can write the three phase quantities in more brief form by using the "a" operator. Where:

$$a \triangleq 1\angle 120^\circ \text{ or } a \triangleq 1\angle -240^\circ \quad \dots(5)$$

The effect of multiplying a vector by a is that the vector rotates by  $120^\circ$ . Consequently:

$$a^2 = 1\angle -120^\circ \text{ or } a^2 = 1\angle 240^\circ \quad \dots(6)$$

In positive sequence voltages:

$$V_{bn} = a^2 V_{an} \text{ and } V_{cn} = a V_{an} \quad \dots(7)$$

And in negative sequence:

$$V_{bn} = a V_{an} \text{ and } V_{cn} = a^2 V_{an} \quad \dots(8)$$

### Zero-Sum property

One important property of the three-phase voltages is that it sums zero, we can show that analytically or graphically as shown below:

Based on Eq. (1)

$$v_{an} + v_{bn} + v_{cn} = V_{ph}[\sin(2\pi ft + \phi) + \sin(2\pi ft + \phi - 120) + \sin(2\pi ft + \phi + 120)]$$

Using the trigonometric identity:  $\sin(A + B) = \sin A \cos B + \cos A \sin B$  and denoting  $2\pi ft + \phi$  by x

$$v_{an} + v_{bn} + v_{cn} = V_{ph}[\sin x + \sin(x - 120) + \sin(x + 120)]$$

$$= \sin x + \sin x \cos(-120) + \cos x \sin(-120) + \sin x \cos(120) + \cos x \sin(120)$$

$$= \sin x [1 + \cos(-120) + \cos(120)] = \sin x [1 - 0.5 - 0.5] = 0$$

The graphical proof is based on adding the three vectors as shown in Fig. 5

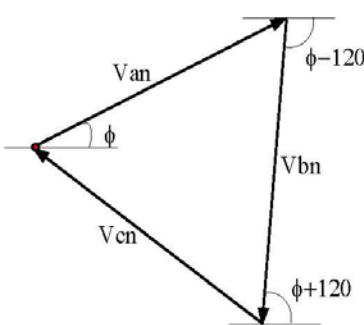


Fig. 5

### The Phase Voltages and the Line Voltages

Referring to Fig. 1, in the configuration shown the sources is said to be Y-connected. The supply common point is known as the neutral point denoted by N and the other individual lines (A, B, and C) are known as the

supply lines. The voltage between any line and the common neutral line is the **phase voltage**. The three phase voltages are ( $V_{AN}$ ,  $V_{BN}$  and  $V_{CN}$ ).

The line-to-line voltages are the three voltages between the three lines; defined as:

$$\begin{aligned} V_{AB} &= V_{AN} - V_{BN} = V_{ph} - (-aV_{ph}) = V_{ph}(1 + a) = V_{ph}[(1 + \cos(120)) + j(\sin(120))] = V_{ph} \left[ \frac{3}{2} + j \frac{\sqrt{3}}{2} \right] \\ &= V_{ph} \left( \sqrt{\left(\frac{3}{2}\right)^2 + \frac{3}{4}} \right) \angle \tan^{-1} \left( \frac{\frac{\sqrt{3}}{2}}{\frac{3}{2}} \right) = V_{ph}(\sqrt{3}) \angle \tan^{-1} \left( \frac{1}{\sqrt{3}} \right) = \sqrt{3}V_{ph} \angle 30^\circ \\ V_{AB} &= \sqrt{3}V_{ph} \angle 30^\circ \end{aligned} \quad \dots(9)$$

In the same way it can be shown that the line-to-line voltages ( $V_{AB}$ ,  $V_{BC}$  and  $V_{CA}$ ) forms a three phase of voltages system; related to the phase voltages by the following:

- $\sqrt{3}$  amplitude ratio:  $|V_{LL}| = \sqrt{3}|V_{LN}|$
- 30° phase shift:
  - For positive sequence systems, the line-to-line voltages lead the phase voltages by 30°.
  - For negative sequence systems, the line-to-line voltages lags the phase voltages by 30°.

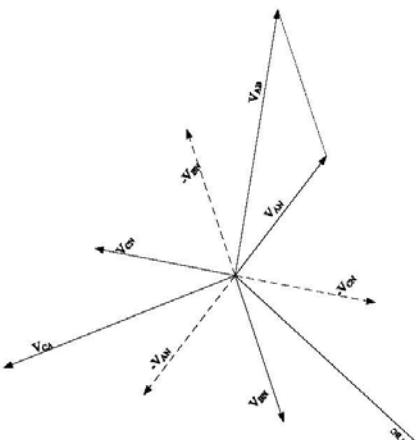


Fig. 6

## 2. The balanced three-phase system

In this section we will consider a three phase circuit analysis. The balanced system has a three identical parts connected to the terminals of the three phase supply. In the circuit shown in Fig. 7. The phase circuit is composed of the supply and a load impedance denoted by  $Z_p$ . The common point of the three load impedances (N) is also connected to the supply neutral point (n). This configuration is called Y-Y 4-wire system. Let's determine the current  $I_{Nn}$ :

$$I_{Nn} = I_A + I_B + I_C = \frac{V_{an}}{Z_p} + \frac{V_{bn}}{Z_p} + \frac{V_{cn}}{Z_p} = \frac{0}{Z_p} = 0$$

From the above, it is shown that the neutral line current is zero (in balanced systems) and therefore if we remove the wire connecting N-to-n, it will have no effect on the circuit operation, i.e. the points "n" and "N" will still have the same voltage and we can say that  $V_{AN}=V_{an}$ .

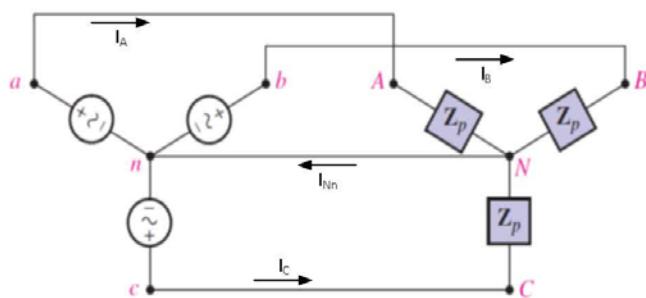


Fig. 7

**Example 1:** For the circuit of Fig. 8, find both the phase and line currents, and the phase and line voltages throughout the circuit; then calculate the total power dissipated in the load.

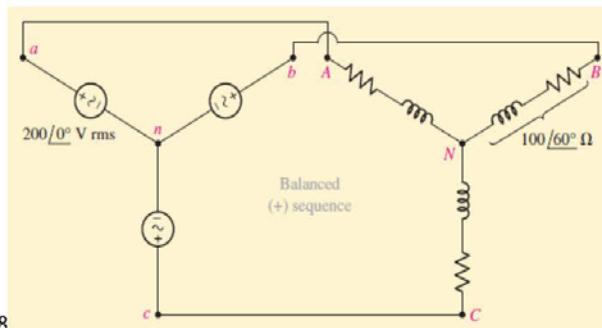


Fig. 8

Sol.

*The phase voltages:*

$$V_{AN} = V_{an} = 200\angle 0^\circ \text{ V}; V_{BN} = V_{bn} = 200\angle -120^\circ \text{ V}; V_{CN} = V_{cn} = 200\angle 120^\circ \text{ V}$$

*The line Voltages:*

$$V_{AB} = \sqrt{3}V_{an}\angle 30^\circ = 346.4\angle 30^\circ \text{ V}; V_{BC} = 346.4\angle -90^\circ \text{ V}; V_{CA} = 346.4\angle 150^\circ \text{ V}$$

*The phase (and line) currents*

$$I_A = \frac{200\angle 0}{100\angle 60} = 2\angle -60^\circ \text{ A};$$

$$I_B = 2\angle (-60 - 120) = 2\angle 180^\circ \text{ A}$$

$$I_C = 2\angle (-60 + 120) = 2\angle 60^\circ \text{ A}$$

From Example 1, it is shown that symmetry between the phases can be utilized to extend the analysis of one phase to the other phases simply by shifting the phase angle. For more complex circuits the technique of "single-line diagram" is normally employed as shown in Example 2.

Before the example recall the Y-Δ conversion techniques used in circuit simplification. If we have equal impedances; the conversion becomes as follows:

$$Z_Y = \frac{Z_\Delta}{3} \quad \dots(9)$$

**Example 2:** Determine  $I_{aA}$  and  $v_{Bn}$  for the circuit in Fig. 9

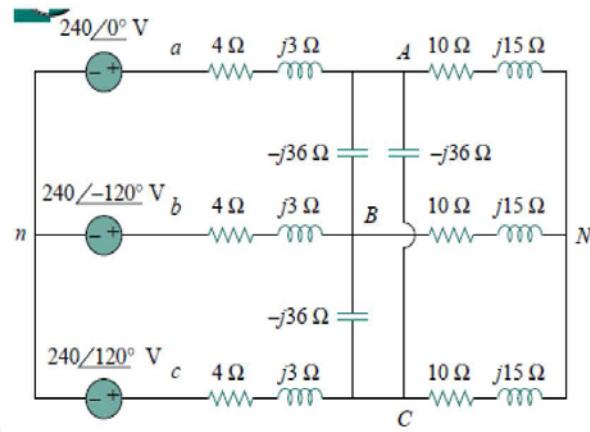


Fig. 9


// notice that the  $\Delta$ -connected element cannot be used in the single line diagram; (SLD) as the this diagram shows the connection to neutral;

Therefore, B4 drawing the SLD, we replace the  $\Delta$ -connected elements by the Y-equivalents//

- 1- We replace the  $\Delta$ -connected capacitor load by its Y-equivalent. The per-phase equivalent impedance:

$$Z_Y = -\frac{j36}{3} = -j12$$

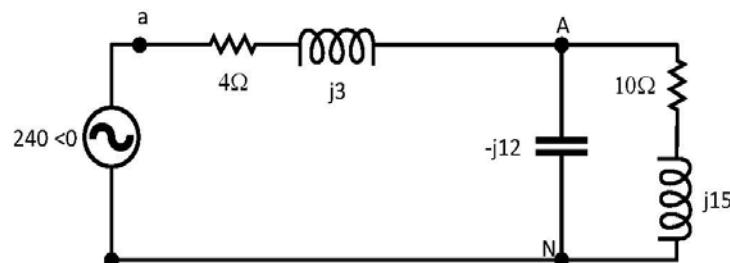- 2- We draw the per-phase equivalent circuit to determine,  $i_{aA}$  :



$$Z_{eq} = 4 + j3 + (-j12 \parallel (10 + j15))$$

$$Z_{eq} = 4 + j3 + \frac{180 - j120}{10 + j3} = 4 + j3 + \frac{216.33\angle -33.69^\circ}{10.44\angle 16.7^\circ}$$

$$Z_{eq} = 4 + j3 + 20.72\angle -50.4^\circ = 4 + j3 + 13.2 - j15.97$$

$$Z_{eq} = 17.2 - j12.97 = 21.54\angle -37^\circ$$

$$I_{aA} = \frac{240\angle 0}{21.54\angle -37} = 11.142\angle 37 A$$

To determine  $v_{Bn}$ , we determine,  $v_{An}$

$$v_{An} = 240\angle 0 - 11.142\angle 37 * (4 + j3)$$

$$v_{An} = 240\angle 0 - 55.71\angle 73.87 = 224.5 - j53.52$$

$$v_{An} = 230.8\angle -13.4^\circ A$$

$$v_{Bn} = v_{An}\angle -120 = 230.8\angle -133.4^\circ$$

### 3- The Δ-connection

#### Phase and line quantitates for Y-connected element:

The relationship between the phase and line voltage of a Y-connected supply is derived [Eq. (9)] and defined in the past section. This relationship is re-stated and extended to Y-connected in Table 1 (Reference Table 12.1 textbook).

#### Phase and line quantitates for Δ-connected element:

The source may also be connected in Δ configuration, as shown in Fig. 10.

// The Δ-connection of the supply is not so common because any unbalance in the supply causes a considerable amount of “circulating current” in the Δ-circuit and causes losses; however unbalanced systems are beyond our field of study//

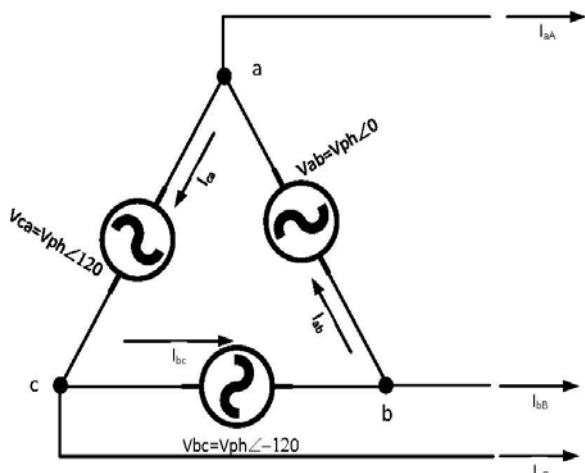


Fig. 10

In Δ-connected source the line voltages are equal to the phase voltages; while the amplitudes of phase currents ( $I_{ab}$ ,  $I_{bc}$  and  $I_{ca}$  in Fig. 10) and the line current ( $|I_{aa}|$ ,  $|I_{bb}|$  and  $|I_{cc}|$ ) are related by:

$$|I_{LL}| = \sqrt{3} |I_{ph}| \quad \dots(10)$$

The line current lags the phase currents by  $30^\circ$  for positive sequence systems as indicated in table 1. In Fig. 10, the line and phase current are related by:

$$I_{aa} = I_{ab} - I_{ca}; I_{bb} = I_{bc} - I_{ab}; I_{cc} = I_{ca} - I_{bc};$$

Table 1

Load	Phase Voltage	Line Voltage	Phase Current	Line Current	Power per Phase
Y	$V_{AN} = V_p \angle 0^\circ$ $V_{BN} = V_p \angle -120^\circ$ $V_{CN} = V_p \angle -240^\circ$	$V_{AB} = V_{ab}$ $= (\sqrt{3}/30^\circ) V_{AN}$ $= \sqrt{3} V_p \angle 30^\circ$  $V_{BC} = V_{bc}$ $= (\sqrt{3}/30^\circ) V_{BN}$ $= \sqrt{3} V_p \angle -90^\circ$  $V_{CA} = V_{ca}$ $= (\sqrt{3}/30^\circ) V_{CN}$ $= \sqrt{3} V_p \angle -210^\circ$	$I_{aA} = I_{AN} = \frac{V_{AN}}{Z_p}$ $I_{bB} = I_{BN} = \frac{V_{BN}}{Z_p}$ $I_{cC} = I_{CN} = \frac{V_{CN}}{Z_p}$	$I_{aA} = I_{AN} = \frac{V_{AN}}{Z_p}$ $I_{bB} = I_{BN} = \frac{V_{BN}}{Z_p}$ $I_{cC} = I_{CN} = \frac{V_{CN}}{Z_p}$	$\sqrt{3} V_L I_L \cos \theta$ where $\cos \theta =$ power factor of the load
$\Delta$	$V_{AB} = V_{ab}$ $= \sqrt{3} V_p \angle 30^\circ$  $V_{BC} = V_{bc}$ $= \sqrt{3} V_p \angle -90^\circ$  $V_{CA} = V_{ca}$ $= \sqrt{3} V_p \angle -210^\circ$	$V_{AB} = V_{ab}$ $= \sqrt{3} V_p \angle 30^\circ$  $V_{BC} = V_{bc}$ $= \sqrt{3} V_p \angle -90^\circ$  $V_{CA} = V_{ca}$ $= \sqrt{3} V_p \angle -210^\circ$	$I_{AB} = \frac{V_{AB}}{Z_p}$ $I_{BC} = \frac{V_{BC}}{Z_p}$ $I_{CA} = \frac{V_{CA}}{Z_p}$	$I_{aA} = (\sqrt{3} \angle -30^\circ) \frac{V_{AB}}{Z_p}$ $I_{bB} = (\sqrt{3} \angle -30^\circ) \frac{V_{BC}}{Z_p}$ $I_{cC} = (\sqrt{3} \angle -30^\circ) \frac{V_{CA}}{Z_p}$	$\sqrt{3} V_L I_L \cos \theta$ where $\cos \theta =$ power factor of the load

### Example 3


A negative-sequence balanced three-phase Y-connected source supplies power to a balanced, three-phase  $\Delta$ -connected load with an impedance of  $12 + j9 \Omega/\text{phase}$ . The source voltage in the b-phase is  $240 \angle -50^\circ \text{ V}$ . The line impedance is  $1 + j1 \Omega/\text{phase}$ . Draw the single phase equivalent circuit for the a-phase and use it to find the current in the a-phase of the load.

Sol.

$$Z_\Delta = \frac{Z_Y}{3} = 4 + j3\Omega$$

For negative-sequence supply  $v_{bn} = av_{an}$
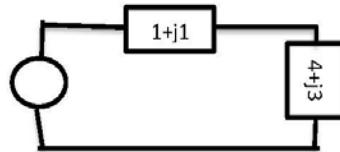
$$v_{an} = \frac{v_{bn}}{a} = 240 \angle -50^\circ - 120 = 240 \angle -170^\circ$$



$$I_{aA} = \frac{240 \angle -170^\circ}{(1 + j1) + (4 + j3)} = 37.48 \angle 151.34^\circ$$

$$I_{AB} = \frac{37.48 \angle 151.34^\circ}{\sqrt{3}} \angle -30^\circ = 21.64 \angle -121.34^\circ A$$

### Related Book Problems 15-35



## Lectures of Electrical Engineering Department

**S**ubject Title: Electrical Networks

**C**lass: 2<sup>nd</sup> Stage

Lecture Contents	Lecture sequences:	8 <sup>nd</sup> lecture	Instructor Name: Omer Sharaf Aldeen Ali Abbawi
	<b>The major contents:</b>	<b>Analysis and Power Calculation of Three-Phase Circuits</b>	
	<b>The detailed contents:</b>	<b>1- Analysis of three-phase circuits with Y-connected supply</b> <b>2- Analysis of systems with Delta-connected supply</b> <b>3- Power Calculations in Three-Phase Systems</b>	

### Chapter 3

#### Analysis and Power Calculation of Three-Phase Circuits

This lecture presents the analysis of balanced three-phase circuits using single line diagram. A special emphasis is given for the  $\Delta$ -connected supply. Power calculation in three-phase circuits in terms of phase and line quantities is also presented.

##### a. Analysis of three-phase circuits with Y-connected supply.

We have shown in the first lecture that the three-phase system can be seen as similar single phase systems (except the  $120^\circ$ -phase shift). We can use this symmetry to simplify the analysis using the single line diagram approach providing that we have neutral points at the supply and load. In this section we will consider Y-connected supply. We can provide an imaginary neutral point for the  $\Delta$ -connected load using  $\Delta$ -Y transformation. For equal impedances.

$$Z_Y = \frac{Z_\Delta}{3} \quad \dots(1)$$

**Example 2:** Determine  $I_{aA}$  and  $v_{Bn}$  for the circuit in Fig. 1

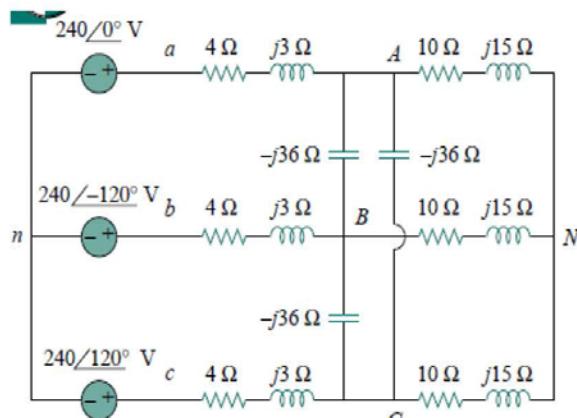


Fig. 1


// notice that the  $\Delta$ -connected element cannot be used in the single line diagram; (SLD) as the this diagram shows the connection to neutral;

Therefore, B4 drawing the SLD, we replace the  $\Delta$ -connected elements by the Y-equivalents//

- 1- We replace the  $\Delta$ -connected capacitor load by its Y-equivalent. The per-phase equivalent impedance:

$$Z_Y = -\frac{j36}{3} = -j12$$

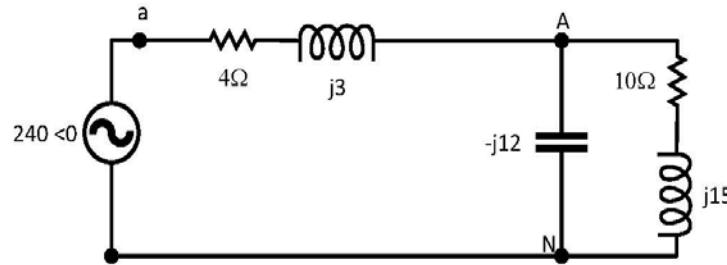- 2- We draw the per-phase equivalent circuit to determine,  $i_{aA}$  :



$$Z_{eq} = 4 + j3 + (-j12) \parallel (10 + j15)$$

$$Z_{eq} = 4 + j3 + \frac{180 - j120}{10 + j3} = 4 + j3 + \frac{216.33\angle -33.69^\circ}{10.44\angle 16.7^\circ}$$

$$Z_{eq} = 4 + j3 + 20.72\angle -50.4^\circ = 4 + j3 + 13.2 - j15.97$$

$$Z_{eq} = 17.2 - j12.97 = 21.54\angle -37^\circ$$

$$I_{aA} = \frac{240\angle 0}{21.54\angle -37} = 11.142\angle 37^\circ A$$

To determine  $v_{Bn}$ , we determine,  $v_{An}$

$$v_{An} = 240\angle 0 - 11.142\angle 37 * (4 + j3)$$

$$v_{An} = 240\angle 0 - 55.71\angle 73.87 = 224.5 - j53.52$$

$$v_{An} = 230.8\angle -13.4^\circ A$$

$$v_{Bn} = v_{An}\angle -120 = 230.8\angle -133.4^\circ$$

Table 1 presents the phase and line quantities for Y- and Δ-connected elements. This relationship has been defined earlier for Y-connected loads.

Table 1

Load	Phase Voltage	Line Voltage	Phase Current	Line Current	Power per Phase
Y	$V_{AN} = V_p/0^\circ$	$V_{AB} = V_{ab} = (\sqrt{3}/30^\circ)V_{AN} = \sqrt{3}V_p/30^\circ$	$I_{aA} = I_{AN} = \frac{V_{AN}}{Z_p}$	$I_{aA} = I_{AN} = \frac{V_{AN}}{Z_p}$	$\sqrt{3}V_L I_L \cos \theta$ where $\cos \theta$ = power factor of the load
	$V_{BN} = V_p/-120^\circ$	$V_{BC} = V_{bc} = (\sqrt{3}/30^\circ)V_{BN} = \sqrt{3}V_p/-90^\circ$	$I_{bB} = I_{BN} = \frac{V_{BN}}{Z_p}$	$I_{bB} = I_{BN} = \frac{V_{BN}}{Z_p}$	
	$V_{CN} = V_p/-240^\circ$	$V_{CA} = V_{ca} = (\sqrt{3}/30^\circ)V_{CN} = \sqrt{3}V_p/-210^\circ$	$I_{cC} = I_{CN} = \frac{V_{CN}}{Z_p}$	$I_{cC} = I_{CN} = \frac{V_{CN}}{Z_p}$	
Δ	$V_{AB} = V_{ab} = \sqrt{3}V_p/30^\circ$	$V_{AB} = V_{ab} = \sqrt{3}V_p/30^\circ$	$I_{AB} = \frac{V_{AB}}{Z_p}$	$I_{aA} = (\sqrt{3}/-30^\circ)\frac{V_{AB}}{Z_p}$	$\sqrt{3}V_L I_L \cos \theta$ where $\cos \theta$ = power factor of the load
	$V_{BC} = V_{bc} = \sqrt{3}V_p/-90^\circ$	$V_{BC} = V_{bc} = \sqrt{3}V_p/-90^\circ$	$I_{BC} = \frac{V_{BC}}{Z_p}$	$I_{bB} = (\sqrt{3}/-30^\circ)\frac{V_{BC}}{Z_p}$	
	$V_{CA} = V_{ca} = \sqrt{3}V_p/-210^\circ$	$V_{CA} = V_{ca} = \sqrt{3}V_p/-210^\circ$	$I_{CA} = \frac{V_{CA}}{Z_p}$	$I_{cC} = (\sqrt{3}/-30^\circ)\frac{V_{CA}}{Z_p}$	

For  $\Delta$ -connection: (1) Line voltage=Phase voltage and (2) Line current = $\sqrt{3}$  phase current with ( $-30^\circ/+30^\circ$ ) phase shift for (positive sequence/negative sequence systems).

### b. Analysis of systems with $\Delta$ -connected supply

The source may also be connected in  $\Delta$  configuration, as shown in Fig. 2.

// The  $\Delta$ -connection of the supply is not so common because any unbalance in the supply causes a considerable amount of "circulating current" in the  $\Delta$ -circuit and causes losses; however unbalanced systems are beyond our field of study//

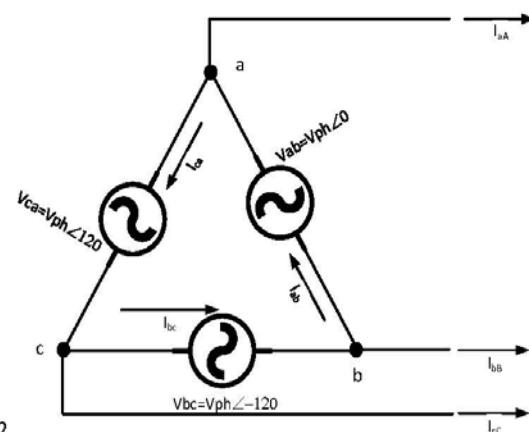


Fig. 2

In  $\Delta$ -connected source the line voltages are equal to the phase voltages; while the amplitudes of phase currents ( $I_{ab}$ ,  $I_{bc}$  and  $I_{ca}$  in Fig. 10) and the line current ( $|I_{aa}$ ,  $|I_{bb}$  and  $|I_{cc}$ ) are related by:

$$|I_{LL}| = \sqrt{3} |I_{ph}| \quad \dots(10)$$

The line current lags the phase currents by  $30^\circ$  for positive sequence systems as indicated in table 1. In Fig. 2, the line and phase current are related by:

$$I_{aa} = I_{ab} - I_{ca}; I_{bb} = I_{bc} - I_{ab}; I_{cc} = I_{ca} - I_{bc};$$

The verification of the line- and phase- currents relationships s shown in Fig.3 using the phasor diagram.

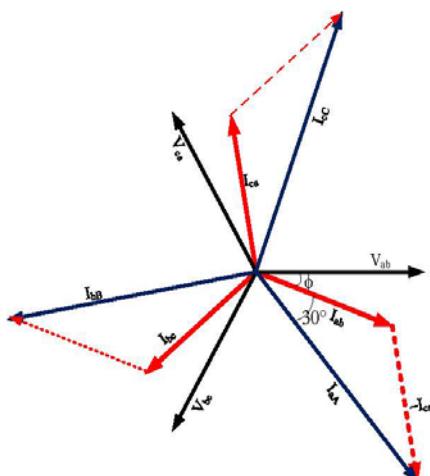


Fig.3

**Example 2**

A negative-sequence balanced three-phase source supplies power to a balanced, three-phase load with an impedance of  $12 + j9 \Omega/\text{phase}$ . The source voltage in the b-phase is  $240\angle-50^\circ \text{ V}$ . The line impedance is  $1 + j1 \Omega/\text{phase}$ . Draw the single phase equivalent circuit for the a-phase and use it to find the current in line current ( $I_{aA}$ ) for each of the following combinations:


- Y-connected source and Y-connected load
- Y-connected source and  $\Delta$ -connected load
- $\Delta$ -connected source and Y-connected load
- $\Delta$ -connected source and  $\Delta$ -connected load.

Sol.

For negative-sequence supply  $v_{bn} = av_{an}$

$$v_{an} = \frac{v_{bn}}{a} = 240\angle -50^\circ - 120 = 240\angle -170^\circ = 240\angle 190^\circ$$

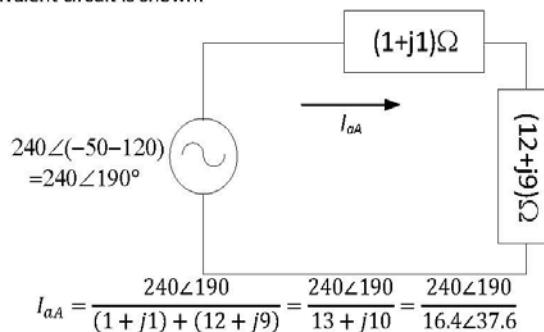a. The per-phase equivalent circuit is shown:




$$I_{aA} = \frac{240\angle 190}{(1 + j1) + (12 + j9)} = \frac{240\angle 190}{13 + j10} = \frac{240\angle 190}{16.4\angle 37.6}$$

$$I_{aA} = 14.6\angle 152.4^\circ \text{ A}$$

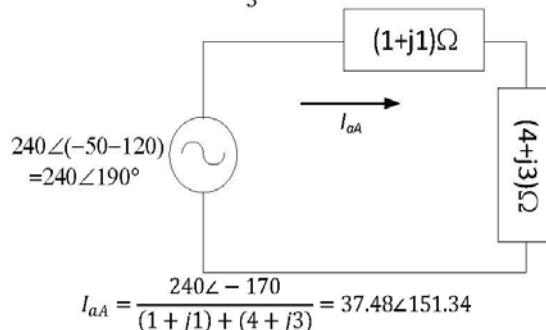b. By constructing the SLD we convert the load to its Y-equivalent


$$Z_Y = \frac{Z_\Delta}{3} = 4 + j3\Omega$$



$$I_{aA} = \frac{240\angle -170}{(1 + j1) + (4 + j3)} = 37.48\angle 151.34$$

c. The per-phase equivalent of a line voltage is determined by:

$$|V_{ph}| = \frac{|V_L|}{\sqrt{3}}; \quad \angle V_{ph} = \angle(V_L + 30^\circ) \text{ for negative sequence voltages. The SLD is as shown:}$$

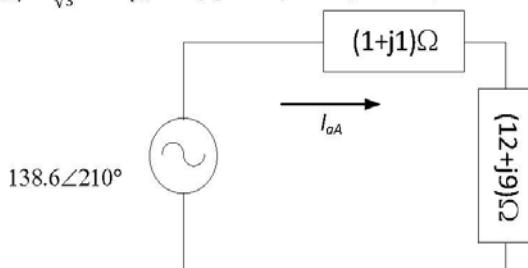


$$I_{aA} = \frac{138.6 \angle 210}{16.4 \angle 37.6}$$

$$I_{aA} = 8.45 \angle 172.4^\circ A$$

// what is the supply phase current  $I_{ab}$  ??

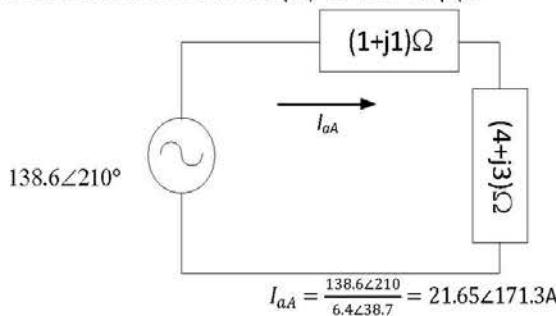d. //We connect the source of (c) to load of (b)//



// A great deal of simplification is achieved by the SLD approach. In order to appreciate this, try to analyze the circuit using the basic circuit methods; my attempt is shown below:

Handwritten notes show the following calculations:

$$Z_1 = \frac{138.6 \angle 210}{(1+j1)(j3+4)} = 21.65 \angle 171.3 A$$

$$Z_2 = \frac{(1+j1)(j3+4)}{(1+j1)(j3+4)} = 1 A$$

$$Z_3 = \frac{(1+j1)(j3+4)}{(1+j1)(j3+4)} = 1 A$$

$$I_A = 21.65 \angle 171.3 A$$

$$I_B = -7.16 \angle 178.46 A$$

$$I_C = 21.65 \angle 61.74 A$$

#### Related Book Problems 15-35

## c. Power Calculations in Three-Phase Systems

Note : ALL Voltages and Current indicated in the following material is in RMS which is equivalent (for sine wave to the peak  $(\sqrt{2})$ ; unless indicated otherwise).

The power associated to any element in the three-phase circuit (source, line or load) can be calculated using the SLD which represents one phase (or more precisely one phase of the Y-Y connected equivalent circuit). As the three-phase system power is  $3 \times$  (the power in the SLD). And since the quantities shown the in SLD are the per-phase quantities:

$$S_{3\phi} = 3 \times S_{1\phi} = 3 \times [V_{ph} I_{ph}]$$

Similarly:

$$P_{3\phi} = 3 \times [V_{ph} I_{ph} \cos \phi]; \text{ and}$$

$$Q_{3\phi} = 3 \times [V_{ph} I_{ph} \sin \phi]$$


Recall that :

For Y-connection	For Δ-connection
$V_L = \sqrt{3} V_{ph}$ and $I_L = I_{ph}$	$V_L = V_{ph}$ and $I_L = \sqrt{3} I_{ph}$
For any connection :	
$S_{3\phi} = \sqrt{3} \times [V_L I_L]$	
$P_{3\phi} = \sqrt{3} \times [V_L I_L \cos \phi]$	
$Q_{3\phi} = \sqrt{3} \times [V_L I_L \sin \phi]$	

The three above equations are specially important when we have no information about the load and source and determining the power by line voltage and current information (or measurements).

**Example3:** The frequency of the supply in the circuit shown in below is 60Hz. Find for the three-phase system:

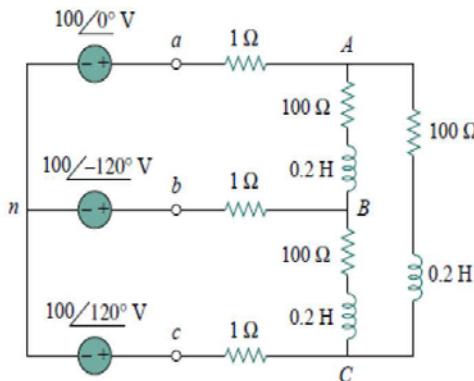- a) The load power, P.
- b) The power dissipated in the line resistor
- c) The supply apparent, average and reactive power
- d) The capacitance of a three delta connected capacitors to be introduced at the load side (points A,B, and C) to make the source power factor =1.



Sol.

-determine the inductive reactance:


$$XL = 2\pi fL = 24\pi = 75.4$$

-determine the Y-equivalent impedance of the load

$$Z_Y = \frac{100 + j75.4}{3} = (33.3 + j25.13)\Omega$$

From the SLD:
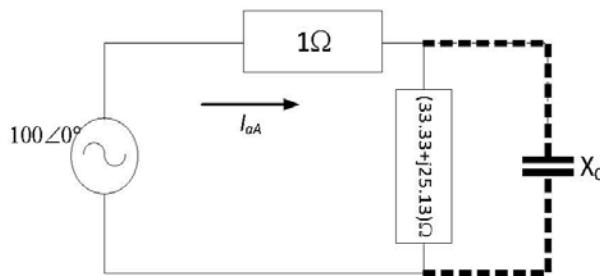
$$I_{AA} = \frac{100\angle 0}{1 + (33.3 + j25.13)} = 1.8966 - j1.388 A = 2.35\angle -36.2^\circ A$$



- a) Now the load power can be determined using more than one method, as shown:

$$\text{First method: } P_{\text{Load}} = 3(I_{\text{ph}})^2 R = 3(|1.8966 - j1.388|^2 33.33) = 552.4W$$

$$\text{Second Method: } P_{\text{Load}} = 3V_{\text{ph}}I_{\text{ph}} \cos \phi = 3(I_{\text{ph}}Z_L)I_{\text{ph}} \cos \phi$$

$$P_{\text{Load}} = 3(1.8966 - j1.388)^2 (33.3 + j25.13) \cos \tan^{-1} \left( \frac{25.13}{33.33} \right)$$

$$P_{\text{Load}} = 552.4W$$

//obviously the first method is simpler//

b)  $P_{TL} = 3 * ((2.35^2) * 1) = 16.572W$

c)  $S_{\text{Supply}} = 3V_{\text{ph}}I_{\text{ph}} = 3 * 100 * 2.35 = 705VA$

$$P_{\text{Supply}} = 3V_{\text{ph}}I_{\text{ph}} \cos \phi = 705 \cos 36.2 = 568.9W$$

$$Q_{\text{Supply}} = 3V_{\text{ph}}I_{\text{ph}} \sin \phi = 705 \sin 36.2 = 416.38VAR$$

- d) First determine the capacitive reactance that appears in the SLD  $X_C$

-Since the supply power factor is 1; the equivalent imedance seen by the supply has imajinary component impedance =0.

$$\begin{aligned} \text{Im}[1 + Z_{LC}] &= \text{Im}[Z_{LC}] = 0 \\ \text{Im}\left[\frac{(33.33 + j25.13) \times (-jX_C)}{(33.33 + jX)}\right] &= 0 \end{aligned}$$

Where  $jX=j(25.13-X_C)$

$$\begin{aligned} \text{Im}\left[\frac{(33.33 + j25.13) \times (-jX_C)}{(33.33 + jX)}\right] &= 0 \\ \text{Im}[(25.13X_C - j33.33X_C) \times (33.33 - jX)] &= 0 \end{aligned}$$

$$[(-25.13XX_C - 33.33^2X_C)] = 0$$

$$X = -\frac{33.33^2}{25.13} = -44.2$$

$$X_C = -44.2 - 25.13 = -69.33\Omega$$

As  $X_C$  is the Y equivalent of the actual Δ connected capacitors; we find the actual capacitive reactance:

$$Z_\Delta = 3Z_Y$$

$$X_{C\Delta} = 3(-j69.33) = -j208\Omega$$

$$C = \frac{1}{120\pi * 208} = 12.75\mu F$$











## Lectures of Electrical Engineering Department

**S**ubject Title: Electrical Networks

**C**lass: 2<sup>nd</sup> Stage

Lecture Contents	Lecture sequences:	9 <sup>nd</sup> lecture	Instructor Name: Omer Sharaf Aldeen Ali Abbawi
	<b>The major contents:</b>	<b>Power Measurements in Three-Phase Circuits</b>	
	<b>The detailed contents:</b>	<b>1- The wattmeter</b> <b>2- Power measurements in three phase systems</b> <b>3- The two wattemeter method</b>	

## Chapter 3

### Power Measurements in Three-Phase Circuits

The wattmeter is the basic power measurement instrument. In practical three-phase system it is required to consider unbalance. The famous power measurement method that uses two wattmeter and valid for balanced and unbalanced systems is presented in this lecture.

#### a. The wattmeter

In AC circuits, power measurement is accomplished through the use of a wattmeter that contains two separate coils. One of these coils is the current coil; the second coil is the potential (or voltage) coil. The value indicated by the wattmeter indicates the product of the current through its current coil and the voltage across its voltage coil. Fig. 1 shows the schematic diagram of the wattmeter.

In our discussion we will assume that the current coil has zero impedance and the voltage coil has infinite impedance.

In Fig. 1, one side of each coil is marked by (+); this indicates that the wattmeter is a polarity-sensitive device. If a positive current is entering that (+) side of the current coil and the voltage of the (+) side of the voltage coil is (+) with respect to the other side then the power is positive, or being transferred to the load side. Note the following:

- The wattmeter measures the average power ( $P$ ). (Not the instantaneous power).
- Reversing the connection of one coil reverses the polarity of the power being measured. While revering both coils does not change the power polarity.

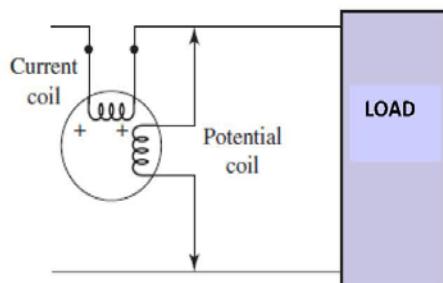


Fig.1

#### b. Power measurements in three phase systems.

To measure the power drawn by a three-phase load we will discuss the straightforward method first. We place one wattmeter in each of the three phases and add the results. The connections for a Y- and  $\Delta$ -connected loads are shown in Fig.2.

The method is theoretically correct but **not practical**. One main reason is because the three phase loads have only three lines contacts and other **contacts are not accessible**.

The connection shown in fig. 3 uses the line currents and it establishes a common point ( $x$ ) as a common voltage coil side for the three wattmeters. There are two possibilities:

- Either the system is balanced (the supply voltages and the load are balanced). In this case the point  $x$  has the same potential as the neutral and the voltage of each voltage coil is the phase voltage. The power indicated by the three wattmeters is equal.

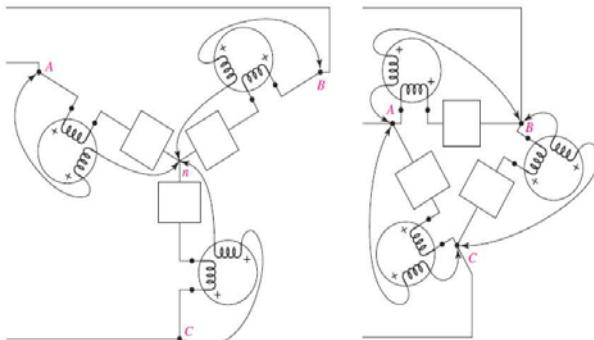


Fig. 2

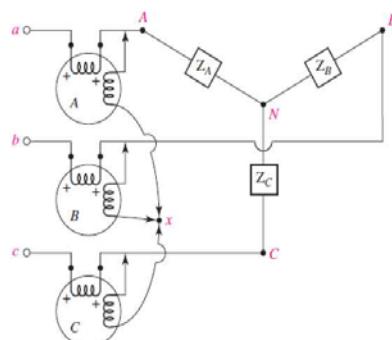


Fig. 3

- or there is an unbalance that makes a voltage difference between points (N and x). In this case the power measured:

$$P = P_A + P_B + P_C = \frac{1}{T} \int_0^T (v_{Ax} i_{aA} + v_{Bx} i_{bB} + v_{Cx} i_{cC}) dt$$

The three voltages "seen" by the wattmeters are:

$$\begin{aligned} v_{A,x} &= v_{A,N} + V_{Nx} \\ v_{B,x} &= v_{B,N} + V_{Nx} \\ v_{C,x} &= v_{C,N} + V_{Nx} \end{aligned}$$

Substitutes to determine P

$$P = \frac{1}{T} \int_0^T (v_{AN} i_{aA} + v_{BN} i_{bB} + v_{CN} i_{cC}) dt + \frac{1}{T} \int_0^T v_{Nx} (i_{aA} + i_{bB} + i_{cC}) dt$$

Since this three-phase load has only three wires:

$$i_{aA} + i_{bB} + i_{cC} = 0$$

And

$$P = \frac{1}{T} \int_0^T (v_{AN} i_{aA} + v_{BN} i_{bB} + v_{CN} i_{cC}) dt = P_{3\emptyset}$$

#### Example 1:

A three-phase supply has a positive sequence and a line voltage of 100V. The load is unbalanced impedances which are  $\Delta$ -connected. The three impedances are as follows:

$$Z_{AB} = -j10\Omega; Z_{BC} = j10\Omega; \text{ and } Z_{CA} = 10\Omega$$

Determine the average power dissipated by the load and the measurement of the three wattmeters which are connected as shown in Fig. 3, to show that the wattmeters measure the load in the unbalanced load.

Sol.

$$V_{AB} = 100\angle 0^\circ;$$

$$V_{BC} = 100\angle -120^\circ \text{ and}$$

$$V_{CA} = 100\angle 120^\circ.$$

$$I_{AB} = \frac{100\angle 0^\circ}{10\angle -90^\circ} = 10\angle 90^\circ;$$

$$I_{BC} = \frac{100\angle -120^\circ}{10\angle 90^\circ} = 10\angle -210^\circ;$$

$$I_{CA} = \frac{100\angle -240^\circ}{10\angle 0^\circ} = 10\angle -240^\circ.$$

The average power dissipated in the load is the resistive part power ( $Z_C$ ) only and it equals:

$$P = |I_{CA}|^2 R_C = 1000W$$

The line currents:

$$I_{aA} = I_{AB} - I_{CA} = 10\angle 90^\circ - 10\angle -240^\circ = 5.1764\angle 15^\circ$$

$$I_{bB} = I_{BC} - I_{AB} = 10\angle -210^\circ - 10\angle 90^\circ = 10\angle -150^\circ$$

$$I_{cC} = I_{CA} - I_{BC} = 10\angle -240^\circ - 10\angle -210^\circ = 5.1764\angle 45^\circ$$

Now determine the equivalent phase voltages

$$V_{AN} = \frac{100}{\sqrt{3}}\angle -30^\circ$$

$$V_{BN} = \frac{100}{\sqrt{3}}\angle -150^\circ$$

$$V_{CN} = \frac{100}{\sqrt{3}}\angle 90^\circ$$

The three measured powers:

$$P_A = 5.1764 \times \frac{100}{\sqrt{3}} \cos(-30 - 15) = 211.5W$$

$$P_B = 10 \times \frac{100}{\sqrt{3}} \cos(-150 - (-150)) = 577W$$

$$P_C = 5.1764 \times \frac{100}{\sqrt{3}} \cos(90 - 45) = 211.5W$$

$$\therefore P_{3\phi} = P_A + P_B + P_C$$

The example shows that the sum of the three wattmeters powers is equivalent to the actual power dissipated in this unbalanced load.

c. The two wattmeter method.

It is shown that point x, in Fig. 3; could be at any voltage and the three wattmeters will still measure the three phase power for balanced or unbalanced system. If we place point x at any one of the three lines (say line B as shown in Fig. 4), the wattmeter at that line sees zero voltage and measures zero power. Therefore, this wattmeter is removed and the remaining two wattmeters measure the voltage of the balanced or unbalanced three-phase load.

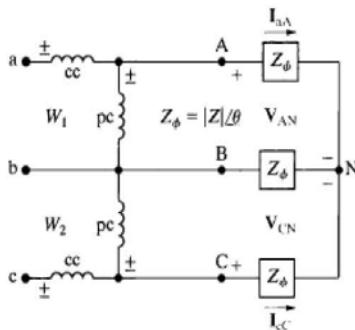


Fig. 4

In balanced systems let's look at the two wattmeter measurements,  $W_1$  and  $W_2$  according to Fig. 4

$$P_1 = |V_{AB}| |I_{aA}| \cos \theta_1 = V_L I_L \cos \theta_1$$

$$P_2 = |V_{CB}| |I_{cC}| \cos \theta_2 = V_L I_L \cos \theta_2$$

The load impedance:  $Z_\phi = |Z_\phi| \angle \theta_\phi$ ; from the phasor diagram in Fig. 5:

$$\theta_1 = \theta_\phi + 30^\circ$$

And

$$\theta_2 = \theta_\phi - 30^\circ$$

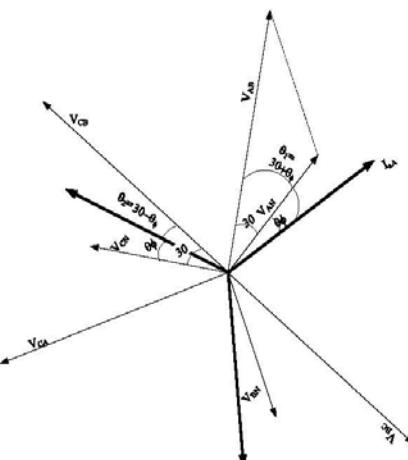


Fig. 5

Now consider the sum of the two measures:

$$P_1 + P_2 = V_L I_L (\cos(30 + \theta_\phi) + \cos(30 - \theta_\phi))$$

$$P_1 + P_2 = V_L I_L (\cos 30 \cos \theta_\phi - \sin 30 \sin \theta_\phi + \cos 30 \cos \theta_\phi + \sin 30 \sin \theta_\phi) \quad )$$

$$P_1 + P_2 = 2V_L I_L \cos 30 \cos \theta_\phi$$

$$P_1 + P_2 = \sqrt{3}V_L I_L \cos \theta_\phi = P_{3\phi}$$

Additionally we can obtain information about the phase angle and, hence, the power factor and reactive power as follows:

$$P_1 - P_2 = V_L I_L (\cos(30 + \theta_\phi) - \cos(30 - \theta_\phi))$$

$$P_1 - P_2 = V_L I_L (\sin \theta_\phi)$$

From the above, we can determine the impedance angle as:

$$\tan \theta_\phi = \frac{\sin \theta_\phi}{\cos \theta_\phi} = \sqrt{3} \frac{P_2 - P_1}{P_1 + P_2}$$

#### Example 2:

Refer to Fig.4; Calculate the reading of the two wattmeters and show that the sum of the two measures equals to the power delivered to the load if the load phase voltage is 120V and  $Z_\phi = 8 + j6\Omega$ . Determine also the impedance angle angle, the reactive power and the apparent power using the  $P_1$  and  $P_2$

Sol.

$$(a) Z_\phi = 10\angle 36.87^\circ, V_L = 120\sqrt{3}V \text{ and } I_L = \frac{120}{10} = 12A$$

$$P_1 = 120\sqrt{3} \times 12 \times \cos(36.87 + 30) = 979.75W$$

$$P_2 = 120\sqrt{3} \times 12 \times \cos(36.87 - 30) = 2476.25W$$

$$P_{3\phi} = 3I^2R = 3 \times 12^2 \times 8 = 3456W = P_1 + P_2$$

Also...

$$\tan \theta = \sqrt{3} \frac{P_2 - P_1}{P_2 + P_1} = \sqrt{3} \frac{(1496.5)}{3456} = 0.75$$

$$\theta = \tan^{-1}(0.75) = 36.87^\circ$$

$$\text{The reactive power, } Q = S \sin \theta = \frac{P}{\cos \theta} \sin \theta = P \tan \theta = 3456 * 0.75 = 2592VAR$$

$$\text{The apparent power, } S = \frac{P}{\cos \theta} = \frac{3456}{0.8} = 4320VA$$

**Practice: Repeat Example 2 for the following values of Z:**

- (a)  $Z_\phi = 8 - j6\Omega$ .
- (b)  $Z_\phi = 5 + j5\sqrt{3}\Omega$ .
- (c)  $Z_\phi = 10\angle -75^\circ$ .

Related book problems: form 15 to 44



# Lectures of Electrical Engineering Department

**S**ubject Title: Electrical Networks

**C**lass: 2<sup>nd</sup> Stage

Lecture Contents	Lecture sequences:	8 <sup>nd</sup> lecture	Instructor Name: Omer Sharaf Aldeen Ali Abbawi
	<b>The major contents:</b>	<b>Magnetically-Coupled Circuits</b>	
	<b>The detailed contents:</b>	<b>1 - Definition of Mutual Inductance</b> <b>2- Dot Convention</b> <b>3- Energy stored magnetically-coupled coils</b>	

## Chapter 4

### Magnetically-Coupled Circuits

The phenomenon described by mutual inductance is defined, and quantized. Circuits with magnetic coupling analysis is presented in this lecture. The energy stored in magnetically coupled coils is defined.

The following lectures present the most common device based on magnetic coupling: *the transformer*.

#### a. Definition of Mutual Inductance

Recall the inductance from its physical basis, refer to Fig.1

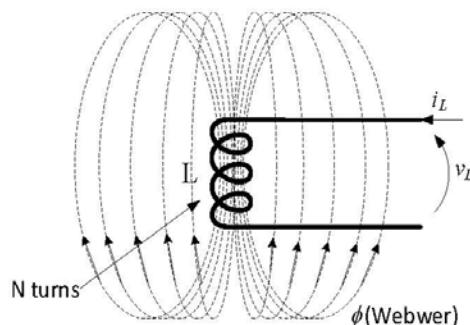


Fig. 1

Based of Amperes Law, the current carrying conductor (or coil) produces a magnetic flux proportional to the MMF (magneto-motive force) or the Ampere-turns.

$$\phi = \frac{Ni}{\mathfrak{R}} = \wp Ni$$

Where  $\mathfrak{R}$  and  $\wp$  represent the magnetic flux path reluctance and permanence respectively. This parameter is determined by the characteristics of magnetic flux path such as length, cross-section area and the medium permeability ( $\mu$ ).

According to Faraday's law, the voltage induced in a coil subjected to a time varying magnetic flux is given by:

$$v = \frac{d\lambda}{dt} = \frac{dN\phi}{dt} = \frac{dN \times \wp Ni}{dt} = \wp N^2 \frac{di}{dt}$$

Since:  $v = L \frac{di}{dt}$ , the circuit inductance can be related to the circuit magnetic characteristics by:  $L = \wp N^2$ .

Since  $L$  relates the voltage and current of the same coil, we will call it in this chapter "*the self-inductance*". In contrast, we will study the *mutual* inductance which (in a similar way) relates the voltage induced in one coil by the current of another coil.

Fig. 2 shows a current carrying coil with inductance  $L_1$  and there is another coil  $L_2$  within the magnetic field of  $L_1$ . The total flux of the coil  $L_1$  is denoted by  $\phi_1$ . This flux  $\phi_1$  is divided to two parts:

- $\phi_{21}$  is the part of  $\phi_1$  which is intersecting the windings of coil  $L_2$ , (both  $L_1$  and  $L_2$ ) and

- $\phi_{11}$  is the part of  $\phi_1$  which is intersecting the windings of coil  $L_1$  only.

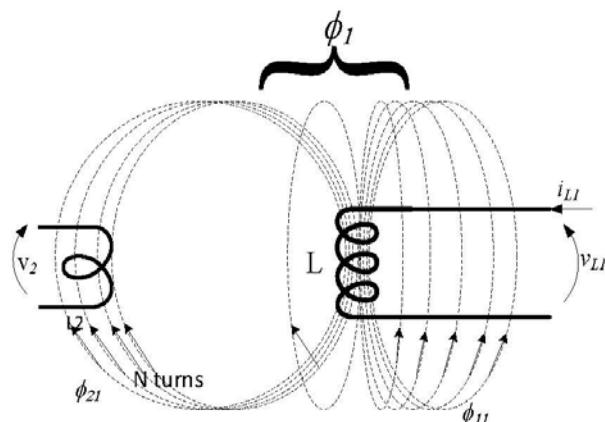


Fig. 2

Again apply Faraday's law for the two-coil case shown in Fig.2 (assuming a time-varying current)

$$v_1 = \frac{d\lambda_1}{dt} = \frac{dN_1\phi_1}{dt} = \mathcal{B}_1 N_1^2 \frac{di_1}{dt} = L_1 \frac{di_1}{dt}$$

And

$$\begin{aligned} v_2 &= \frac{d\lambda_2}{dt} = \frac{dN_2\phi_{21}}{dt} = N_2 \frac{d\phi_{21}\phi_{21}}{dt} \\ v_2 &= N_2 \frac{d\mathcal{B}_{21}N_1 i_1}{dt} = \mathcal{B}_{21} N_1 N_2 \frac{di_1}{dt} = M_{21} \frac{di_1}{dt} \end{aligned}$$

Where  $M_{21}$  is the inductance that relates the voltage induced in coil 2 to the current of coil 1.

Since  $M_{21}$  depends on: the permanence of the magnetic flux path between the two coils and the product of the number of turns of the two coils, it must be true that:

If  $v_1 = M_{12} \frac{di_2}{dt}$  then  $M_{12} = M_{21} \triangleq M$  the mutual inductance between the two coils.

#### Dot Convention

It is important to relate the polarity of the induced voltage to the direction of the current in magnetically coupled coils. For this purpose, the dot ( $\bullet$ ) marking has been introduced.

In dot convention a  $\bullet$  sign is placed at one end of each of the two coils which are mutually coupled. We determine the sign of the mutual voltage as follows:

If  $di/dt$  of current entering the dotted terminal of one coil is positive it produces a positive voltage at the dotted terminal with respect to the undotted terminal of second coil.

Thus, in Fig. 3.  $i_1$  enters the dotted terminal of  $L_1$ ,  $v_2$  is sensed positively at the dotted terminal of  $L_2$ , and  $v_2 = M di_1/dt$ . The voltage equations are also indicated in Fig. 3.

For AC circuits (sinusoidal supply) the two voltage equations can be expressed more easily in vector notation:

$$\begin{aligned}V_1 &= j\omega L_1 I_1 + j\omega M I_2 \\V_2 &= j\omega M I_1 + j\omega L_2 I_2\end{aligned}$$


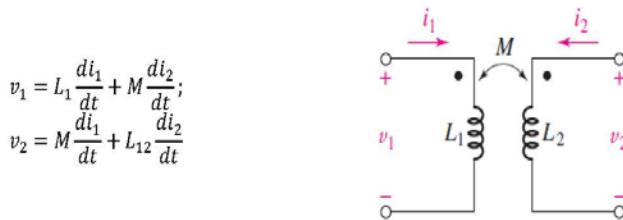


Fig. 3

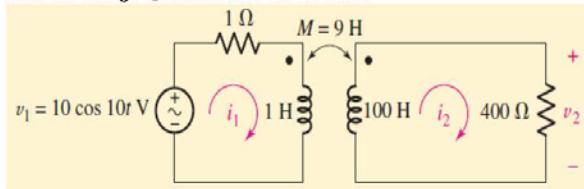**Example 1:** Determine the voltage  $v_2$  in the circuit shown below



Sol.

- // write the two loop equations to determine  $i_1$  and  $i_2$  //

$V_1 = I_1(1 + j10 * 1) - I_2(j10 * 9)$  //from loop 1; where  $w=10$  and the current  $I_2$  is leaving the dot therefore the second term has a negative sign//

$$0 = -I_1(j10 * 9) + I_2(400 + j10 * 100)$$

$$I_2 = \frac{I_1(j90)}{(400 + j1000)}$$

$$V_1 = I_1(1 + j10) - \frac{I_1(j90)}{400 + j1000}j90$$

$$V_1 = I_1 \left( 1 + j10 + \frac{8100}{400 + j1000} \right)$$

$$I_1 = \frac{V_1}{Z} = 2.063 \angle -38.5^\circ$$

$$I_2 = \frac{2.063 \angle -38.5^\circ * (j90)}{(400 + j1000)} = 0.1724 \angle -16.7^\circ$$

$$V_2 = 68.96 \angle -16.7^\circ$$

--Book Practice 13.2 and 13.3

#### The coupling coefficient: (Definition)

$$L_1 = N_1^2 \phi_1$$

$$L_2 = N_2^2 \phi_2$$

$$L_1 L_2 = N_1^2 N_2^2 \phi_1 \phi_2$$

$$L_1 L_2 = N_1^2 N_2^2 (\phi_{11} + \phi_{21})(\phi_{22} + \phi_{12})$$

Since:  $\phi_{12} = \phi_{21}$

$$L_1 L_2 = N_1^2 N_2^2 \phi_{12}^2 \left( \frac{\phi_{11}}{\phi_{12}} + 1 \right) \left( \frac{\phi_{22}}{\phi_{12}} + 1 \right)$$

$$L_1 L_2 = M^2 \left( \frac{\phi_{11}}{\phi_{21}} + 1 \right) \left( \frac{\phi_{22}}{\phi_{12}} + 1 \right)$$

$\phi_{11}$  and  $\phi_{22}$  will be zeros if the two coils are ideally tied magnetically in such a way that 100% of the flux of both coils is a mutual flux. In this case the **coupling coefficient ( $k$ )** said to be =1. i.e.

When  $k=1$ :

Or in general

$$M(k=1) = \sqrt{L_1 L_2}$$

$$M = k\sqrt{L_1 L_2} \text{ where } 0 \leq k \leq 1$$

### b. Energy stored magnetically-coupled coils

To determine the energy stored in two magnetically coupled coils, refer to Fig. 4. In this figure we consider the two coils (coil 1 and coil 2) of self-inductances  $L_1$  and  $L_2$  and mutual inductance  $M$ . Initially the system carries no current and therefore stores no energy.

The synchronized graphs in Fig. 4 show the voltages, currents powers and accumulative energy of the system drawn in a way consistent with the basic equations indicated in Fig. 3. Fig. 4 shows that:

- During  $t_1$ : a constant voltage is applied to coil 1, while coil 2 is open-circuited. The current of coil 1 increases linearly. The power absorbed by coil 1 is the triangular shape and the energy transferred to the coils is given by:

$$W_{t_1} = \int_0^{t_1} p_1(t) + p_2(t) dt = \int_0^{t_1} v_1(t)i_1(t) + v_2(t)i_2(t) dt$$

$$W_{t_1} = \int_0^{t_1} V_1 \frac{V_1 t}{L_1} + v_2(t) \times 0 dt = \frac{V_1^2 t_1^2}{2L_1}$$

$$\text{Since } i_{L1}(t_1) = I_1 = \frac{V_1 t_1}{L_1}$$

$$W_{t_1} = \frac{1}{2} L_1 I_1^2$$

Now assume that the current of coil 1 is maintained at  $I_1$  after  $t_1$ .

After the above described event:

- During  $t_2$ : a constant voltage is applied to coil 2, while coil 1 current is held constant. The current of coil 2 increases linearly. The power absorbed by coil 2 is the triangular shape and the energy transferred to the coil is (by similarity to the above derivation)  $= \frac{1}{2} L_2 I_2^2$ . During the same time another amount of energy is absorbed by the magnetically-coupled coils. This energy is equivalent to the area of the rectangular  $p_1$  during  $t_2$  and equivalent to  $M I_1 I_2$ . This second amount of energy is supplied by the circuit of  $L_1$  which is maintaining  $I_1$  constant as suggested earlier.

So we can see that the total energy stored in the two magnetically-coupled coils is:

$$W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M I_1 I_2$$

**Example 2:** Two magnetically-coupled coils with  $L_1 = 0.4 \text{ H}$ ,  $L_2 = 2.5 \text{ H}$ ,  $k = 0.6$ , and  $i_1 = 4i_2 = 20 \cos(500t - 20^\circ) \text{ mA}$ . Determine  $v_1(0)$  and the total energy stored in the system at  $t = 0$ .

**Sol.**

In order to determine the value of  $v_1$ , we need to include the contributions from both the self-inductance of coil 1 and the mutual inductance:

$$M = k\sqrt{L_1 L_2} = 0.6\sqrt{0.4 \times 2.5} = 0.6 \text{ H}$$

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_1(0) = 0.4[20 \times 500(-\sin(500(0) - 20))] + 0.6 \frac{1}{4}[20 \times 500(-\sin(500(0) - 20))] \text{ mV}$$

$$v_1(0) = 5.5 \times \sin(20) = 1.8811 \text{ V}$$

$$i_1(0) = 20 \cos(-20) = 18.794 \text{ mA}; i_2(0) = \frac{i_1(0)}{4} = 4.698 \text{ mA}$$

$$W(0) = \frac{1}{2} 0.4(18.794 \times 10^{-3})^2 + \frac{1}{2} 2.5(4.698 \times 10^{-3})^2 + 0.6 \times 18.794 \times 4.698 \times 10^{-6}$$

$$W(0) = 0.1512 \text{ mJ}$$

--- Book Practice 13.4 P504.  
---covered Text Book Exercises 1-to-29


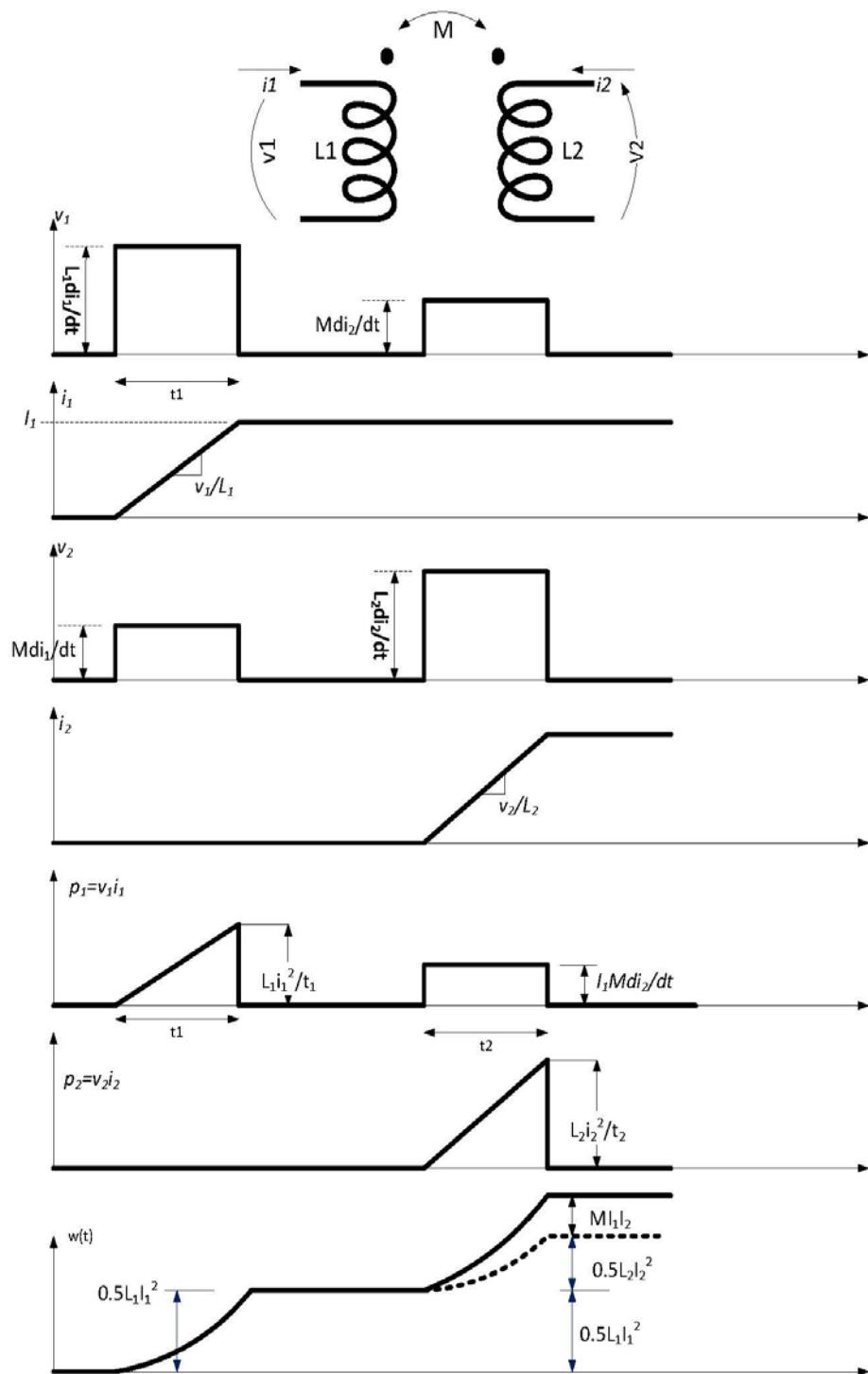


Fig.4

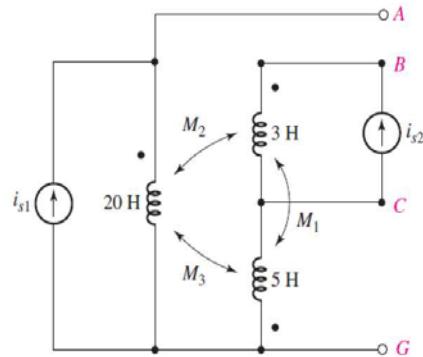16. Consider the circuit of Fig. 13.46. The two sources are  $i_{s1} = 2 \cos t$  mA and  $i_{s2} = 1.5 \sin t$  mA. If  $M_1 = 2$  H,  $M_2 = 0$  H, and  $M_3 = 10$  H, calculate  $v_{AG}(t)$ .



■ FIGURE 13.46

Sol.

$$I_{s1} = 2\angle 0^\circ; I_{s2} = 1.5\angle -90^\circ$$

$$\omega = 1 \text{ rad/sec}$$


$$V_{AG} = I_1 j X L_1 + I_2 j X M_2 + I_3 j X M_3$$

$$V_{AG} = 2j20 + I_2 j0 + 0jX M_3$$

$$V_{AG} = j40 = 40\angle 0^\circ$$

$$v_{AG} = 40 \cos(t + 90)\text{mV}$$

21. Note that there is no mutual coupling between the 5 H and 6 H inductors in the circuit of Fig. 13.50. (a) Write a set of equations in terms of  $\mathbf{I}_1(j\omega)$ ,  $\mathbf{I}_2(j\omega)$ , and  $\mathbf{I}_3(j\omega)$ . (b) Find  $\mathbf{I}_3(j\omega)$  if  $\omega = 2 \text{ rad/s}$ .

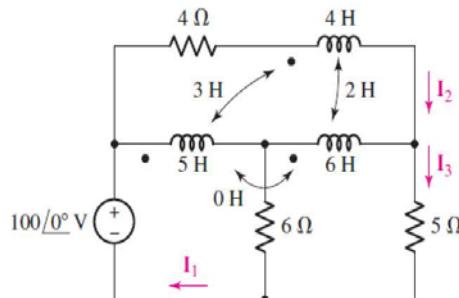**FIGURE 13.50**

$$100\angle 0^\circ = j10(I_1 - I_2) + j6I_2 + 6(I_1 - I_3)$$

$$100\angle 0^\circ = I_1(6 + j10) - I_2(j4) - I_3(6) \quad (1)$$

$$0 = 4I_2 + j8I_2 + j6(I_1 - I_2) + j4(I_3 - I_2) + j12(I_2 - I_3) - j4I_2 + j10(I_2 - I_1) - j6I_2$$

$$0 = I_1(-j4) + I_2(4 + j10) + I_3(-j8) \quad (2)$$

$$0 = 6(I_3 - I_1) + j12(I_3 - I_2) + j4I_2 + 5I_3$$

$$0 = -6I_1 + I_2(-j8) + I_3(11 + j12) \quad (3)$$

Rewrite in matrix form

$$\begin{bmatrix} 100\angle 0^\circ \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} (6 + j10) & -j4 & -6 \\ -j4 & (4 + j10) & -j8 \\ -6 & -j8 & (11 + j12) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 6.067 - j9.54 \\ 6.115 - j4.178 \\ 2.521 - j3.51 \end{bmatrix} = \begin{bmatrix} 11.31\angle -57.55^\circ \\ 7.41\angle -34.34^\circ \\ 4.32\angle -54.31^\circ \end{bmatrix} (A)$$











## Lectures of Electrical Engineering Department

**S**ubject Title: Electrical Networks

**C**lass: 2<sup>nd</sup> Stage

Lecture Contents	Lecture sequences:	11 <sup>nd</sup> lecture	Instructor Name: Omer Sharaf Aldeen Ali Abbawi
	<p><b>The major contents:</b></p> <p><b>Magnetically-Coupled Circuits: Linear Transformer</b></p>		
<p><b>The detailed contents:</b></p> <p><b>1- The Linear Transformer</b></p> <p><b>2- The T-Model</b></p> <p><b>3- The <math>\Pi</math> model</b></p>			

### Magnetically-Coupled Circuits: Linear Transformer

Two magnetically coupled coils form a transformer. The transformer circuits have two features: first they are analyzed as ac circuits and second the analysis focus on the effect of the transform on the load and the supply.

#### 1. The Linear Transformer

The transform has two magnetically coupled coils one is connected to the supply and the other to the load. In the circuit shown in Fig. 1, the coil connected to the supply side (usually known as the primary side) has a resistance  $R_1$  and self-inductance  $L_1$ . The second coil connected to the load is known as the secondary side has a resistance  $R_2$  and self-inductance  $L_2$ . The impedance  $Z_s$  represent the internal impedance of the supply and  $M$  is the mutual inductance between  $L_1$  and  $L_2$ .

The following analysis aims to determine the effect of the transformer compared to the case of connecting the load directly to the supply. The analysis start by determining the currents  $I_1$  and  $I_2$  using the circuit parameters.

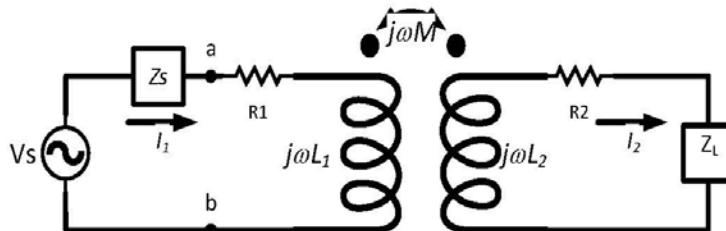


Fig. 1

#### Reflected Impedance:

To determine  $I_1$  and  $I_2$ , write the loop equations:

$$V_s = I_1(Z_s + R_1 + j\omega L_1) - j\omega M I_2 \quad \dots(1)$$

$$0 = -j\omega M I_1 + I_2(R_2 + j\omega L_2 + Z_L) \quad \dots(2)$$

To simplify manipulation, denote:  $(Z_s + R_1 + j\omega L_1)$  by  $Z_{11}$  and  $(R_2 + j\omega L_2 + Z_L)$  by  $Z_{22}$ . Equation (2) gives:

$$I_2 = \frac{j\omega M}{Z_{22}} I_1$$

Substitute into (1):

$$V_s = I_1 \left( Z_{11} + \frac{\omega^2 M^2}{Z_{22}} \right)$$

Giving:

$$I_1 = \frac{Z_{22}}{Z_{11} Z_{22} + \omega^2 M^2} V_s$$

And

$$I_2 = \frac{j\omega M}{Z_{22}} I_1 = \frac{j\omega M}{Z_{11}Z_{22} + \omega^2 M^2} V_s$$

Now the impedance seen by the voltage source is  $\frac{V_s}{I_1}$

$$Z_t = Z_{11} + \frac{\omega^2 M^2}{Z_{22}}$$

The impedance of the circuit seen at the source terminals:

$$Z_{ab} = Z_t - Z_s$$

$$Z_{ab} = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{(R_2 + j\omega L_2 + Z_L)}$$

The last term of the above equation is defined as the “reflected impedance” as it represents the image of the secondary circuit seen at the primary side.

$$Z_r \triangleq \frac{\omega^2 M^2}{(R_2 + j\omega L_2 + Z_L)}$$

**Example 1:** The parameters of a linear transformer are:

$R_1(\Omega)$	$R_2(\Omega)$	$L_1(H)$	$L_2(H)$	$k$
200	100	9	4	0.5


This transformer is used to connect a 300V, 400rad/sec source with internal impedance of  $(500+j100)\Omega$  to a load consists of series  $800\Omega$  resistor and  $1\mu F$  capacitor. // the supply voltage should be taken as rms and at angle =zero; as it has not been indicated otherwise//

- (a) Draw the equivalent circuit in frequency domain // in frequency domain (unlike time domain) implies to write the reactance as impedance and represent ac quantities as vectors// \
- (b) Calculate the self-impedance of the primary side
- (c) Calculate the self-impedance of the secondary side
- (d) Calculate the impedance reflected into the primary winding.
- (e) Calculate the impedance seen looking at the primary terminals of the transformer.
- (f) Calculate the primary current.
- (g) Calculate the secondary current.
- (h) Calculate the voltage at the load terminals.
- (i) Calculate the power delivered to load.
- (j) Determine the percentage of the power delivered to the load to the power received by the transformer.

Sol.

$L_1$ (H)	$j\omega L_1$ (Ω)	$L_2$ (H)	$j\omega L_2$ (Ω)	$k$	$M$ (H)	$j\omega M$ (Ω)	$C$ (F)	$j1/\omega C$
9	$j3600$	4	$j1600$	0.5	3	$j1200$	$1\mu$	$-j2500$

The equivalent circuit:

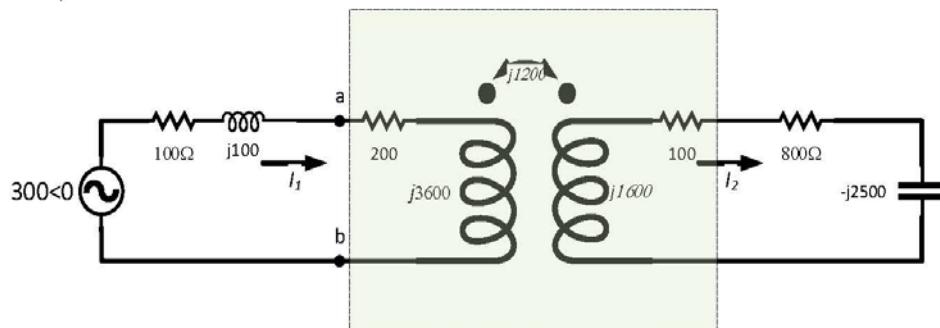

1. the self-impedance of the primary side :

$$Z_{11} = 100 + 200 + j(100 + 3600) = (300 + j3700)\Omega$$

2. the self-impedance of the secondary side

$$Z_{22} = 100 + 800 + j(1600 - 2500) = (900 - j900)\Omega$$

3. the impedance reflected into the primary winding.

$$Z_r = \frac{\omega^2 M^2}{(R_2 + j\omega L_2 + Z_L)} = \frac{(1200)^2}{(900 - j900)} = (800 + j800)\Omega$$

4. the impedance seen looking at the primary terminals of the transformer.

$$Z_{ab} = 200 + j3600 + 800 + j800 = (1000 + j4400)\Omega$$

5. the primary current.

$$I_s = \frac{V_s}{Z_s + Z_{ab}} = \frac{300\angle 0}{1500 + j4500} = (20 - j60)mA$$

6. the secondary current.

$$I_2 = \frac{j\omega M}{Z_{22}} I_1 = \frac{j1200}{(900 - j900)} (20 - j60) = \frac{(80 + j160)}{3} mA$$

$$I_2 = 59.63\angle 63.43mA$$

7. the voltage at the load terminals.

$$V_L = I_2 Z_L = \frac{(80 + j160) * 10^{-3} * (800 - j2500)}{3}$$

$$V_L = 156.5\angle -8.82^\circ V$$

8. the power delivered to load.

$$P_L = |I_2|^2 R_L = (0.05963)^2 \times 800 = 2.844W$$

9. the percentage of the power delivered to the load to the power received by the transformer.

$$P_{IN} = |I_1|^2 (R_1 + R_r) = 4W$$

$$\% \frac{P_o}{P_{in}} = \frac{2.844}{4} \times 100\% = 71.1\%$$

### b. T and II model

It is convenient to represent the magnetically-coupled coils by a basic inductor elements removing the mutual inductance. T and II models have been derived as equivalent circuit for the two mutual inductors in linear transformer. This section shows how to develop these model.

#### The T-Model:

Consider the linear transformer shown in Fig. 2; where the lower terminal of the two sides is connected to form a three-point arrangement. Refer to the T-equivalent model shown in Fig. 3. For both circuits the following equations are applicable:

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

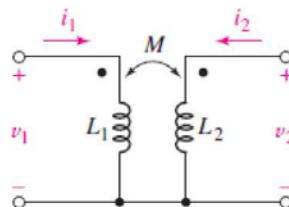


Fig. 2


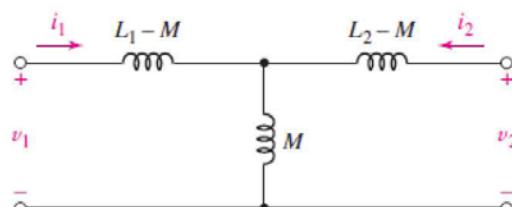


Fig. 3

If one of the dots of the coils in Fig. 2, is changed to the other coil side, the effect of this on the equation voltages can be seen as if M has been replaced by  $(-M)$  then the three elements in of the equivalent circuit in Fig. 3 become  $(L_1+M)$ ,  $(-M)$  and  $(L_2+M)$ .
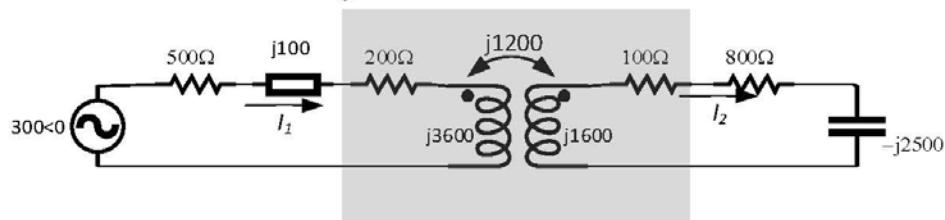
#### Example 2:

Find  $I_1$  and  $I_2$  in the circuit shown using T-model.



**Sol.**


(a) Considering the dots positions:

$$XL_1 - XM = 3600 - 1200 = 2400$$

$$XL_2 - XM = 1600 - 1200 = 400$$

$$XM = 1200$$

Now redraw the circuit with the T-model

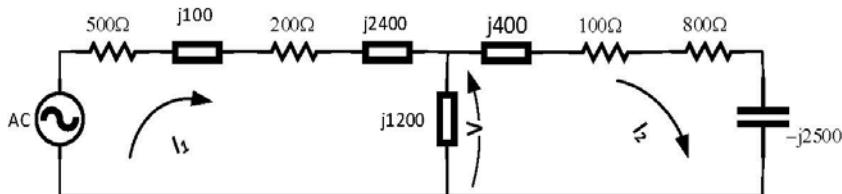

Now write the equation of the middle node currents in terms of V.

$$\frac{V - 300}{700 + j2500} + \frac{V}{j1200} + \frac{V}{900 - j2100} = 0$$

Gives

$$V = 136 - j8 = 136.24\angle - 3.37^\circ$$

Then

$$I_1 = \frac{300 - V}{700 + j2500} = 63.25\angle - 71.57^\circ mA$$

And

$$I_2 = \frac{V}{900 - j2100} = 59.63\angle 63.43^\circ mA$$

**Practice:** Repeat Example2 with the polarity dot on the secondary side moved to the lower terminal.

### The II-model:

We can derive the II- model of the coils shown in Fig 2 using the voltage equations:

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

The following derivation is based on solving the equations for  $\frac{di_1}{dt}$  and  $\frac{di_2}{dt}$  and then regarding the resulting expressions as a pair of node-voltage equations; as follows:

$$\frac{di_1}{dt} = \begin{vmatrix} v_1 & M \\ v_2 & L_2 \\ \hline L_1 & M \\ M & L_2 \end{vmatrix} = \frac{L_2}{L_1 L_2 - M^2} v_1 - \frac{M}{L_1 L_2 - M^2} v_2;$$

$$\frac{di_2}{dt} = \begin{vmatrix} L_1 & v_1 \\ M & v_2 \\ \hline L_1 & M \\ M & L_2 \end{vmatrix} = -\frac{M}{L_1 L_2 - M^2} v_1 + \frac{L_1}{L_1 L_2 - M^2} v_2$$

By multiplying both sides of the above equations by  $dt$  then integrating

$$i_1 = i_1(0) + \frac{L_2}{L_1 L_2 - M^2} \int_0^t v_1 dx - \frac{M}{L_1 L_2 - M^2} \int_0^t v_2 dx$$

$$i_2 = i_2(0) - \frac{M}{L_1 L_2 - M^2} \int_0^t v_1 dx + \frac{L_1}{L_1 L_2 - M^2} \int_0^t v_2 dx$$

Now regard  $v_1$  and  $v_2$  as two node equations of the circuit shown in Fig. 4

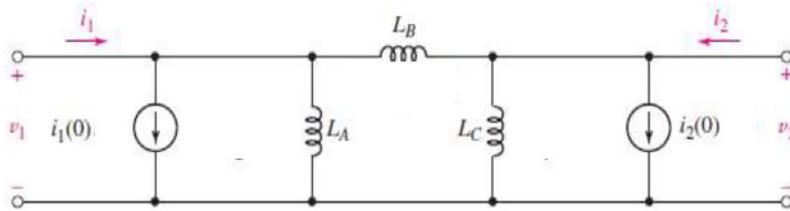


Fig. 4

$$i_1 = i_1(0) + \frac{1}{L_A} \int_0^t v_1 dx + \frac{1}{L_B} \int_0^t (v_1 - v_2) dx$$

$$i_2 = i_2(0) + \left( \frac{1}{L_A} + \frac{1}{L_B} \right) \int_0^t v_1 dx - \frac{1}{L_B} \int_0^t v_2 dx$$

And

$$i_2 = i_2(0) + \frac{1}{L_C} \int_0^t v_2 dx + \frac{1}{L_B} \int_0^t (v_2 - v_1) dx$$

$$i_2 = i_2(0) - \frac{1}{L_B} \int_0^t v_1 dx + \left( \frac{1}{L_B} + \frac{1}{L_C} \right) \int_0^t v_2 dx$$

By comparing to the above equations:

$$L_B = \frac{L_1 L_2 - M^2}{M}$$


$$L_A = \frac{L_1 L_2 - M^2}{L_2 - M}$$

$$L_C = \frac{L_1 L_2 - M^2}{L_1 - M}$$

Evidently in ac steady-state analysis, the initial current sources become zero; moreover we could have been used the Y-Δ equations to obtain the equivalent model //without so much hustle @//. But the Π-model that has been derived is more general indeed. It shows the effect of initial current which is necessary if the circuit transient model is required.

**Example 3:**

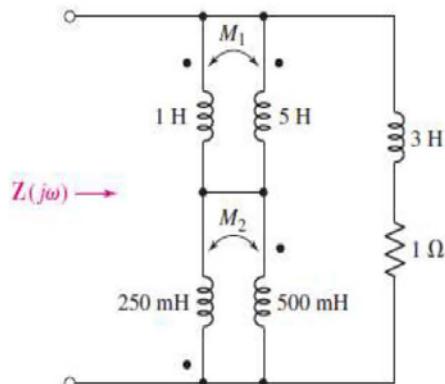39. With respect to the network shown in Fig. 13.63, derive an expression for  $Z(j\omega)$  if  $M_1$  and  $M_2$  are set to their respective maximum values.




■ FIGURE 13.63

Sol.

$$M_{1,max} = \sqrt{1 * 5} = \sqrt{5} H$$

$$M_{2,max} = \sqrt{\frac{1}{4} * \frac{1}{3}} = \frac{1}{2\sqrt{2}} H$$

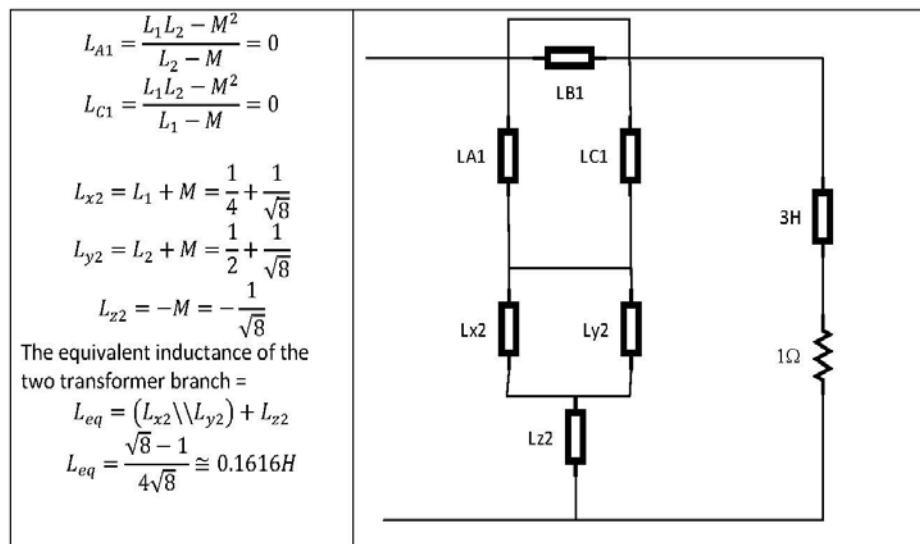We replace the first transformer by the Π equivalent model and the second by T model



$$Z(j\omega) = (j\omega L_{eq}) / (1 + j3\omega)$$

$$Z(j\omega) = \frac{-3L_{eq}\omega^2 + j\omega L_{eq}}{1 + j(3 + L_{eq})\omega}$$

$$Z(j\omega) = \frac{-0.4848\omega^2 + j\omega 0.1616}{1 + j(3.1616)\omega} \Omega$$