

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

جامعة الموصل – كلية علوم الحاسوب والرياضيات
قسم الامن السيبراني

CIRCUTE DESIGN

المحاضرة الأولى
Logic Gates

Sura Sabah I. Ahmed

Logic Gates

There are a basic elements that makeup a **digital system**.

The electronic gates: It is a circuit that is able to operate on a number of binary inputs in order to perform a particular logical function. The **GATE** is used to describe a circuit that performs a basic logic operation.

According to the type of logical operation between inputs and output basically there are 8 standard gates which are used in digital circuit design.

They are: AND, OR, NOT, NAND, NOR, EXCLUSIVE-OR, EXCLUSIVE NOR, and TRANSFER (BUFFER).


AND Gate

It is one of the basic gates which has two or more inputs and one output. It performs what is known as **LOGICAL MULTIPLICATION**.

Two inputs AND Gate

If two inputs **A** and **B** are combined using the AND operation, the result can be represented as **$Y=A.B$** or **$Y=AB$** . In this expression the “dot” sign standard for Boolean AND operation.

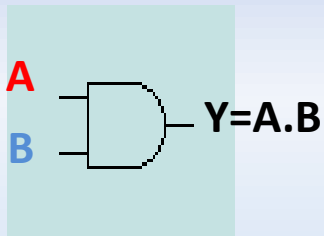The Logic symbol of Two inputs AND Gate is:



The output equation or output expression:

$$Y=A.B \quad \text{or} \quad Y=AB$$

The truth table of two inputs AND gate:

A	B	$Y=A.B$
0	0	0
0	1	0
1	0	0
1	1	1


- The operation of AND Gate is such that the output is **HIGH** only when all of the inputs are **HIGH**.
- When any of the input is **LOW**, the output is **LOW**.

AND Gate

Pulsed Operation:



In many application, the input to a gate may be voltages that change with time between the two logic levels and are called as pulsed waveform . In studying the pulsed operation of the AND gate, we consider the inputs with respect to each other in order to determine the output level at any given time.

The Logic levels:

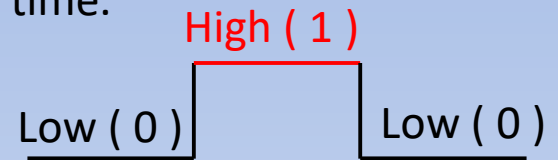

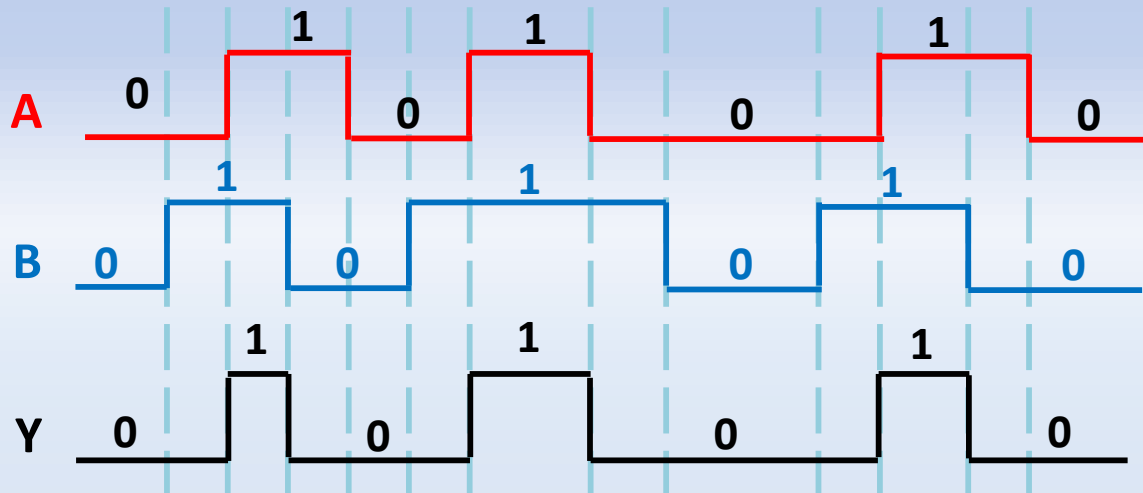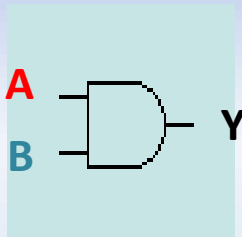Example:

Determine the output y from the AND gate for the given input waveforms shown below.




AND Gate

Standard Package:

The pin diagram of the chip (IC 7408), a TTL quad-2 input AND gate is shown below, this IC contains (Four 2-input AND gate) and it is (14-pin dual-line package).




The TTL quad-2 input AND gate (7408)

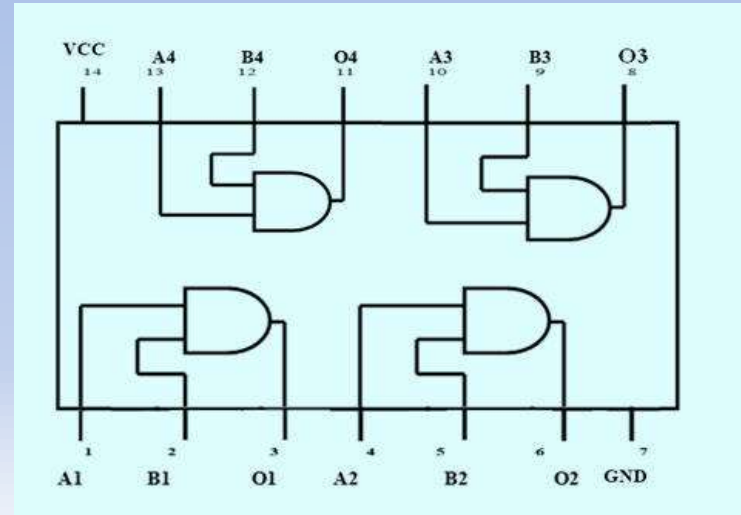

The pin diagram of the chip (IC 7408)


AND Gate

Three inputs AND gate:

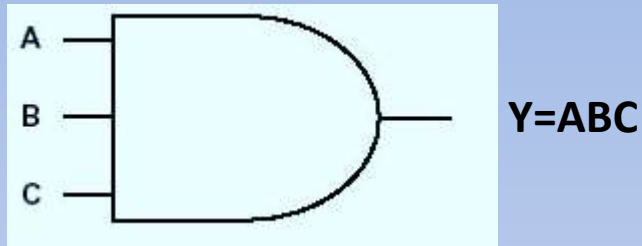

The truth table of three inputs AND gate:

INPUTS			OUTPUT
A	B	C	$Y=ABC$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

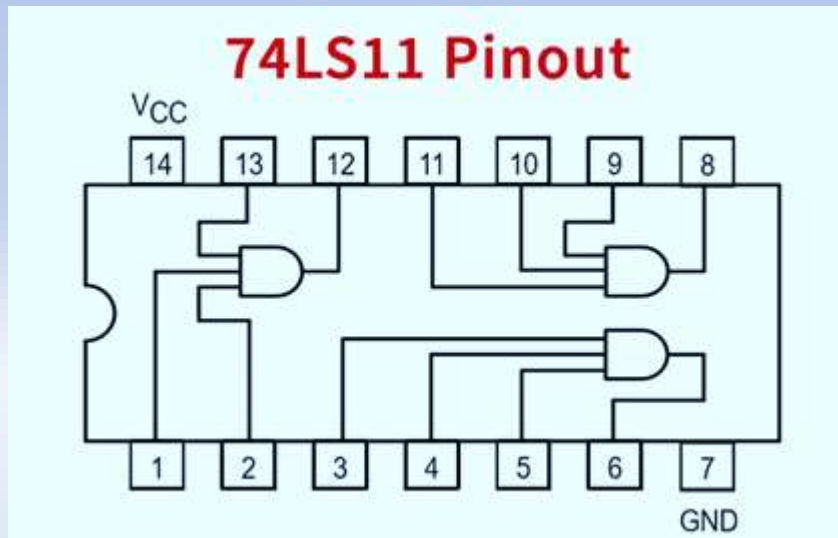




The pin diagram of the chip
(IC 7411)

AND Gate

Build a 3-inputs AND gates using **TWO** 2-nputs AND gates only?



We can use two (2-inputs AND gates) to perform three inputs AND operation.

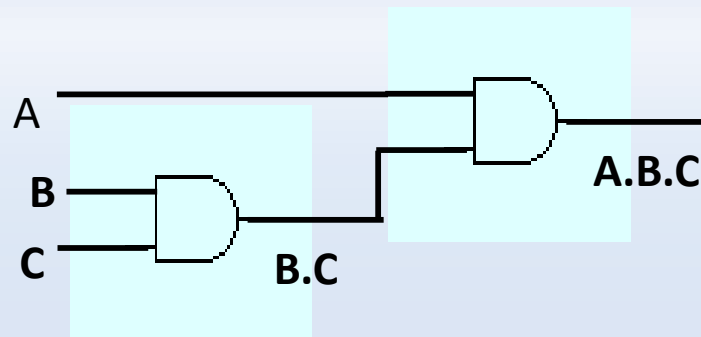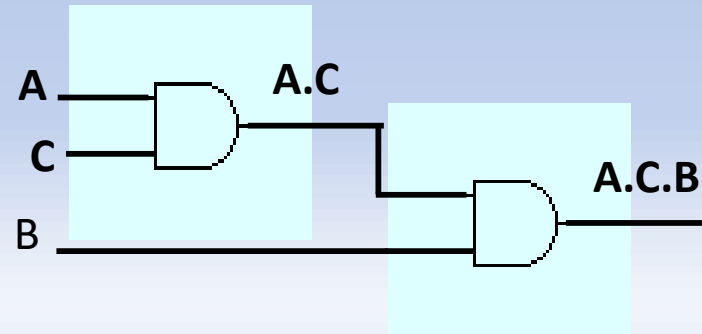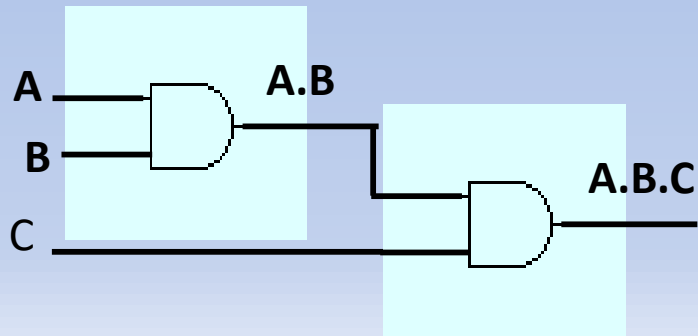Since $A.B=B.A$ then The output equation can be written as : $Y=A.B.C$ $Y=(A.B).C$
or $Y=A.(B.C)$ or $Y=(A.C).B$



AND Gate

Four inputs AND gate:

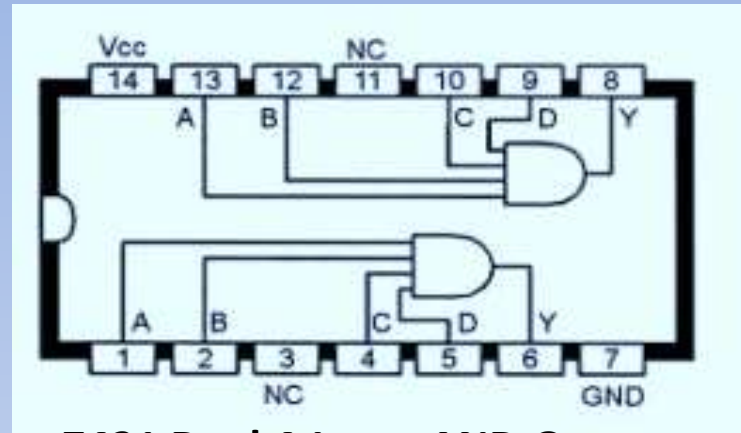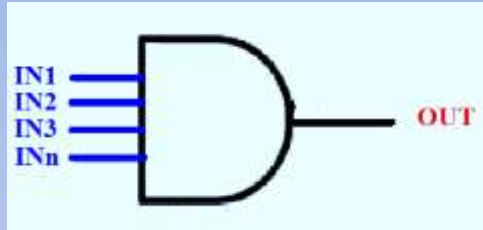

7421 Dual 4-Input AND Gates

H.W:

Write the truth table and the output equation of the 4-inputs AND gate?

Conclusion:



- 1) The AND operation is performed like ordinary multiplication of 1's and 0's.
- 2) An output equal to "1" occurs only for the single case where all inputs are "1".
- 3) The output is "0" for any case where one or more inputs are "0".
- 4) For an n-inputs AND gate, the output $Y=A.B.C.....$.
- 5) With AND operation $1.1=1$, $1.1.1.1.1$. so on=1.

AND Gate

Application Example:

The AND gate as Enable/Inhibit Device:

- A common application of the AND gate is to enable (that is to allow) the passage of a signal (pulse waveform) from one point to another at certain times and to inhibit (prevent) the passage at another times.
- A simple example of this particular use of an AND gate is shown below, where the AND gate controls the passage of a signal (waveform A). The enable pulse is applied at B input. When the enable pulse is **HIGH**, waveform passes through the gate, and when the enable pulse is **LOW**, waveform A is prevented from passing through the gate, that is inhibited (or the gate is disabled).

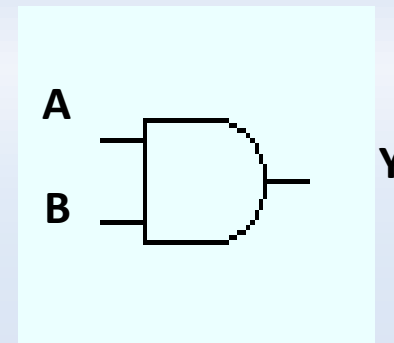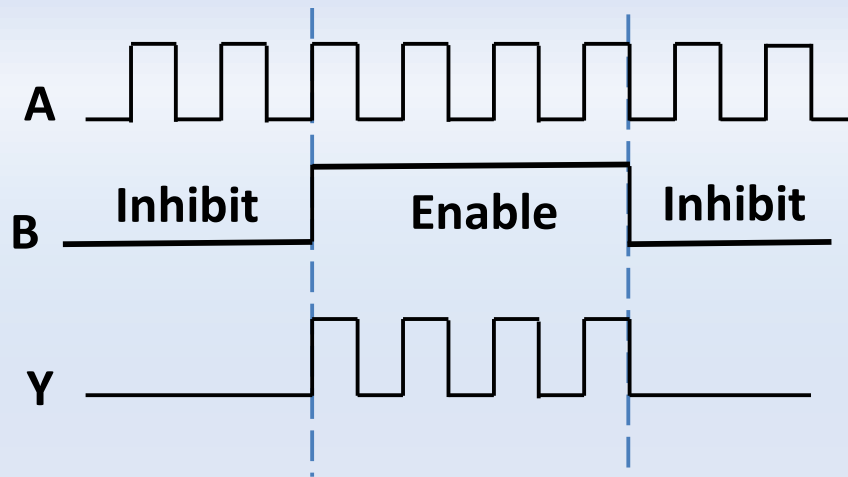

Thank you