Dr.Haleema Essa

Memory Design

RAM is made up of memory cells arranged in a grid of rows and columns. Each cell stores a bit of data, represented as either 0 or 1.

✓ Types of RAM:

- SRAM (Static RAM): Uses flip-flops to store data, providing faster access but at a higher cost and power consumption.
- o **DRAM (Dynamic RAM):** Stores data in capacitors, which need to be refreshed periodically. It's slower than SRAM but more cost-effective and has higher density.

Addressing: Each memory cell in RAM is accessed using a unique address. The address lines select the row and column to read or write data.

✓ Design Considerations:

- Size and Capacity: Determined by the number of rows and columns. For example, designing a 512x8 RAM from 128x8 RAM involves using multiple chips and a decoder to manage the increased address space.
- Speed: Influenced by the type of RAM and the design of the memory cells and access circuitry.
- Power Consumption: Important for battery-operated devices, with SRAM generally consuming more power than DRAM.
 - **❖** Designing M x N memory with D x W chips, where M and D are the *Address Space*, while N and W are used for *Data*.


Note: Always M > D, and N > W.

There are three basic steps in memory designing:

- 1. Find the Number of rows = \mathbf{M}/\mathbf{D}
- 2. Find the Number of columns = N/W
- 3. Find the Number of chips = $M/D \times N/W$


<u>Computer Science Dept. / 2nd year 1st Course (2024-2025)</u> <u>Microprocessor</u>

<u>Dr.Haleema Essa</u>

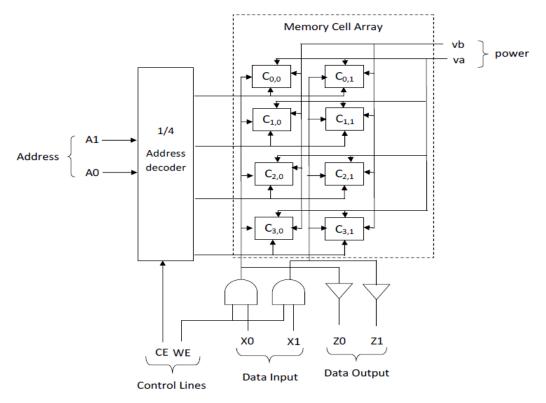

The internal structure for the 4*2-bit RAM

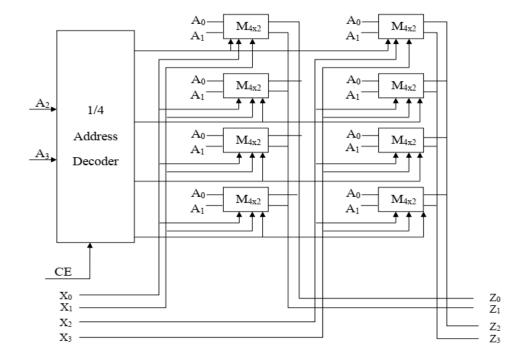Example: Design a 16*4-bit memory using 4*2-bit ICs.



Computer Science Dept. / 2nd year 1st Course (2024-2025)

Microprocessor

<u>Dr.Haleema Essa</u>

HW:

- 1. Design 64kb*8bit Memory using 8k*8bit RAM ICs.
- 2. Design 64kb*8bit Memory using 8k*4bit RAM ICs.

For Discussion: To design a 64M x 32 memory, what we could use ??