

Logical Design



Lecture 6: Boolean Algebra

Produced By: Dr. Haleema Essa


2023-2024

Laws of Boolean Algebra


1- Commutative Law

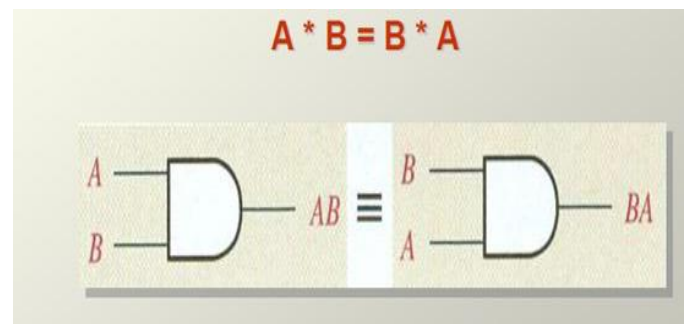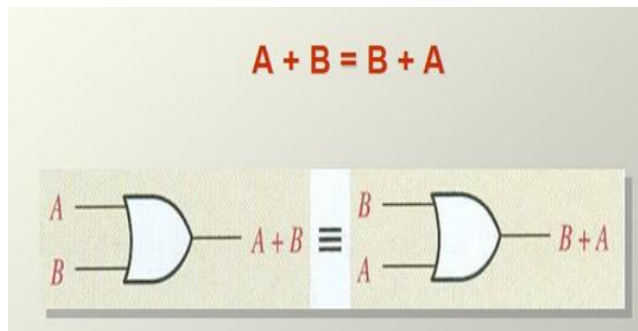


2- Associative Law (Addition)

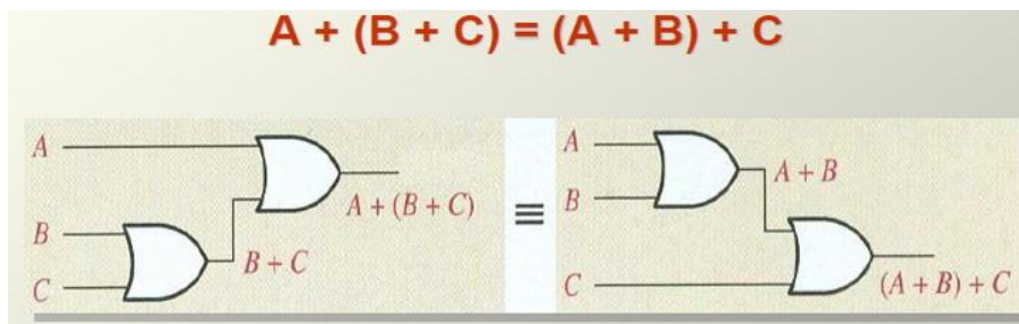

3- Associative Law (Multiplication)

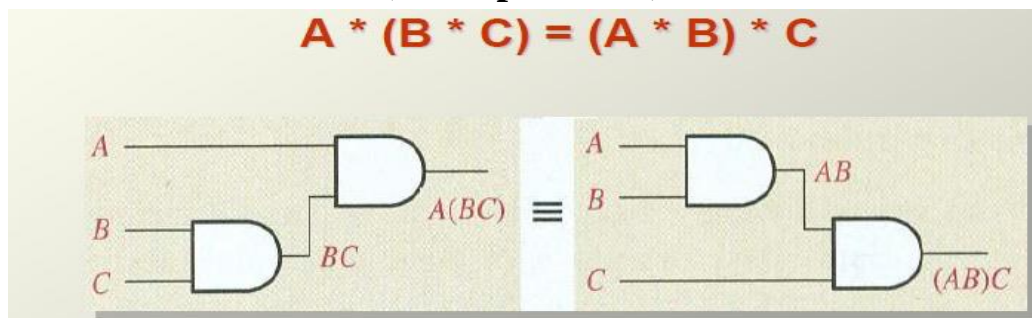

4- Distributive Law

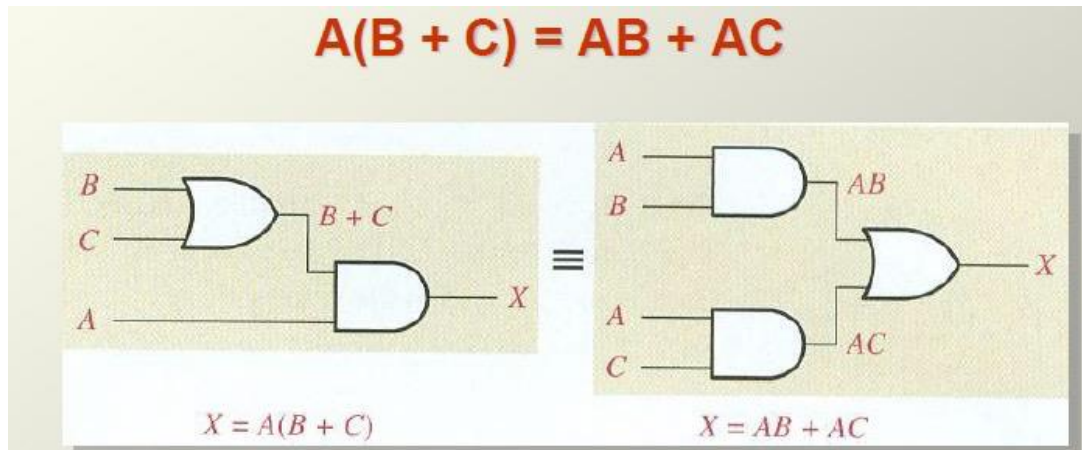


Rules of Boolean Algebra

Rule1:


a- Identity (Addition)

$$X = A + 0 = A$$

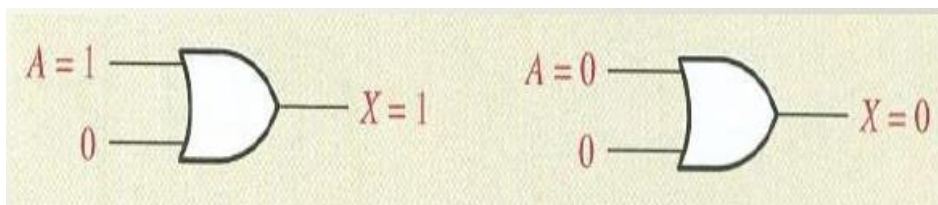

b- Identity (Multiplication)


$$X = A * 1 = A$$

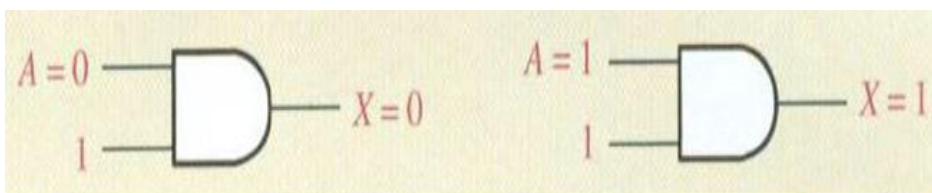

Rule2:


a- NULL Rule (Addition)

$$X=A+1=1$$

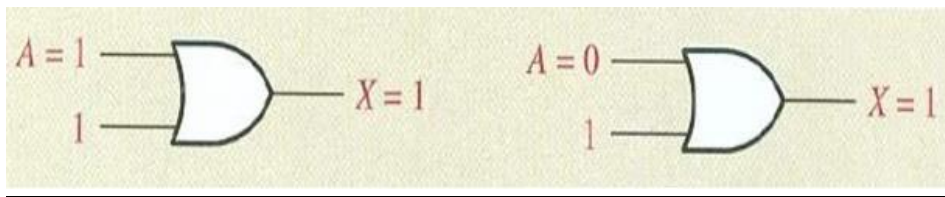

b-NULL Rule (Multiplication)


$$X=A*0=0$$

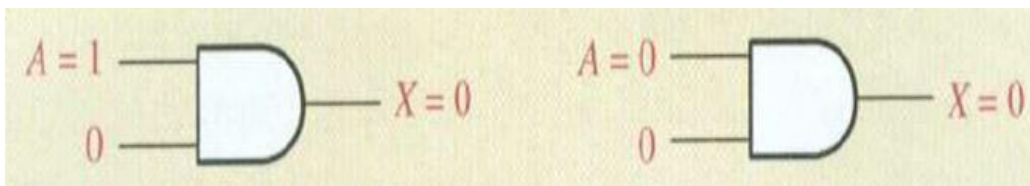

Rule3:


a- Idempotent (Addition)

$$X=A+A=A$$

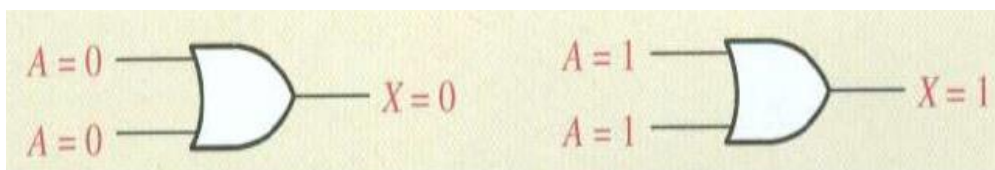

b-Idempotent (Multiplication)


$$X= A*A=A$$

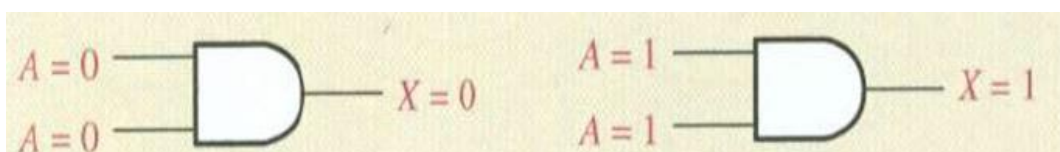

Rule4:


a- Complement (Addition)

$$X = A + \bar{A} = 1$$

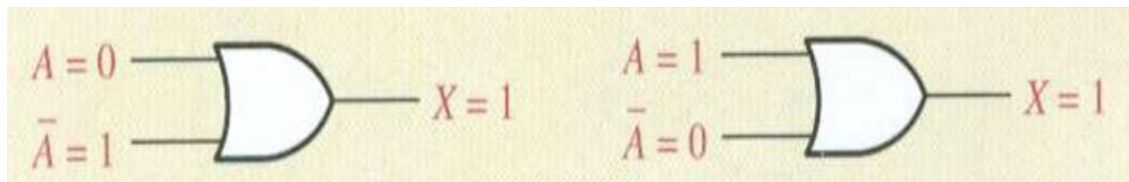

b- Complement (Multiplication)

$$X = A * \bar{A} = 0$$

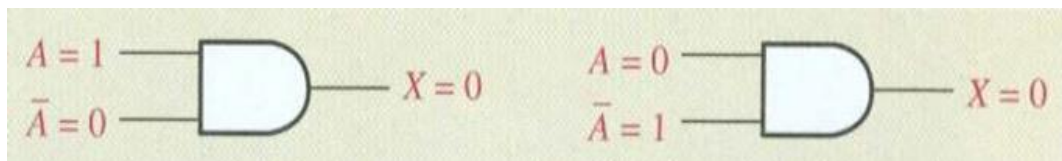

Rule4:

OR Absorption: $A + (A \cdot B) = A$

A	B	AB	A + AB
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

↑ equal ↑

Logic diagram illustrating the OR absorption rule: $A + (A \cdot B) = A$. The diagram shows an OR gate with inputs A and $(A \cdot B)$. A red arrow points to the input A , labeled "straight connection", indicating that the output is simply A .

The proof:


Left side = $A + AB$

$$\begin{aligned}
 &= A (1+B) \\
 &= A \cdot 1 \\
 &= A
 \end{aligned}$$

Rule5:

AND Absorption: $A \cdot (A + B) = A$

A	B	A+B	A.(A+B)
0	0	0	0
0	1	1	0
1	0	1	1
1	1	1	1

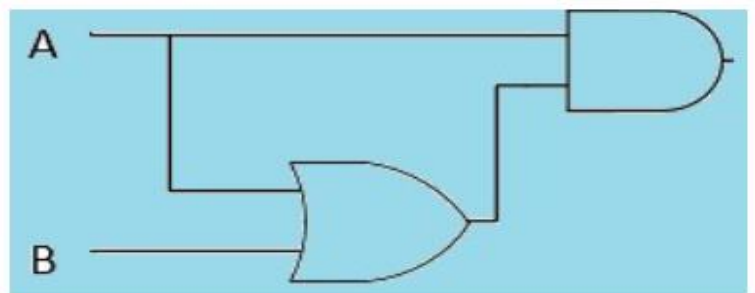

The proof:

$$\begin{aligned}
 \text{Left side} &= A(A+B) \\
 &= A \cdot A + AB \\
 &= A + AB \\
 &= A(1 + B) \\
 &= A \cdot 1 \\
 &= A
 \end{aligned}$$

Rule6:

$(A + B)(A + C) = A + BC$

A	B	C	A + B	A + C	(A + B)(A + C)	BC	A + BC
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

↑ equal ↑

The proof:


$$\begin{aligned}\text{Left side} &= (A+B)(A+C) \\ &= AA + AC + AB + BC \\ &= A + AC + AB + BC \\ &= A(1 + C + B) + BC \\ &= A \cdot 1 + BC \\ &= A + BC = \text{Right side}\end{aligned}$$

DeMorgan's Theorem (First Theorem)

The complement of a product of variables is equal to the sum of complemented variables.

$$\overline{AB} = \bar{A} + \bar{B}$$

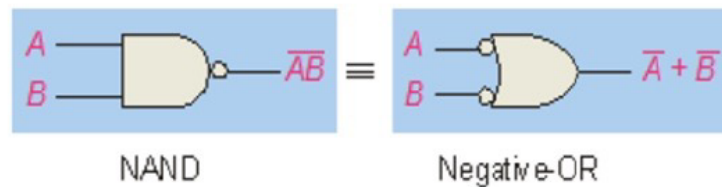Applying DeMorgan's First Theorem to gates:




A	B	~ A	~ B	~ AB	~ A + ~B
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

DeMorgan's Theorem (Second Theorem)

The complement of a sum of variables is equal to the product of complemented variables.

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

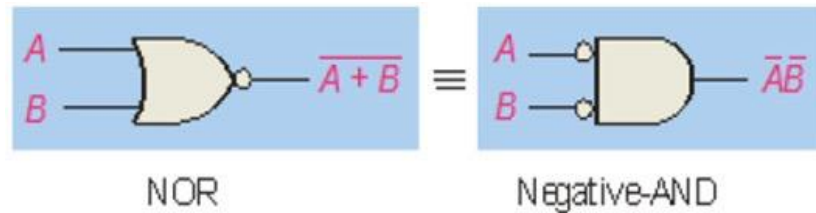Applying DeMorgan's Second Theorem to gates:



A	B	~ A	~ B	~ (A+B)	~ A . ~B
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

Example 1: Apply DeMorgan's theorem to simplify the following expression.

$$X = \overline{\bar{C} + D}$$

To apply DeMorgan's theorem to the above expression, we can break the over-bar that covers both terms and change the sign between them as follows:

$$X = \bar{\bar{C}} \cdot \bar{D}$$

$$X = C \cdot \bar{D}$$


Example 2: Simplify the following expression, and then draw the logic circuit after simplification.

$$Y = \overline{\bar{A} + \bar{B} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}}$$

$$= \bar{A} \bar{B} + \bar{A} + \bar{B} + \bar{C} + \bar{A} + B$$

$$= \bar{A}(\bar{B} + 1 + 1) + (B + \bar{B}) + \bar{C}$$

$$= \bar{A} + \bar{C}$$

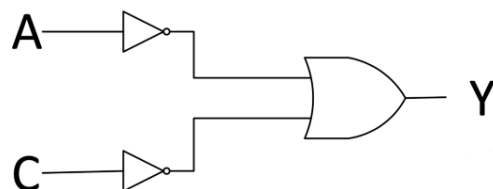

Example 3: Simplify the following expression.

$$\begin{aligned}
 Y &= (A+B)(A+\bar{B}) \\
 &= AA + A\bar{B} + AB + B\bar{B} \\
 &= A + A(\bar{B} + B) \\
 &= A+A \\
 &= A
 \end{aligned}$$

OR:

$$\begin{aligned}
 Y &= AA + A\bar{B} + AB + B\bar{B} \\
 &= AA + A\bar{B} + AB \\
 &= A + A\bar{B} + AB \\
 &= A(1 + \bar{B} + B) \\
 &= A \cdot 1 \\
 &= A
 \end{aligned}$$

H.W: Simplify the following expression.

$$\begin{aligned}
 1- Y &= ABC + A\bar{B}C + AB\bar{C} \\
 2- Y &= ABC + A\bar{B}(\bar{A}\bar{C})
 \end{aligned}$$

Example4: Determine if the following equation is valid (Derived from the truth table)

$$\bar{X}_1 \bar{X}_3 + X_2 X_3 + X_1 \bar{X}_2 = \bar{X}_1 X_2 + X_1 X_3 + \bar{X}_2 \bar{X}_3$$

Left-Hand Side (LHS)						
Row number	x_1	x_2	x_3	$\bar{x}_1 \bar{x}_3$	$x_2 x_3$	$x_1 \bar{x}_2$
0	0	0	0	1	0	0
1	0	0	1	0	0	0
2	0	1	0	1	0	0
3	0	1	1	0	1	0
4	1	0	0	0	0	1
5	1	0	1	0	0	1
6	1	1	0	0	0	0
7	1	1	1	0	1	0

Right-Hand Side (RHS)						
Row number	x_1	x_2	x_3	$\bar{x}_1 x_2$	$x_1 x_3$	$\bar{x}_2 \bar{x}_3$
0	0	0	0	0	0	1
1	0	0	1	0	0	0
2	0	1	0	1	0	0
3	0	1	1	1	0	0
4	1	0	0	0	0	1
5	1	0	1	0	1	0
6	1	1	0	0	0	0
7	1	1	1	0	1	0

H.W: For the given equation, give the *truth table*, then *simplify* and *draw* the circuit *before and after* simplification.

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}BC + AB\bar{C} + ABC$$