

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

جامعة الموصل – كلية علوم الحاسوب والرياضيات  
قسم الامن السيبراني

## CIRCUTE DESIGN

المحاضرة الثانية  
Logic Gates

**Sura Sabah I. Ahmed**

## OR Gate


- An Or gate can have two or more inputs and one output.
- It performs what is known as **LOGICAL ADDITION**.
- It produces a **HIGH** on the output when any of the inputs is **HIGH**.
- The output is **LOW** only when all of the inputs are **LOW**.

### Two inputs OR Gate


If two inputs **A** and **B** are combined using the OR operation, the result can be represented as  **$Y=A+B$** .

The output equation  
or output expression:

$$Y=A+B$$

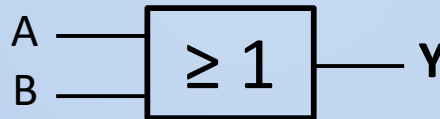

The Logic symbol of Two  
inputs OR Gate

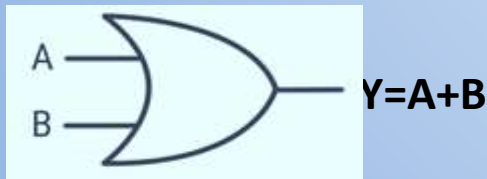

The truth table of two  
inputs OR gate:

A	B	$Y=A+B$
0	0	0
0	1	1
1	0	1
1	1	1


## OR Gate

Example:

Determine the output y from the OR gate for the given input waveforms shown below.



$$Y = A + B$$

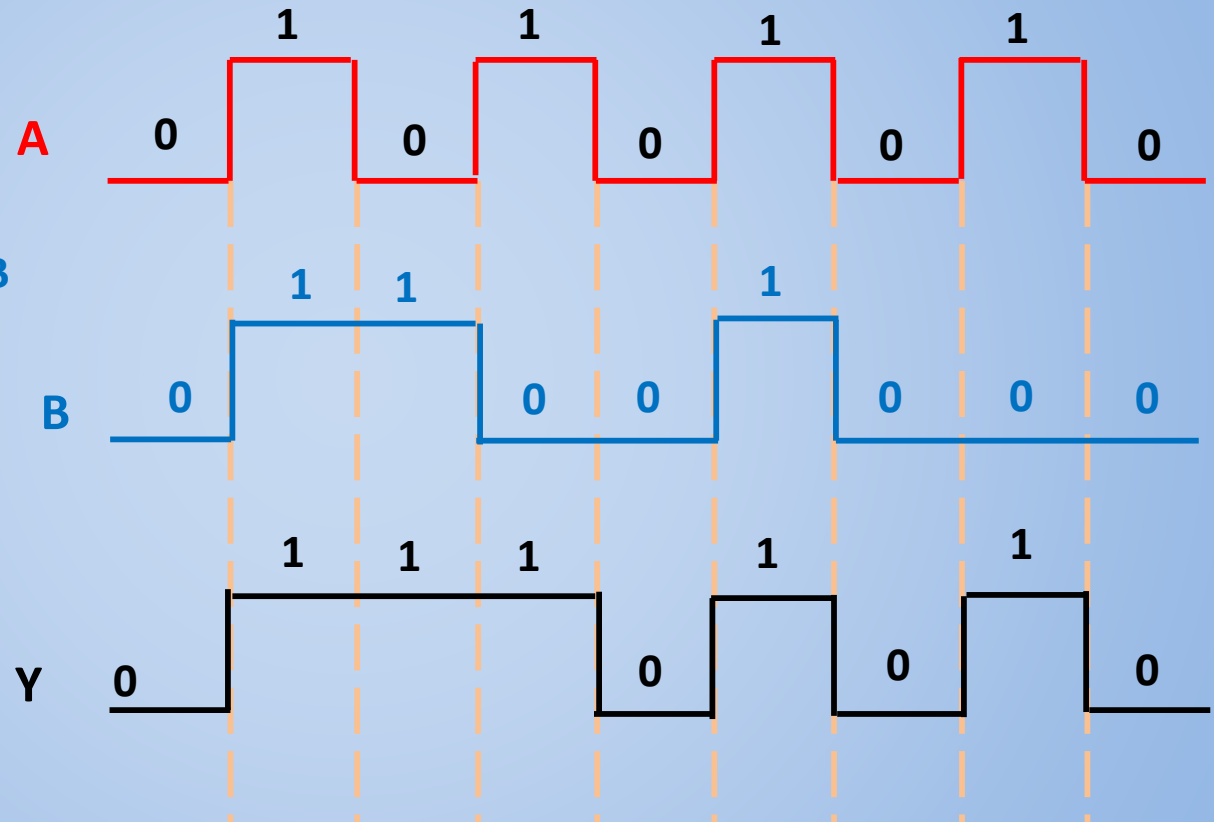


## OR Gate

Standard Package:

The pin diagram of the chip (IC 7432), a TTL quad-2 input OR gate is shown below, this IC contains (Four 2-input OR gate) and it is (14-pin dual-line package).




The TTL quad-2 input OR gate (7432)

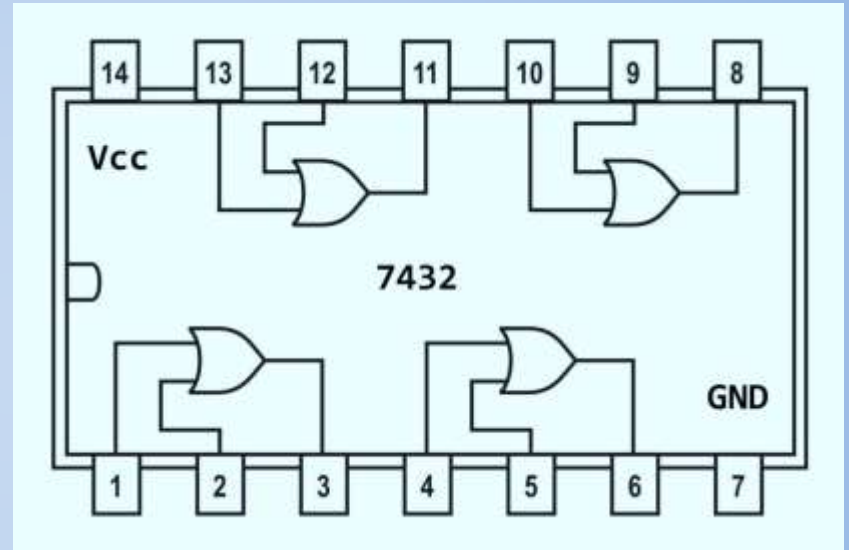

The pin diagram of the chip (IC 7432)

## OR Gate


Three inputs OR gate:

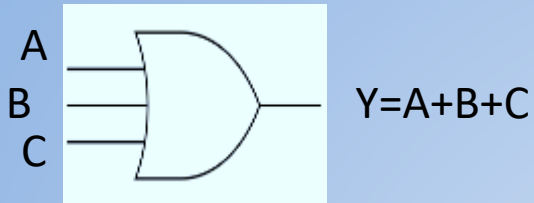

The output equation:  $Y=A+B+C$

The truth table of three inputs OR gate:

INPUTS			OUTPUT
A	B	C	$Y=A+B+C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

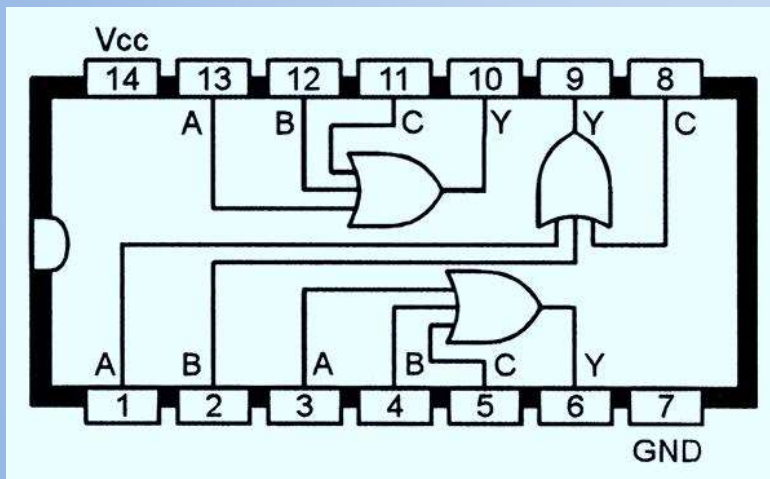




The pin diagram of the 3-inputs OR gate

## OR Gate

Build a 3-inputs OR gates using **TWO** 2-inputs OR gates only?



We can use two (2-inputs or gates) to perform three inputs OR operation.

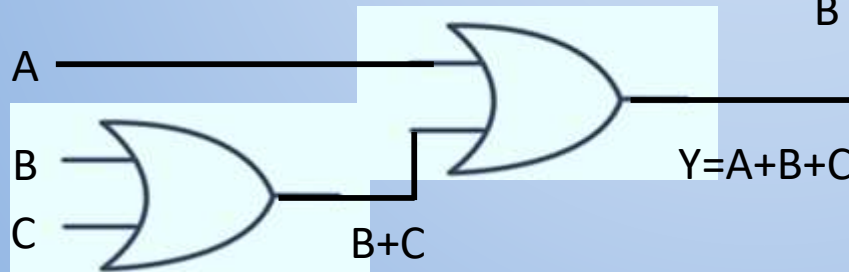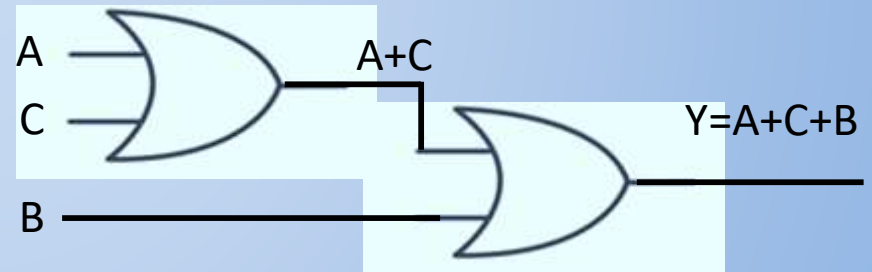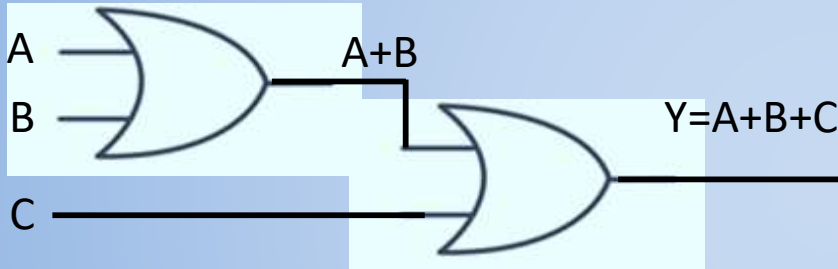Since  $A+B=B+A$  then The output equation can be written as :  $Y=A+B+C$ .  
 $Y=(A+B)+C$  or  $Y=A+(B+C)$  or  $Y=(A+C)+B$



## OR Gate

Four inputs OR gate:

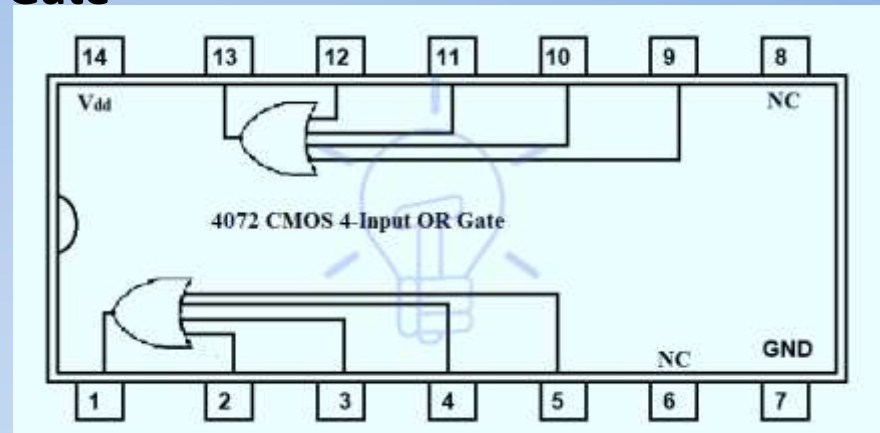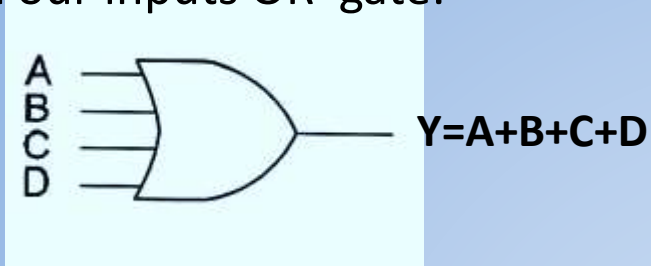


H.W:

### Dual 4-Input OR Gates

Write the truth table and the output equation of the 4-inputs OR gate?

N inputs OR gate:

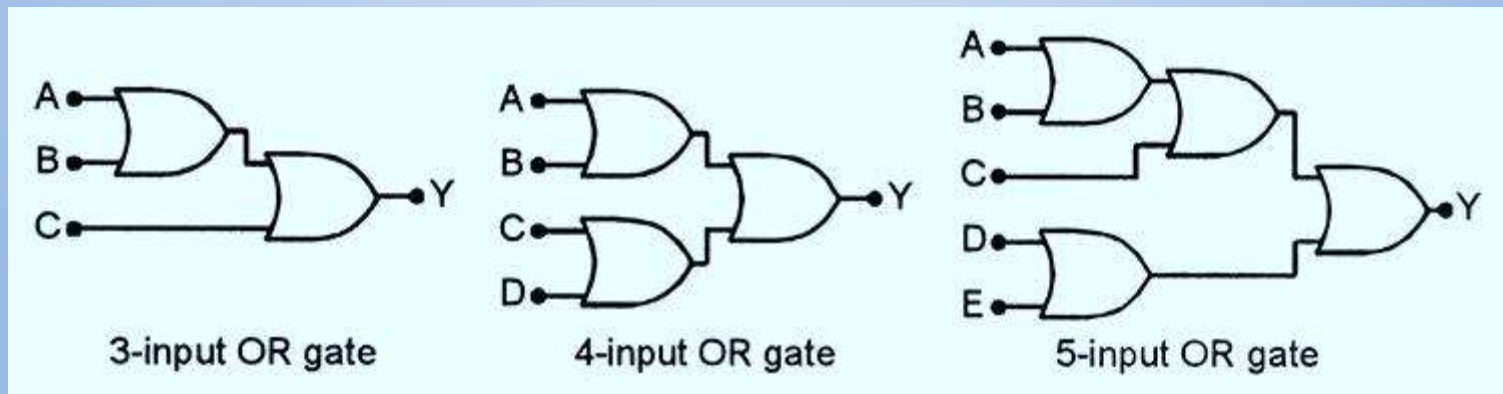

## OR Gate

### Conclusion:


- 1- The OR operation produces a result of “1” when any of the input variable is “1”.
- 2- The OR operation produces a result of “0” **only** when all the input variables are “0”.
- 3- With OR operation  $1+1=1$ ,  $1+1+1+1 \dots=1$ .

### Application Example:

A simple portion of an intrusion detection and alarm system is shown below, this system could be used for one room in a home, a room with two windows and one door. The sensor are magnetic switches that produce a HIGH output when open and a LOW output when closed. As long as the windows and the door are secured, the switches are closed and all three of the OR gate inputs are **LOW**. When one of the windows or the door is opened, a **HIGH** is produced on that input to OR gate, and the gate output goes to **HIGH**, it then activates an alarm circuit to warn of the intrusion.

## OR Gate

HIGH = open  
LOW = closed

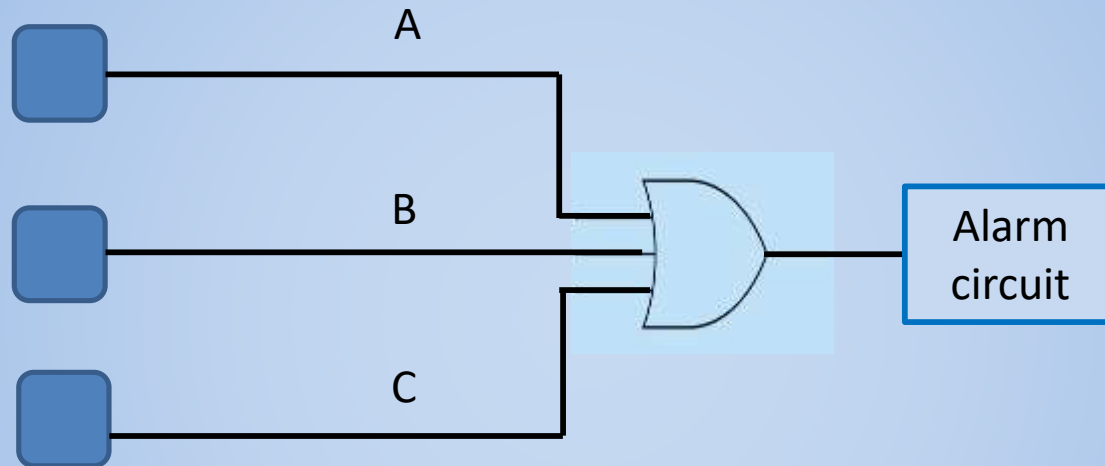

Open door / window sensors

Thank you