

$$= A \bullet A + AB$$

$$= A + AB$$

$$= A(1 + B)$$

$$= A \bullet 1$$


$$= A$$

- Rule 12 Redundancy:

$$A + \overline{A}B = (A + B)$$

A	B	$\overline{A}B$	$A + \overline{A}B$	$A + B$
0	0	0	0	0
0	1	1	1	1
1	0	0	1	1
1	1	0	1	1

↑ equal ↑

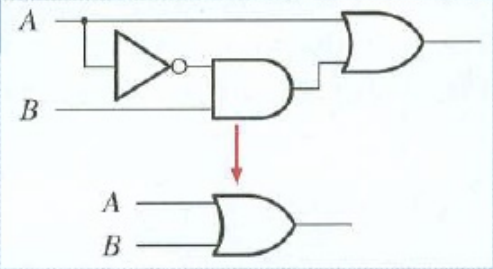

The proof:

$$\text{Left side} = A + \overline{A}B$$

$$= A + AB + \overline{A}B$$

$$= A + B(A + \overline{A})$$

$$= A + B \bullet 1$$

$$= A + B$$


$$= \text{Right side}$$

- Rule 13:

$$(A + B)(A + C) = A + BC$$

A	B	C	A + B	A + C	(A + B)(A + C)	BC	A + BC
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

↑ equal ↑

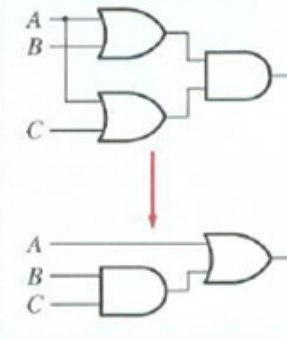

The proof:

$$\text{Left side} = (A + B)(A + C)$$

$$= AA + AC + AB + BC$$

$$= A + AC + AB + BC$$

$$= A(1 + C + B) + BC$$

$$= A \bullet 1 + BC$$

$$= A + BC$$


$$= \text{Right side}$$

■ DeMorgan's Theorem (First Theorem)

- The complement of a product of variables is equal to the sum of complemented variables.

$$\overline{AB} = \overline{A} + \overline{B}$$

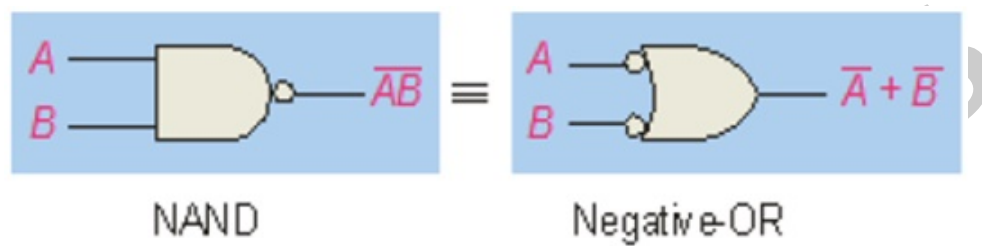- Applying DeMorgan's First Theorem to gates:




A	B	$\sim A$	$\sim B$	$\sim AB$	$\sim A + \sim B$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

■ DeMorgan's Theorem (Second Theorem)

- The complement of a sum of variables is equal to the product of complemented variables.

$$\overline{A + B} = \overline{A} \bullet \overline{B}$$

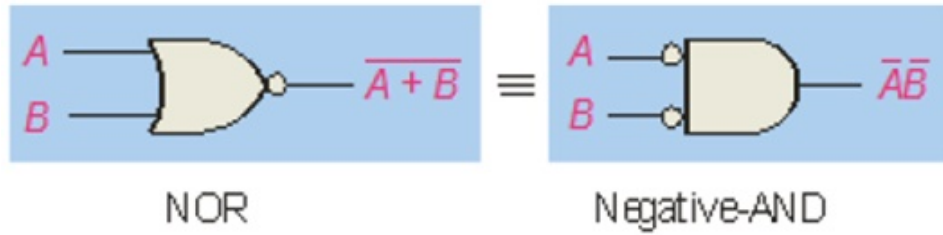- Applying DeMorgan's Second Theorem to gates:



A	B	$\sim A$	$\sim B$	$\sim(A+B)$	$\sim A \cdot \sim B$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

Example:

Apply DeMorgan's theorem to simplify the following expression.

$$X = \overline{\overline{C} + D}$$

To apply DeMorgan's theorem to the above expression, we can break the over-bar that covering both terms and change the sign between them as follows:

$$X = \overline{\overline{C}} \cdot \overline{D}$$

$$X = C \cdot \overline{D}$$

Example:

Simplify the following expression:

$$\begin{aligned}
 Y &= (A + B)(A + \overline{B}) \\
 &= AA + A\overline{B} + AB + B\overline{B} \\
 &= A + A(\overline{B} + B) \\
 &= A + A \\
 &= A
 \end{aligned}$$

Or

$$\begin{aligned}Y &= AA + A\overline{B} + AB + B\overline{B} \\&= AA + A\overline{B} + AB \\&= A + A\overline{B} + AB \\&= A(1 + \overline{B} + B) \\&= A \bullet 1 \\&= A\end{aligned}$$

Example:

$$\begin{aligned}Y &= ABC + A\overline{B}C + AB\overline{C} \\&= AB(C + \overline{C}) + A\overline{B}C \\&= AB + A\overline{B}C \\&= A(B + \overline{B}C) \\&= A(B + C)\end{aligned}$$

Example:

$$\begin{aligned}Y &= ABC + A\overline{B} (\overline{A} \overline{C}) \\&= ABC + A\overline{B} (\overline{\overline{A}} + \overline{\overline{C}}) \\&= ABC + A\overline{B} (A + C) \\&= ABC + A\overline{B} + A\overline{B}C \\&= AC(B + \overline{B}) + A\overline{B} \\&= AC + A\overline{B} \\&= A (C + \overline{B})\end{aligned}$$

- Determine if the following equation is valid (Derived from the truth table)

$$\overline{X1} \overline{X3} + X2 X3 + X1 \overline{X2} = \overline{X1} X2 + X1 X3 + \overline{X2} \overline{X3}$$

Left-Hand Side (LHS)

Row number	x_1	x_2	x_3	$\overline{x_1} \overline{x_3}$	$x_2 x_3$	$x_1 \overline{x_2}$	f
0	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
2	0	1	0	1	0	0	1
3	0	1	1	0	1	0	1
4	1	0	0	0	0	1	1
5	1	0	1	0	0	1	1
6	1	1	0	0	0	0	0
7	1	1	1	0	1	0	1

Right-Hand Side (RHS)

Row number	x_1	x_2	x_3	$\overline{x_1} x_2$	$x_1 x_3$	$\overline{x_2} \overline{x_3}$	f
0	0	0	0	0	0	1	1
1	0	0	1	0	0	0	0
2	0	1	0	1	0	0	1
3	0	1	1	1	0	0	1
4	1	0	0	0	0	1	1
5	1	0	1	0	1	0	1
6	1	1	0	0	0	0	0
7	1	1	1	0	1	0	1

$$\underbrace{\bar{x}_1\bar{x}_3 + x_2x_3 + x_1\bar{x}_2}_{\text{LHS}} \stackrel{?}{=} \underbrace{\bar{x}_1x_2 + x_1x_3 + \bar{x}_2\bar{x}_3}_{\text{RHS}}$$

f		f	
1		1	
0		0	
1		1	
1		1	
1		1	
1		1	
0		0	
1		1	

■ Sum of Product (SOP) and Product of Sum (POS) forms

• Sum of Product (SOP)

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$F = A'B'C + A'BC + AB'C + ABC' + ABC$$

minterm

$$F' = A'B'C' + A'BC' + AB'C'$$

• Product of Sum (POS)

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$F = (A + B + C)(A + B' + C)(A' + B + C)$$


maxterm

$$F' = (A+B+C')(A+B'+C')(A'+B+C')(A'+B'+C)(A'+B'+C')$$

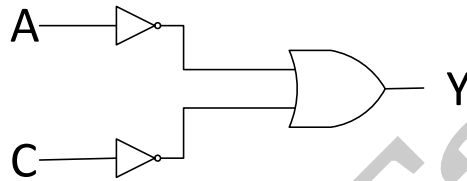Example:

Simplify the following expression, then draw the logic circuit after simplification.

$$\begin{aligned} Y &= \overline{A+B} + \overline{ABC} + \overline{AB} \\ &= \overline{A} \overline{B} + \overline{A} + \overline{B} + \overline{C} + \overline{A} + \overline{B} \\ &= \overline{A}(\overline{B} + 1 + 1) + (\overline{B} + \overline{C}) + \overline{C} \\ &= \overline{A} + \overline{C} \end{aligned}$$




Example:

For the given truth table simplify and draw the circuit before and after simplification.


A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$\begin{aligned}Y &= \overline{A}B\overline{C} + \overline{A}BC + AB\overline{C} + ABC \\&= \overline{A}B(\overline{C} + C) + AB(\overline{C} + C) \\&= \overline{A}B + AB \\&= B(\overline{A} + A) \\&= B\end{aligned}$$

- The circuit after simplification:

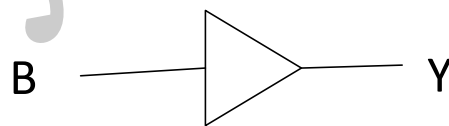

- The circuit before simplification:

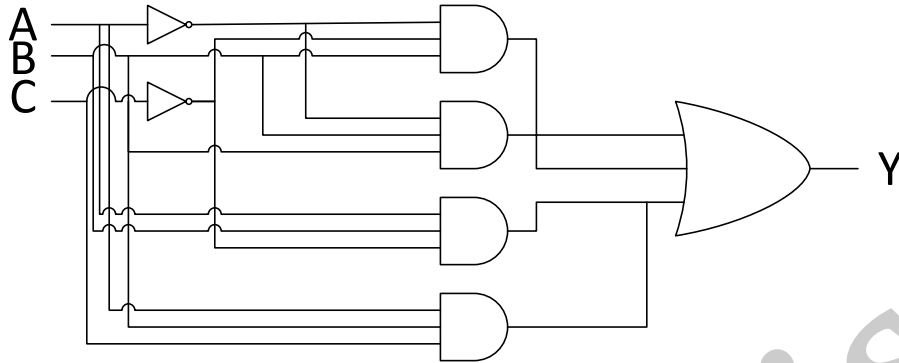

Exercise:

Design a logic circuit with three inputs variables (A, B, C) that will produce a HIGH ("1") output if the input is Odd number?

Exercise:

Write the equation (s) of the following logic circuit:

