

# Logical Design Lectures

Dr. Faris Llwaah and Eman Abdulaziz

January 25, 2020

## Lecture 8 – D & J-K & T Flip Flop & Counters Circuits

- D - Flip Flop

The *D*-type flip-flop is a modification of the **Set/Reset** flip-flop by adding an inverter to prevent the *S* and *R* inputs from being at the same logic level. In fact the *D*– Flip Flop is to a large extent of the clocked flip-flops as it ensures that inputs *S* and *R* are never equal to one logic (0 or 1) at the same time. The D-type flip flop is constructed from a gated *SR* flip-flop with an inverter added between the *S* and the *R* inputs to allow for a single D (Data) input as shown in the figure 1.

 


Figure 1:  $D - FF$  using NAND gates

 


Figure 2: Block Diagram of D FF

CP	D	Q	State
0	0	0	No change
0	1	1	No change
1	0	0	Reset
1	1	1	Set

- When  $CP = 0$ , the output of NAND gates in First-line are logic 1, and the circuit can not change state, regardless of the value of  $D$ .
- When  $CP = 1$  the state takes value as follows:
  - 1– if  $D = 1 \rightarrow$  output of gate 3 is 0 and gate 4 is 1, so the output of gate 1 is at logic 1 and  $Q = 1$
  - 2– if  $D = 0 \rightarrow$  output of gate 3 is 1 and output of gate 4 is 0, with this output of gate 1 is at logic 0 and output of gate 2 is at logic 1 then  $Q = 0$

### • J-K - Flip Flop

The  $JK$  flip flop is an improvement on the  $SR$  flip flop where  $S = R = 1$  is not a problem.

- The  $JK$  is an improvement of the  $RS$  Flip flop.
- The problem of indeterminate state in  $RS$  flip flop solved in  $JK$  flip flop.
- The  $JK$  inputs behave like  $RS$  flip flop to Set or Reset.
- When both inputs of  $JK$  are equal to 1, the  $FF$  switches to complement state, that is, if  $Q = 0$ , it switches to  $Q = 1$  and vice-versa.
- This condition can be written as  $Q_{n+1} = \overline{Q_n}$ , where  $Q_{n+1} = next\ state$ ,  $Q_n = present\ state$ .

 


Figure 3: Clocked JK Flip Flop

 


Figure 4: Block Diagram of JK Flip Flop

$Q_n$	J	K	$Q_{n+1}$	State
0	0	0	0	No change
0	0	1	0	Reset
0	1	0	1	Set
0	1	1	1	Complement $Q_n+1$
1	0	0	1	No change
1	0	1	0	Reset
1	1	0	1	Set
1	1	1	0	Complemen $Q_n+1$

- When  $J = K = 0$ , the flip flop remains in No change state, however  $Q_{n+1} = Q_n$ .
- When  $K = 1, J = 0$ , the flip flop in Reset state i.e.  $Q = 0$ .
- When  $K = 0, J = 1$ , the flip flop in Set state i.e.  $Q = 1$ .
- when  $J = K = 1$ , the flip flop will be in Toggling state, i.e.  $Q_{n+1} = \overline{Q_n}$ . However for repeated CP, the output will turn ON, OFF, ON, OFF and so on.
- **T - Flip Flop**

T flip flop is obtained from the  $JK$  flip flop where J and K inputs are connected together and given to the T input. As shown in the following circuit.

 


Figure 5: Logic circuit of T Flip Flop

Input	Outputs	
	Present State	Next State
T	$Q_n$	$Q_{n+1}$
0	0	0
0	1	1
1	0	1
1	1	0

Figure 6: Truth table of T Flip Flop

- **The applications of Flip Flop**

1– Parallel data storage. A common requirement in digital system is to take several bits of data on parallel lines and store them simultaneously in a group of flip flops.

- Each of the four parallel data lines are connected to the D input/output of a flip flop.
- The clock input/output of all flip flops are connected to a common clock i/ps, so that each FF is triggered at the same time.
- In this example a +ve edge triggered FF is used.
- Also the asynchronous i/ps are connected to a common  $\overline{CLR}$  line which Reset all FFs.
- A group of FFs used for data storage are called registers.

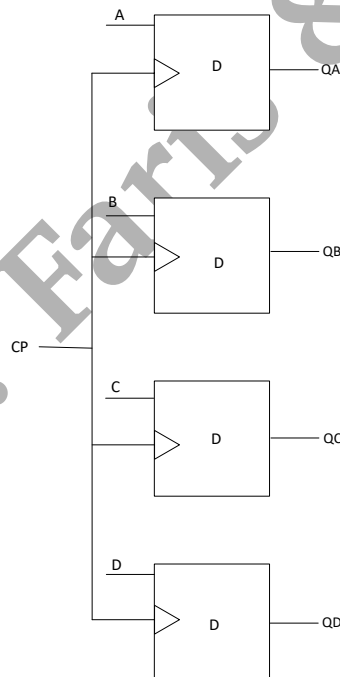


Figure 7: Parallel in Parallel out register