
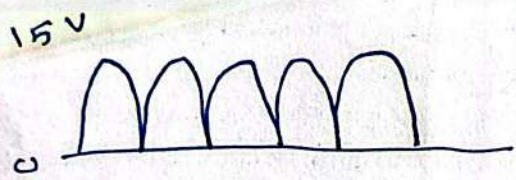
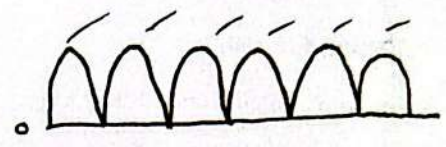






-2.3:- Full-wave Rectifier

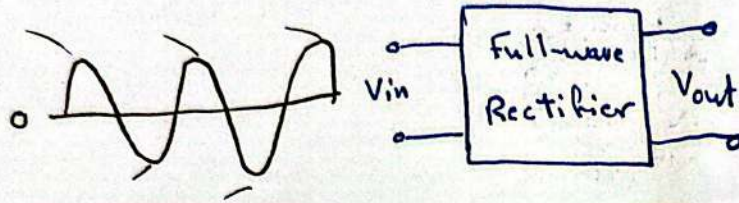


$$V_{dc} = V_{AVG} = \frac{2V_p}{\pi}$$

$$V_{dc} = V_{AVG} = \frac{2V_p}{\pi} = \frac{2(15V)}{\pi} = 9.55V$$

- 2-3.1 Full-wave Bridge Rectifier:

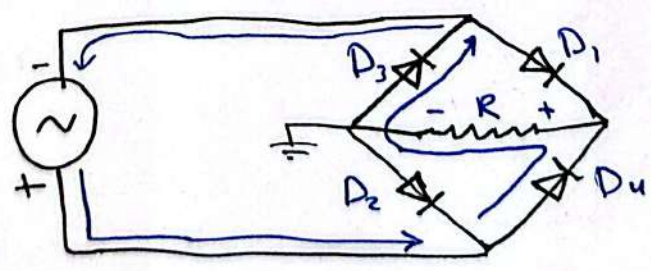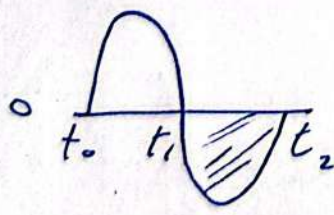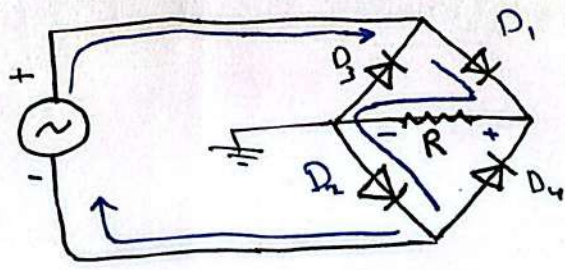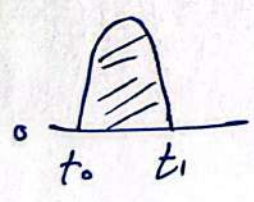

①
Bridge output voltage.

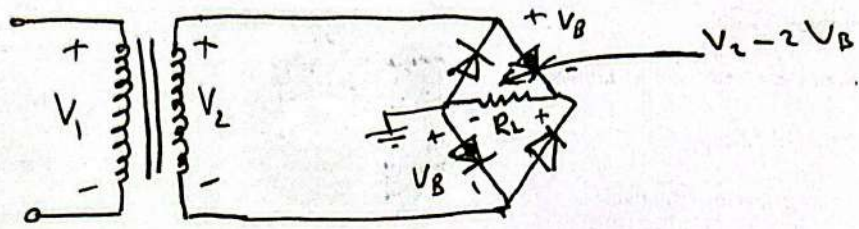


$$V_{out} = V_2 - 2V_B$$

Peak Inverse Voltage (PIV) = V_{out}

ایہ چیز سب سے زیادہ

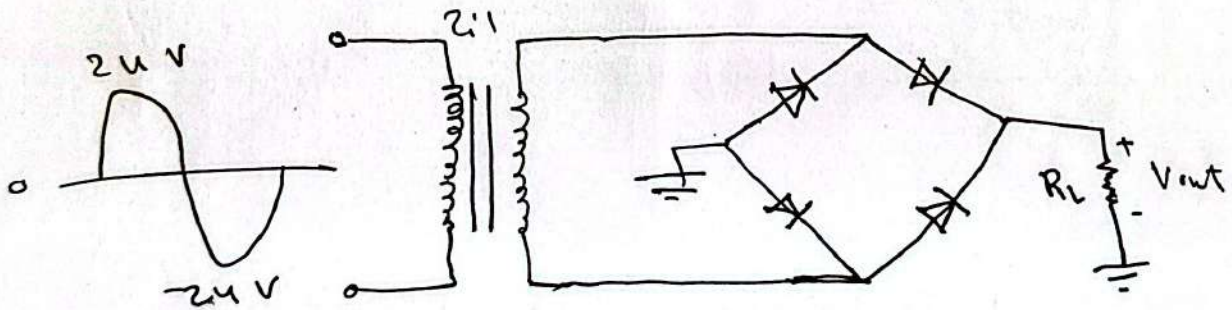ex) Determine the output voltage for the bridge rectifier. what minimum PIV rating is required for the silicon diodes?



$$V_{p(out)} = V_2 - 2V_B$$

$$= \frac{1}{2} V_{p(in)} - 2V_B$$


$$= \frac{1}{2} (24V) - 1.4V = 12 - 1.4 = 10.6V$$

PIV for each diode

$$PIV = V_{p(out)} = 10.6V + 0.7V = 11.3$$

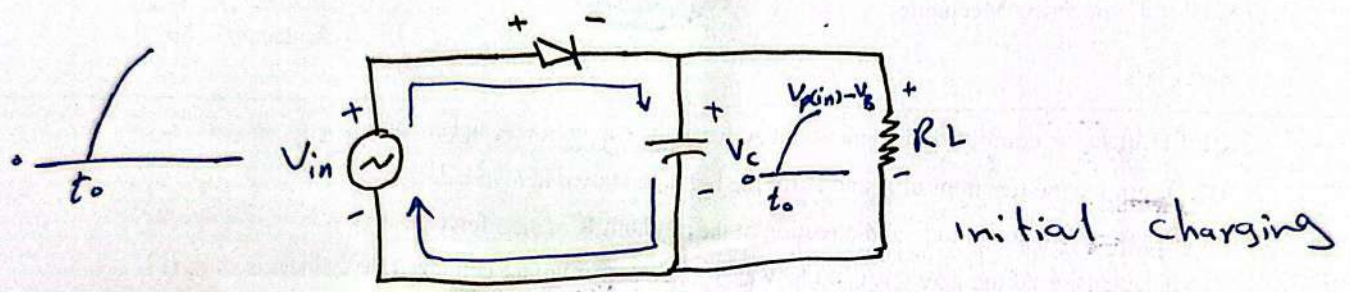
2-4 Capacitor-Input Filter (12)

* During the positive first quarter cycle of the input. The diode is forward-biased, allowing the capacitor to charge to v_i with the diode drop of the input peak.



* when the input begins to decrease below its peak, the capacitor retains its charge and the diode becomes reverse-biased.

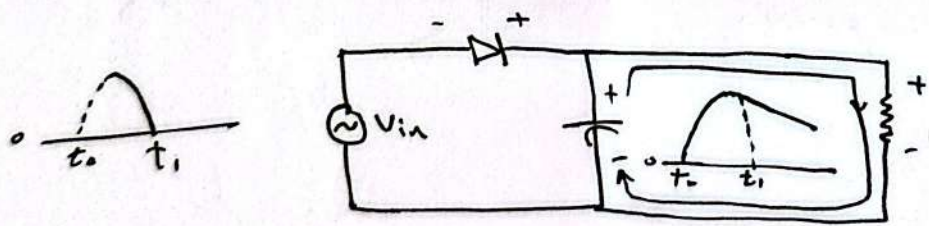During the remaining part of the cycle, the capacitor can discharge only through the load resistance at a rate determined by $R_L C$ time constant. The larger the time constant, the less the capacitor will discharge.



Ripple :-

The capacitor quickly charges at the beginning of ~~ac~~ a cycle and slowly ~~dis~~ discharges after the positive peak (when the diode is reverse-biased). The variation in the output voltage due to the charging and discharging is called the ripple.




Half-wave ripple voltage


The ripple factor is an indication of the effectiveness of the filter and is defined as

$$r = \frac{V_r}{V_{dc}}$$

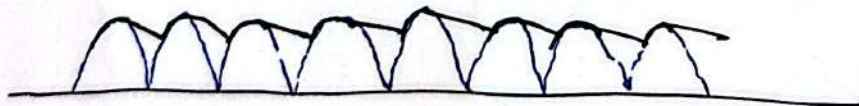where V_r is the rms ripple voltage and V_{dc} is the dc (average) value of the filter's output voltage.



full-wave ripple voltage -

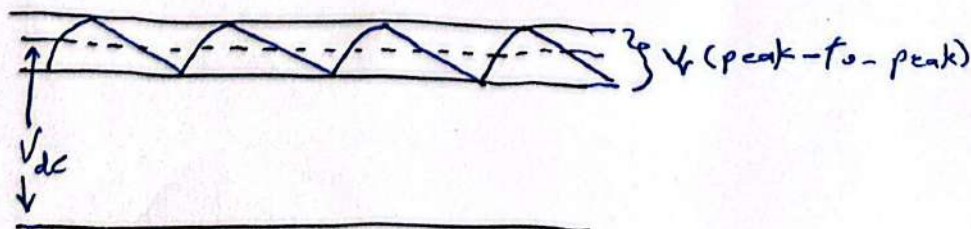

(14)


For a full-wave rectifier

$$V_{dc} = \left(1 - \frac{0.00417}{RLC}\right) V_{p(in)}$$

$$V_r = \frac{0.0024}{RLC} V_{p(in)}$$

where $V_{p(in)}$ is the peak rectified voltage applied to the filter.

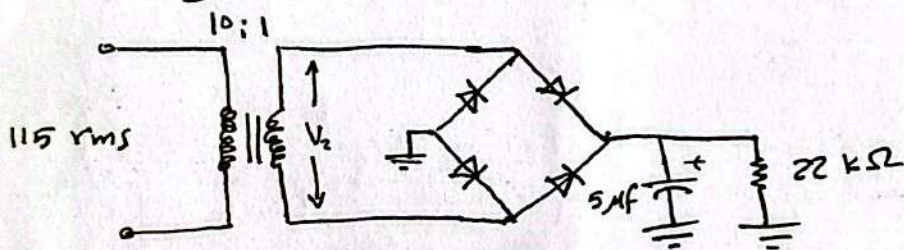ex) Determine the ripple factor for the filtered bridge rectifier



Solution The peak primary voltage is

$$V_{p1} = (1.414) 115 \text{ V} \\ = 162.6 \text{ V}$$

$$\frac{V_p}{\sqrt{2}} = V_{rms}$$

The peak secondary voltage is

$$V_{p2} = \left(\frac{1}{10}\right) 162.6 \text{ V} = 16.26 \text{ V}$$

The peak full-wave rectified voltage at the filter input is

$$V_{p(in)} = V_{p2} - 2V_B = 16.26 \text{ V} - 1.4 \text{ V} \\ = 14.86 \text{ V}$$

(15)

The filtered dc output voltage is

$$\begin{aligned}V_{dc} &= \left(1 - \frac{0.00417}{R_{LC}}\right) V_{p(in)} \\&= \left(1 - \frac{0.00417}{\frac{22 \text{ k}\Omega}{22} (5 \mu\text{F})}\right) 14.86 \text{ V} \\&= (1 - 0.0379) 14.86 \text{ V} \\&= 14.3 \text{ V}\end{aligned}$$

The rms ripple is

$$\begin{aligned}V_r &= \frac{0.0024 V_{p(in)}}{R_{LC}} \\&= \frac{0.0024 (14.86 \text{ V})}{(22 \text{ k}\Omega)(5 \mu\text{F})} = 0.324 \text{ V}\end{aligned}$$

The ripple factor is

$$\begin{aligned}r &= \frac{V_r}{V_{dc}} = \frac{0.324 \text{ V}}{14.3} \\&= 0.0227\end{aligned}$$

The percent of ripple is 2.27%

(18)

Inductor Input Filter:-

When a choke is added to the filter input a reduction in the ripple voltage is achieved.

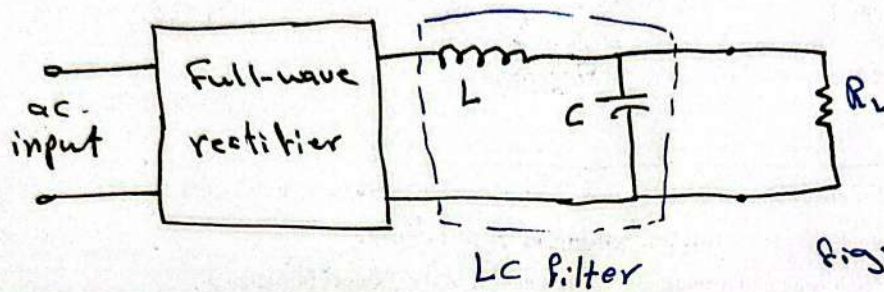


Fig: Rectifier with an LC filter

The choke has a high reactance at the ripple frequency, and the capacitive reactance is low compared to both X_L and R_L . The two reactances form an AC voltage divider.

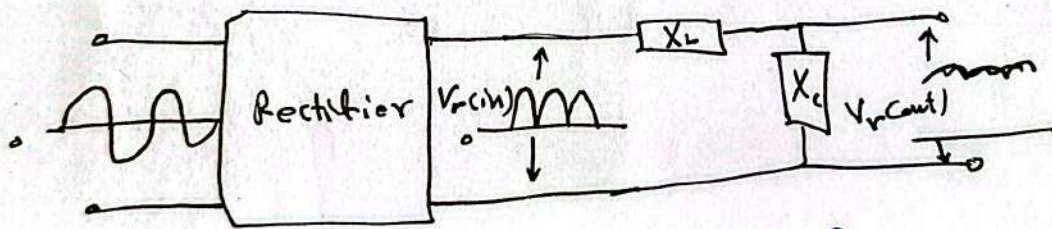


Fig:- The LC filter as it looks to the AC component

The magnitude of the ripple voltage out of the filter is determined with the voltage divider equation.

$$V_r(out) = \left(\frac{X_C}{X_L - X_C} \right) V_r(in)$$

where the amount of rms input ripple using formula ~~for~~ ^{is} the rms ripple of an unfiltered full-wave rectifier signal.

$$V_r(\text{in}) = 0.308 V_p$$

The dc output voltage is determined ~~is~~ ^{mined} as follows

$$V_{dc}(\text{out}) = \left(\frac{R_L}{R_w + R_L} \right) V_{dc}(\text{in})$$

where R_w :- winding resistance for the choke ^{coil}

R_L :- load resistance.

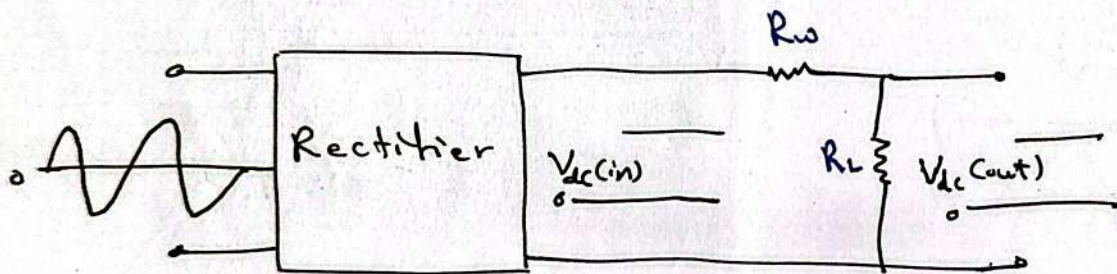
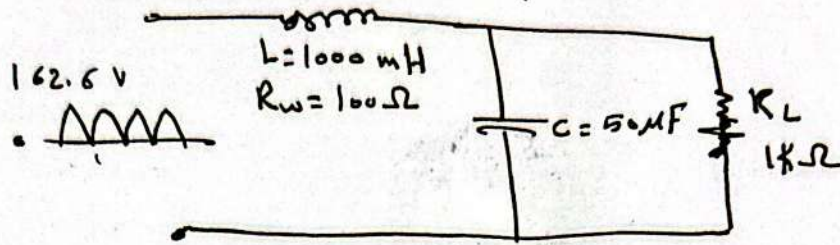


Fig:- The LC Filter as looks to the dc component.

ex) A 120 Hz full-wave rectified voltage with a peak value of 162.6 V is applied to the LC filter. Determine the filter output in terms of its dc value and the rms ripple voltage. What is the ripple factor?

(18)

Solution

$$V_{dc(in)} = V_{AVG} = \frac{2V_p}{\pi}$$

$$= \frac{2(162.6 \text{ V})}{\pi}$$

$$= 103.5 \text{ V}$$

$$V_r(in) = 0.308 V_p$$

$$= 0.308(162.6 \text{ V})$$

$$= 50.1 \text{ V}$$

$$V_{dc(out)} = \left(\frac{R_L}{R_w + R_L} \right) V_{dc(in)}$$

$$= \left(\frac{1 \text{ k}\Omega}{1.1 \text{ k}\Omega} \right) 103.5 \text{ V} = 94.1 \text{ V}$$

$$X_L = 2\pi fL = 2\pi(120 \text{ Hz})(1000 \text{ mH}) = 754 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(120 \text{ Hz})(50 \mu\text{F})} = 26.5 \Omega$$

$$V_r(out) = \left(\frac{X_C}{|X_L - X_C|} \right) V_r(in) = \left(\frac{26.5 \Omega}{|754 \Omega - 26.5 \Omega|} \right) 50.1 \text{ V}$$

$$= 1.82 \text{ V rms}$$

The ripple factor is

$$r = \frac{V_r(out)}{V_{dc}}$$

$$= \frac{1.82 \text{ V}}{94.1 \text{ V}}$$

$$= 0.0193$$

26 / Diode Clipper and Clamper circuits :-

Diode circuits are sometimes used to clip off portions of signal voltages above or below certain levels. These circuits are called clipping. Another type of diode circuit is used to restore a dc level to an electrical signal; these are called clammers.

- Clippers

a diode circuit that clips the positive part of the input voltage. As the input signal goes positive, the diode becomes forward-biased. Since the cathode is at ground potential (0V), the anode cannot exceed 0.7V (assuming silicon). So point A is clipped at +0.7V when the input exceeds this value.

When the input goes back below 0.7V, the diode reverse-biases and appears as an open. The output voltage looks like the negative part of the input, but with a magnitude determined by the R_s and R_L voltage divider as follows:

$$V_{out} = \left(\frac{R_L}{R_s + R_L} \right) V_{in}$$

(20)

if R_s is small compared to R_L , The $V_{out} = V_{in}$.

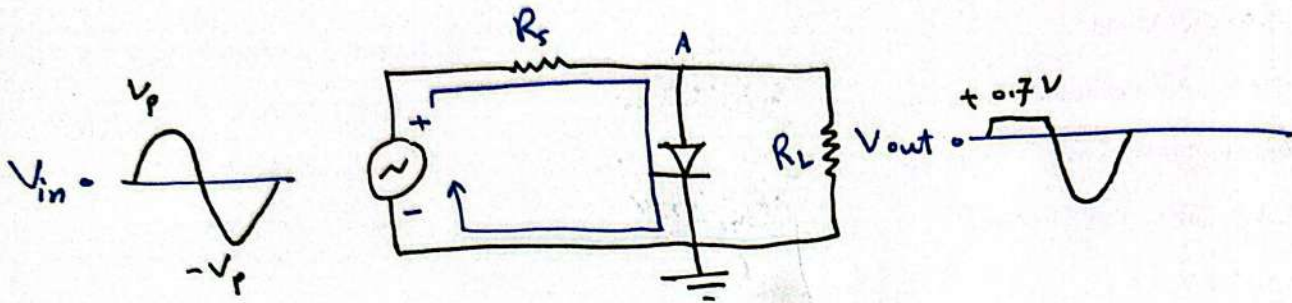


fig: clipping of positive alternation

Now, turn the diode around, and the negative part of input is clipped off. When the diode is forward-biased during the negative part of the input, point A is held at $-0.7V$ by the diode drop. When the input goes above $-0.7V$, the diode is no longer forward-biased and voltage appears across R_L proportional to the input.


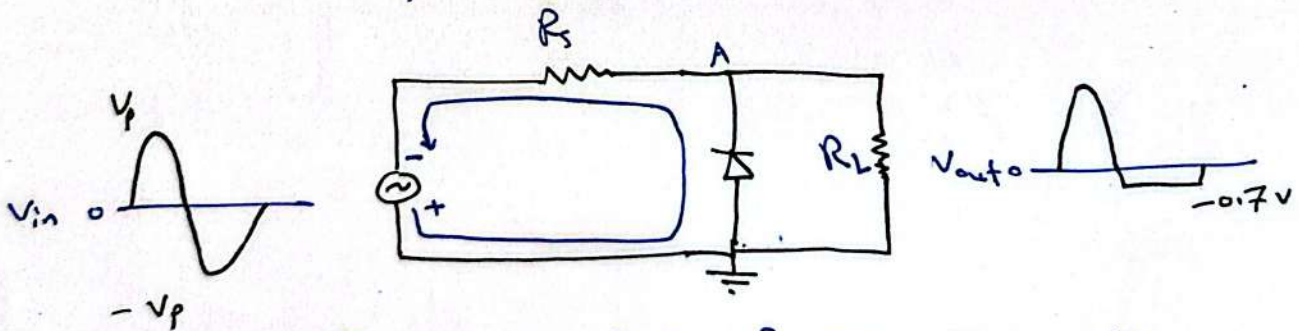


fig:- clipping of the negative alternation.

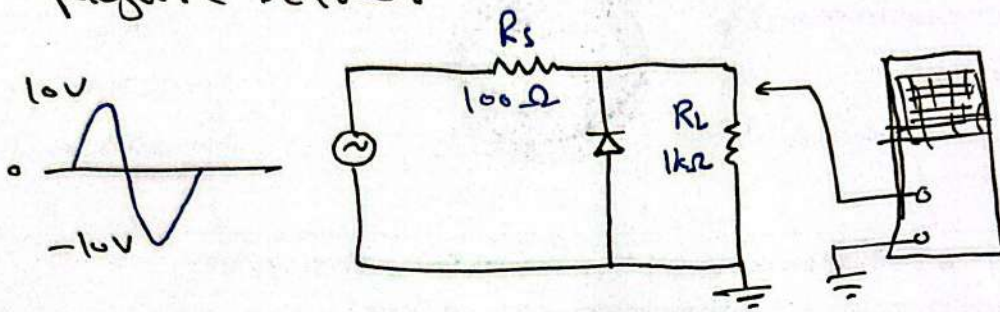Ex) what would you expect to see displayed on an oscilloscope connected as shown in figure below:





Solution

The diode conducts when the input voltage goes below -0.7 V .

So, we have negative clipper with a peak output voltage determined by the following equation


$$\begin{aligned}
 V_{p(\text{out})} &= \left(\frac{R_L}{R_s + R_L} \right) V_p(\text{in}) \\
 &= \left(\frac{1\text{ k}\Omega}{1.1\text{ k}\Omega} \right) 10\text{ V} \\
 &= 9.09\text{ V}
 \end{aligned}$$

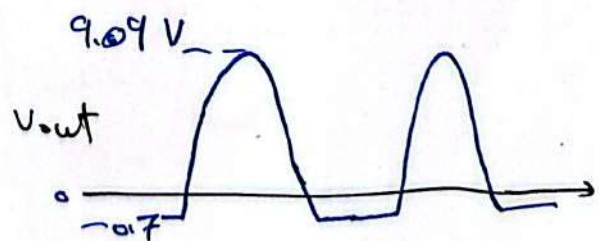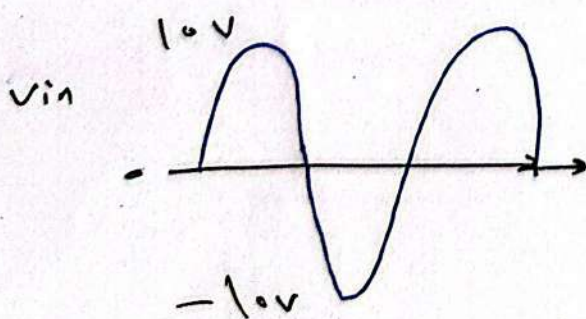The scope will display an output waveform as




22.
 - Adjustment of The clipping level.


Positively biased clipper

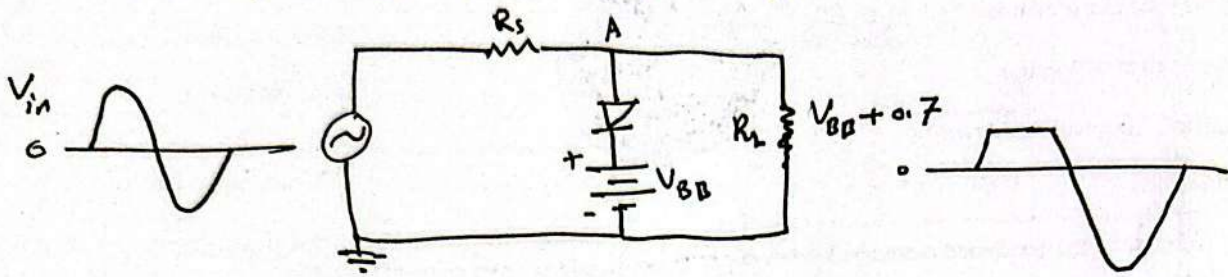


Positive clipper with variable bias.

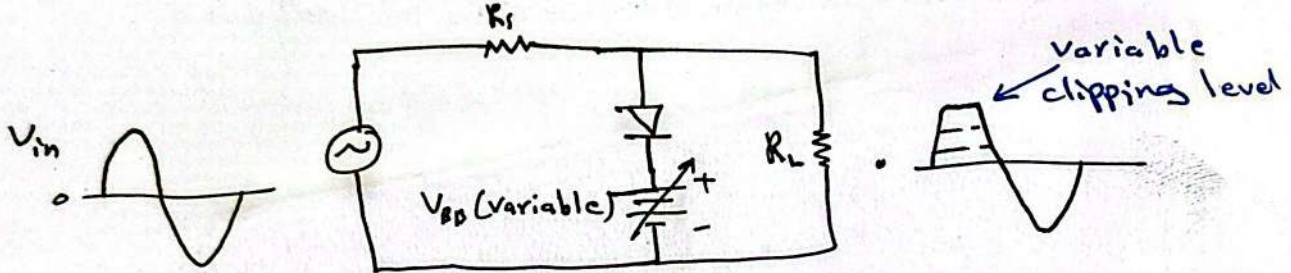

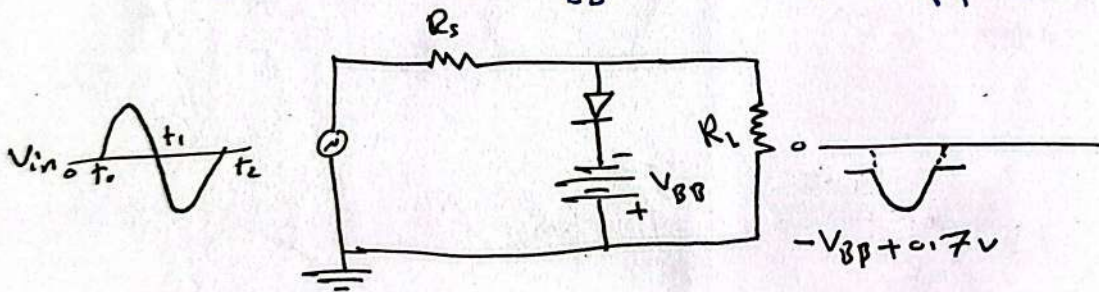
If The polarity of The bias voltage is reversed, voltages above $-V_{BB} + 0.7$ are clipped.



Negative biased clipper

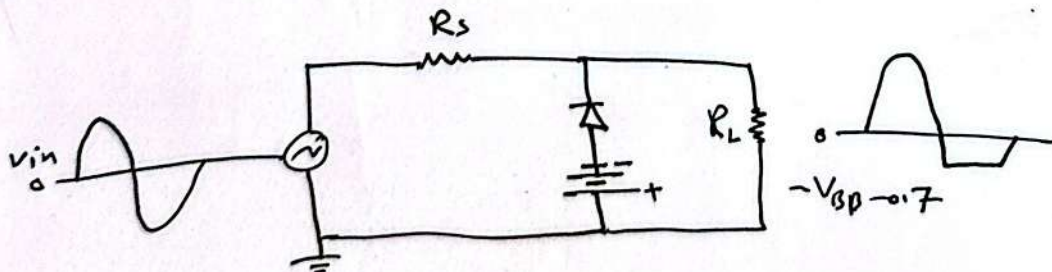

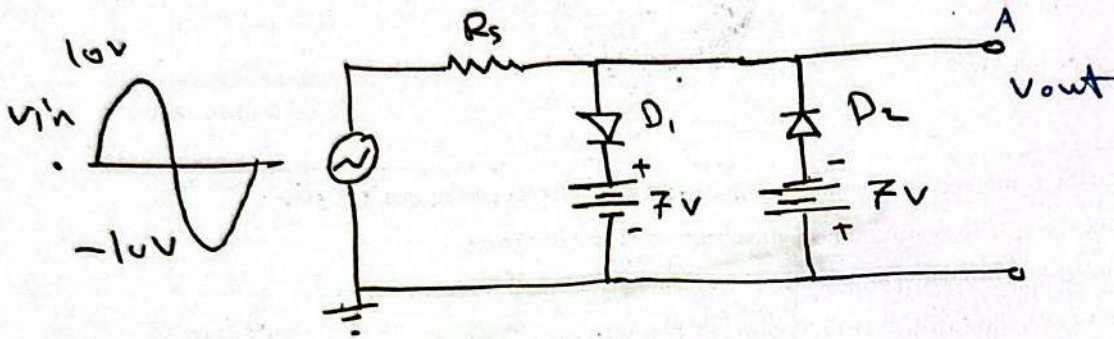8a) Determine the output waveform of the following circuit combining a positive-biased clipper with a negative-biased clipper.



Solution when the voltage at point A reaches $+7.7\text{ V}$, diode D_1 conducts and clips the waveform at $+7.7\text{ V}$. Diode D_2 does not conduct until the voltage reaches -7.7 V .

