
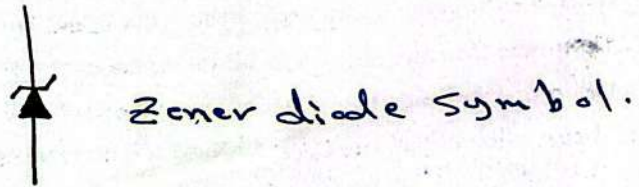


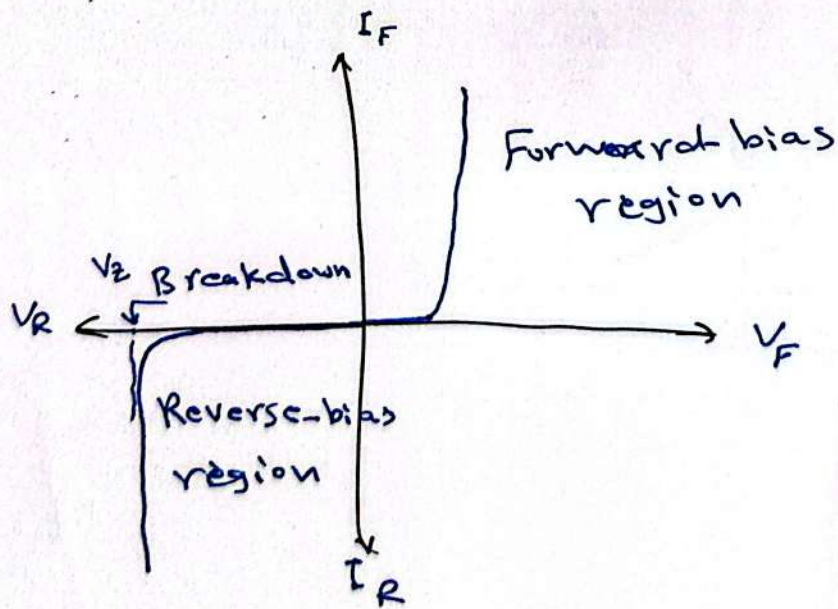3-1 Zener Diodes:-

The Zener diode is used for voltage regulation ^{reg. pt} and, like the rectifier diode, is important in many power-supply applications. The schematic symbol is shown in Figure below.




The Zener is a silicon pn junction device that differs from the rectifier diode in that it is optimized for operation in the reverse breakdown region. The breakdown voltage of a Zener diode is set by carefully controlling the doping level during manufacture. This volt-ampere characteristic is




Zener Breakdown:-

The breakdown voltage (V_Z). Zener diodes with breakdown voltage of less than approximately 5V operate predominately in Zener breakdown. Those with breakdown voltage greater than approximately 5V operate predominately in avalanche breakdown. Both types, however, are called Zener diodes. Zeners are commercially available with breakdown voltages of 1.8V to 200V.


- Breakdown Characteristics

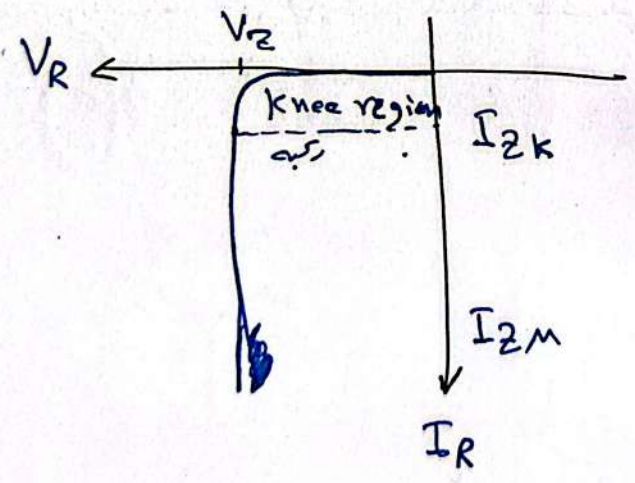


Zener Equivalent Circuit

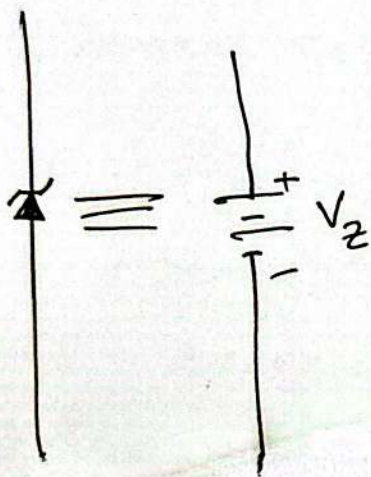

A. Ideal

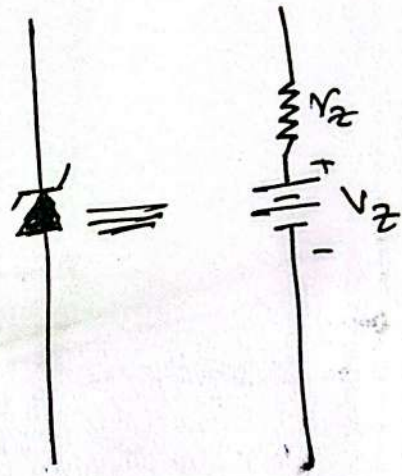

B. practical

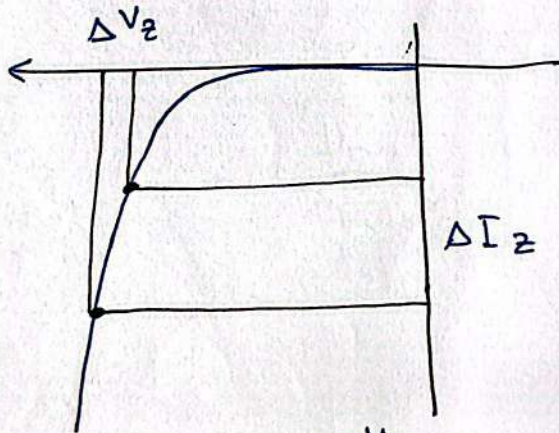

C. $r_z = \frac{\Delta V_z}{\Delta I_z}$

fig: Zener equivalent circuit.


The resistance of Zener is

$$r_z = \frac{\Delta V_z}{\Delta I_z}$$

ex) 1) A certain diode exhibits a 50 mV change in V_z for 2 mA change in I_z . what is the zener resistance

Solu $r_z = \frac{\Delta V_z}{\Delta I_z} = \frac{50 \text{ mV}}{2 \text{ mA}} = 25 \Omega$

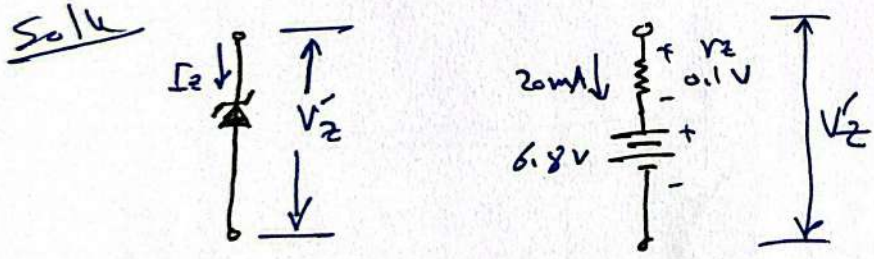ex) 2) A 6.8 V zener diode has resistance of 5 Ω what is the actual voltage across its terminals when the current is 20 mA?



$V_z' = V_z + I_z r_z$
 $= 6.8 \text{ V} + (20 \text{ mA})(5 \Omega)$
 $= 6.8 \text{ V} + 100 \text{ mV}$
 $= 6.9 \text{ V}$


Zener voltage Regulation

1- Regulation with a Varying Input Voltage


Zener diodes are widely used for voltage regulation.

Figure below shows how a Zener diode can be used to regulate a varying dc voltage. This is called input or line regulation.

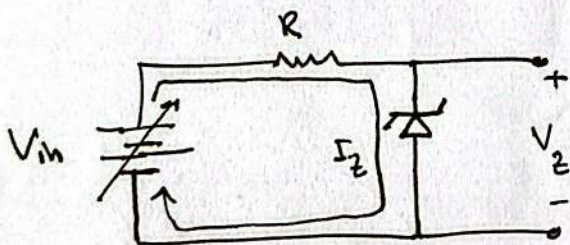However, as V_{in} changes, I_Z will change proportionally so that the limitations on the input variation are set. The minimum and maximum current values with which the Zener can operate. R is the series current-limiting resistor.



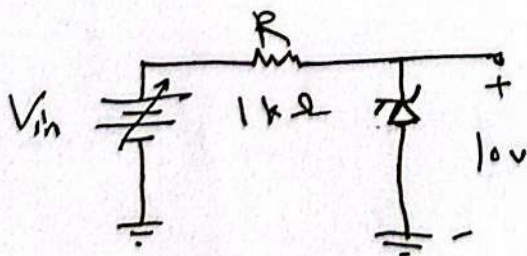ex) Suppose that the Zener diode in figure below can ~~maintain~~ ^{maintain} regulation over a range of current values from 4mA to 40mA.



Sol) for minimum current

$$V_R = (4\text{mA})(1\text{k}\Omega) = 4\text{V}$$

since $V_R = V_{in} - V_Z \Rightarrow V_{in} = V_R + V_Z$

$$\therefore V_{in} = 4\text{V} + 10\text{V} = 14\text{V}$$


for the maximum current

$$V_R = (40\text{mA})(1\text{k}\Omega) = 40\text{V}$$


$$V_{in} = 40\text{V} + 10\text{V} = 50\text{V}$$

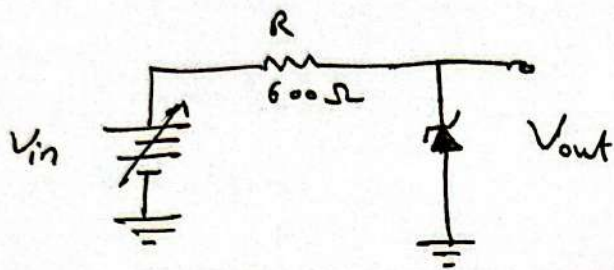(24)

ex) Determine The minimum and The maximum input voltages which can be regulated by The Zener diode.
 Assume $I_{zk} = 1 \text{ mA}$, $I_{zm} = 15 \text{ mA}$, $V_z = 5.1 \text{ V}$ and $r_z = 10 \Omega$



Solution:- The equivalent circuit is -

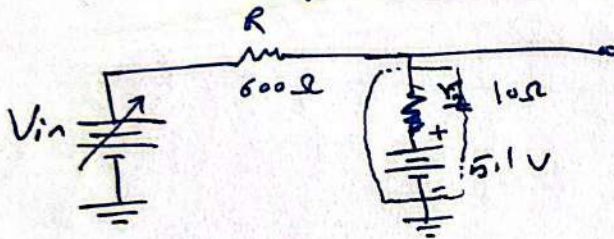

At $I_{zk} = 1 \text{ mA}$

$$V_{out} = V_z + I_{zk} r_z$$

$$= 5.1 \text{ V} + (1 \text{ mA})(10 \Omega)$$

$$= 5.11 \text{ V}$$

Therefore $V_{in(\min)} = I_{zk} R + V_{out}$

$$V_{in(\min)} = (1 \text{ mA})(600 \Omega) + 5.11 \text{ V}$$

$$= 5.71 \text{ V}$$

At $I_{zm} = 15 \text{ mA}$, The output voltage is

$$V_{out} = V_z + I_{zm} r_z$$

$$= 5.1 \text{ V} + (15 \text{ mA})(10 \Omega)$$

$$= 5.1 \text{ V} + 0.15 \text{ V}$$

$$= 5.25 \text{ V}$$

Therefore


$$V_{in(\max)} = I_{zm} R + V_{out}$$

$$= (15 \text{ mA})(600 \Omega) + 5.25 \text{ V}$$

$$= 14.25 \text{ V}$$

2- Regulation with a varying load

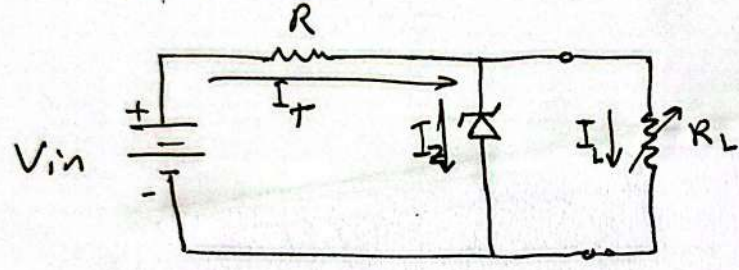The Zener diode maintains a constant voltage across R_L as long as the Zener current is greater than I_{ZK} and less than I_{ZM} . This is called load regulation.




Zener regulation with variable load.

3- No load to full load

- * when the output terminals are open ($R_L = \infty$), the load current is zero and all of the current is through the Zener. when a load resistor is connected, part of the ~~load~~ total current is through the Zener and part through R_L .
- * As R_L is decreased, I_L goes up and I_Z goes down. The Zener diode continues to regulate ~~until~~ ^{until} I_Z reaches its minimum value I_{ZK} . At this point the load current is maximum.

(31)

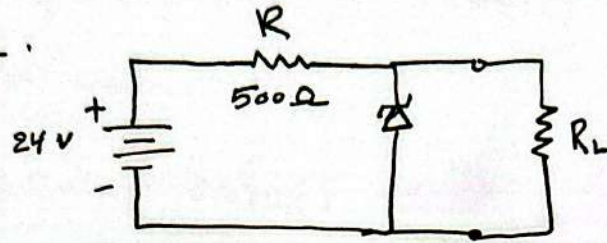Example: Determine the minimum and the maximum load currents for which the Zener diode will maintain regulation. What is the minimum R_L that can be used? $V_Z = 12\text{V}$, $I_{ZK} = 3\text{mA}$, and $I_{ZM} = 90\text{mA}$. Assume $r_Z = 0\ \Omega$.



Solution:-

When $I_L = 0\text{A}$, I_Z is maximum and equal to the total ~~current~~ circuit current I_T .

$$I_Z = \frac{V_{in} - V_Z}{R} = \frac{24\text{V} - 12\text{V}}{500\ \Omega} = 24\text{mA} = I_T$$

Since this is much less than $I_{ZM} = 90\text{mA}$ is an acceptable minimum for I_L

$$I_L(\text{min}) = 0\text{A}$$

The max. value of I_L occurs when I_Z is minimum. So we can solve for $I_L(\text{max})$ as follows:

$$\begin{aligned} I_L(\text{max}) &= I_T - I_Z(\text{min}) \\ &= 24\text{mA} - 3\text{mA} = 21\text{mA} \end{aligned}$$

The minimum value of R_L is

$$R_L = \frac{V_Z}{I_L(\text{max})} = \frac{12\text{V}}{21\text{mA}} = 571\ \Omega$$