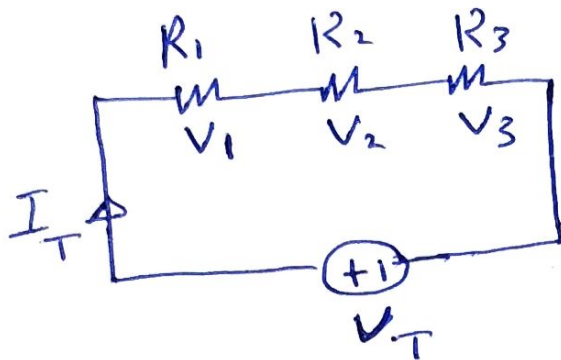


Resistance Combinations

1- Series

We have shown the equivalent resistance in Series for "N" resistor:-




$$R_{eq} = R_1 + R_2 + R_3$$

$$V_T = V_1 + V_2 + V_3$$

$$I_T = I_1 = I_2 = I_3$$

$$R_{eq} = \frac{V_T}{I_T}$$

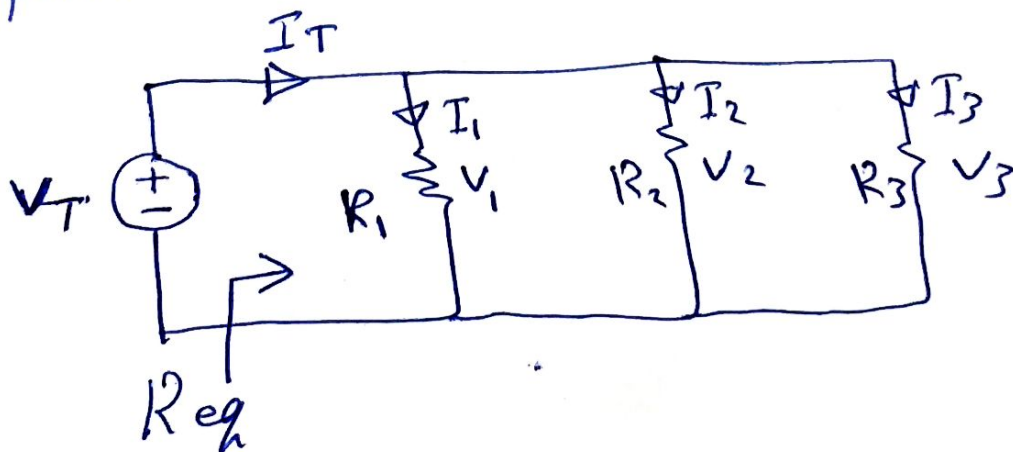2- Parallel :- The equivalent resistance for "N" parallel resistor.




$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$V_T = V_1 = V_2 = V_3$$

$$I_T = I_1 + I_2 + I_3$$

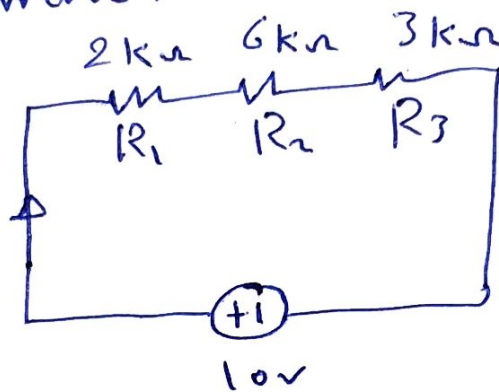Ex 1] For the circuit as shown fig. 1, find the R_{eq} and the current in circuit.



Sol:-

$$R_{eq} = R_1 + R_2 + R_3$$

$$R_{eq} = 2k + 6k + 3k$$

$$R_{eq} = 11k\Omega$$

∴ series Resistance

$$V_T = V_1 + V_2 + V_3$$

$$I_T = I_1 = I_2 = I_3$$

$$R_{eq} = \frac{V_T}{I_T} \Rightarrow I_T = \frac{V_T}{R_{eq}} = \frac{10V}{11k\Omega} = 0.9mA$$

Find the voltage in circuit.

3

$$V_1 = R_1 I_1 \Rightarrow V_1 = 2k \times 0.9m = 1.8V$$


$$V_2 = R_2 I_2 \Rightarrow V_2 = 6 \times 10^3 \times 0.9 \times 10^{-3} = 5.4V$$

$$V_3 = R_3 I_3 \Rightarrow V_3 = 3 \times 10^3 \times 0.9 \times 10^{-3} = 2.7V$$

$$V_T = V_1 + V_2 + V_3$$

$$V_T = 9.9 \approx 10V \quad \checkmark$$

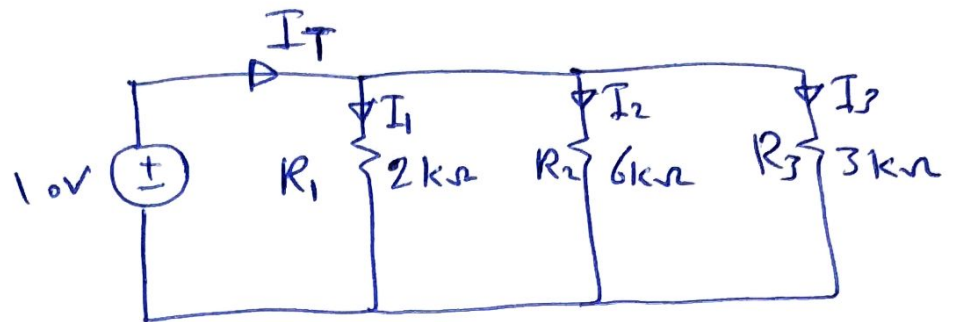EX2] For the circuit as shown in fig 2. find the R_{eq} and the current in each resistor. 4



Sol] the parallel resistance

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{2k} + \frac{1}{6k} + \frac{1}{3k}$$

$$\frac{1}{R_{eq}} = \frac{6k \times 3k + 2k \times 3k + 2k \times 6k}{2k \times 6k \times 3k} = \frac{18M + 6M + 12M}{36G}$$

or

$$\frac{1}{R_{eq}} = \frac{18 \times 10^6 + 6 \times 10^6 + 12 \times 10^6}{36 \times 10^9}$$

$$\frac{1}{R_{eq}} = \frac{36 \times 10^6}{36 \times 10^9}$$

$$R_{eq} = \frac{36 \times 10^9}{36 \times 10^6} = 1 \times 10^3 \Omega$$

$$R_{eq} = 1k\Omega$$

$$I_T = \frac{V_T}{R_{eq}} = \frac{10}{1 \times 10^3} = 10 \times 10^{-3} \text{ A}$$

5

$$I_T = 10 \text{ mA} \quad \therefore V_T = V_1 = V_2 = V_3$$

$$I_1 = \frac{V_1}{R_1} = \frac{10 \text{ V}}{2 \text{ k}\Omega} = 5 \times 10^{-3} \text{ A}$$

$$I_2 = \frac{V_2}{R_2} = \frac{10 \text{ V}}{6 \text{ k}\Omega} = \frac{10}{6} = 1.667 \times 10^{-3} \text{ A}$$

$$I_3 = \frac{V_3}{R_3} = \frac{10}{3 \text{ k}} = 3.333 \times 10^{-3} \text{ A}$$


$$I_T = I_1 + I_2 + I_3 = 10 \times 10^{-3} \text{ A} \checkmark$$

لنا كرم
صحة الكل

Inductance combinations

1 - Series

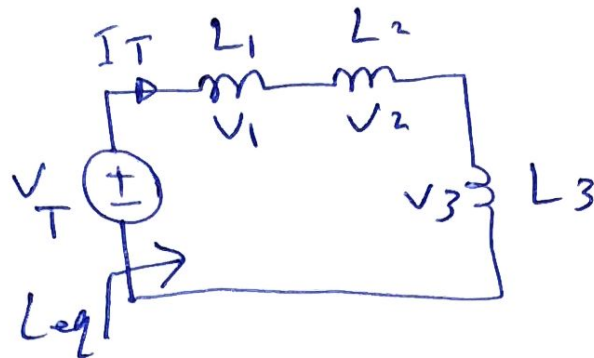We have shown the equivalent Inductance in series for 'N' Inductance :-




$$L_{eq} = L_1 + L_2 + L_3$$

$$V_T = V_1 + V_2 + V_3$$

$$I_T = I_1 = I_2 = I_3$$

2 - Parallel

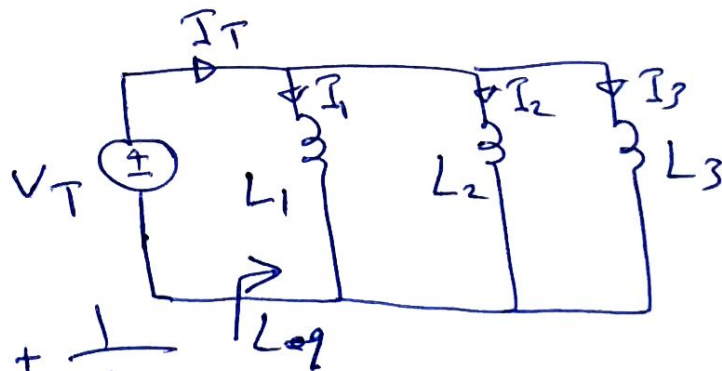

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$


$$V_T = V_1 = V_2 = V_3$$

$$I_T = I_1 + I_2 + I_3$$

Capacitor combinations

7

1 - Series

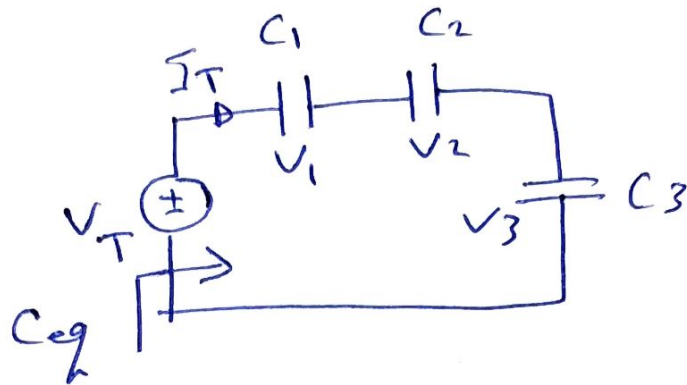


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$I_T = I_1 = I_2 = I_3$$

$$V_T = V_1 + V_2 + V_3$$

2 - Parallel

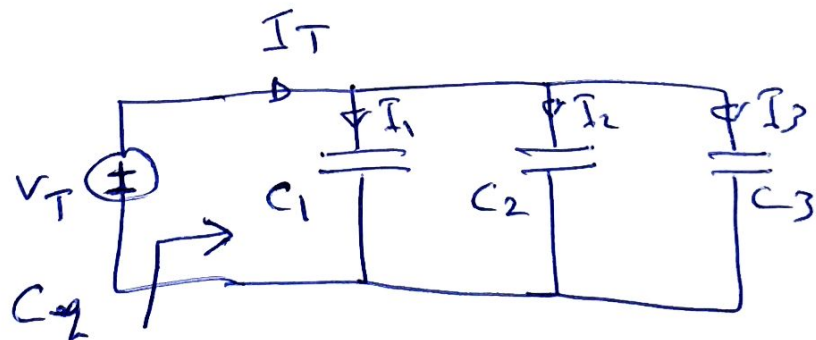


$$C_{eq} = C_1 + C_2 + C_3$$

$$V_T = V_1 = V_2 = V_3$$

$$I_T = I_1 + I_2 + I_3$$

EX3 Find the L_{eq} in fig below.

8

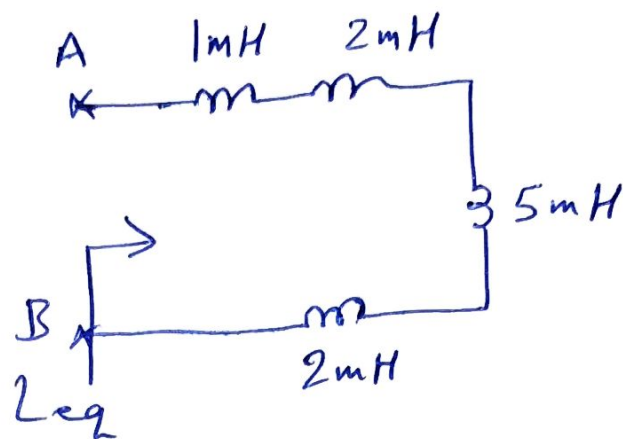

Sol)


\therefore Series

$$L_{eq} = L_1 + L_2 + L_3 + L_4$$

$$L_{eq} = 1 \times 10^{-3} + 2 \times 10^{-3} + 5 \times 10^{-3} + 2 \times 10^{-3} = 10 \times 10^{-3} \text{ H}$$

$$L_{eq} = 10 \text{ mH}$$

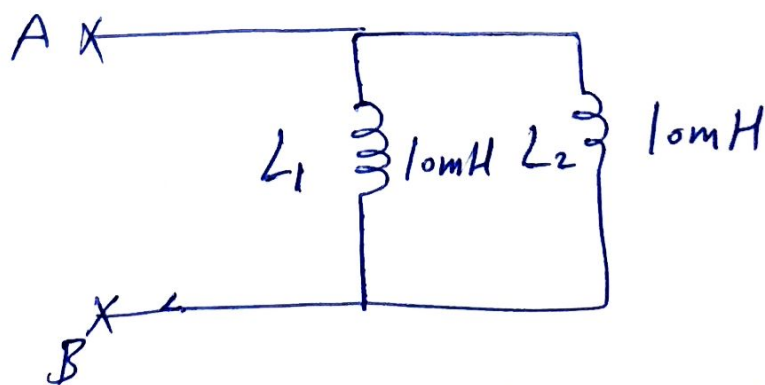EX4 Find the L_{eq} at points A and B in circuit.



Sol)


parallel

$$L_{eq} = 5 \times 10^{-3} \text{ H}$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$\frac{1}{L_{eq}} = \frac{1}{10 \times 10^{-3}} + \frac{1}{10 \times 10^{-3}} \Rightarrow$$

Ex 5) Find C_{eq} in the circuit below

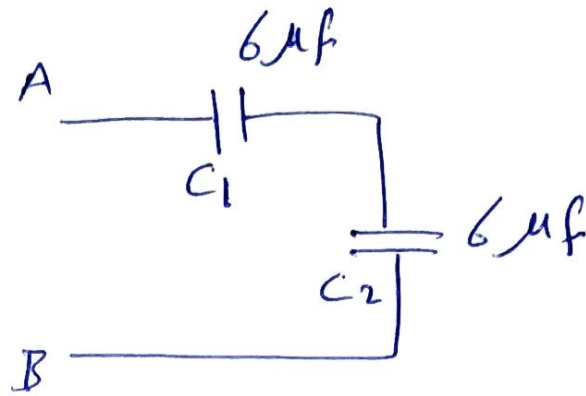


Sol)
∴ Series

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C_{eq}} = \frac{1}{6 \times 10^{-6}} + \frac{1}{6 \times 10^{-6}} = 3\mu f$$

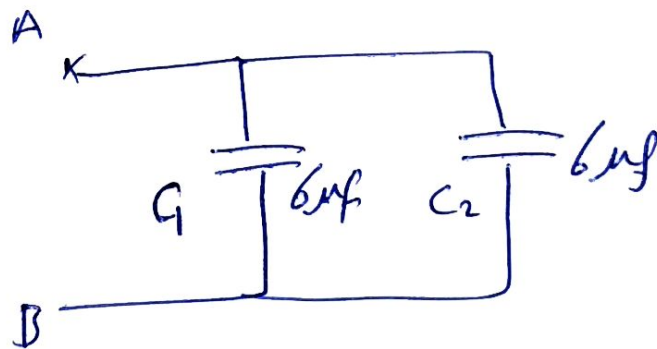Ex 6) Find the C_{eq} in the circuit below



Sol)
Parallel

$$C_{eq} = C_1 + C_2 = 6 \times 10^{-6} + 6 \times 10^{-6}$$

$$C_{eq} = 12 \times 10^{-6} \text{ F} \Rightarrow \boxed{C_{eq} = 12 \mu \text{F}}$$

Basics of electrical eng.

Course 1 contents

1. Basis of electrical engineering.
2. Ohm's Law.
3. Combination of sources.
4. Kirckhoff's Laws.
5. Resistance combinations.
6. wye-Delta transformation.
7. maxwell currents (mesh or Loop analysis).
8. Nodal analysis.
9. Source transformation.
10. Superposition theorem.
11. Thevenin theorem.
12. Norton theorem.
13. Maximum power transfer theorem.

Reference :-

Engineering circuit analysis, 7th edition, William H
Hoyt.

Electrical units

Quantity	Symbol	unit	Symbol
current	I	ampere	A
voltage	V	volt	V
Resistance	R	ohm	Ω
capacitance	C	farad	F
Inductance	L	Henry	H
power	P	watt	W
frequency	f	Hertz	Hz
conductance	G	Siemens	S
Electric charge	Q	coulomb	C
Energy	E	Joule	J

Multiples and submultiples

prefix	Symbol	Exponential format	Multiplier
Milli	m	10^{-3}	0.001
Micro	μ	10^{-6}	0.000 001
nano	n	10^{-9}	0.000 000 001
pico	p	10^{-12}	0.000 000 000 001
Kilo	k	10^3	1000
Mega	M	10^6	1 000 000
Giga	G	10^9	1 000 000 000
tera	T	10^{12}	1 000 000 000 000

Electrical Circuits

Active elements

passive elements

Sources



Loads (R, L, C)

Dependent sources

un-dependent sources

linear Loads

non-linear Loads

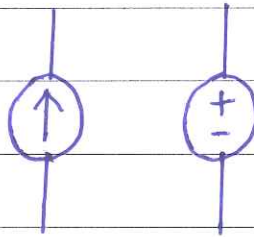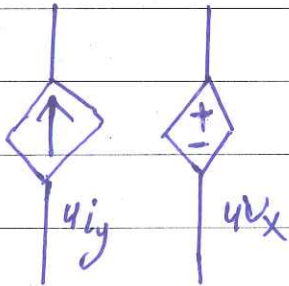

linear loads

electric current : the number of charged particles that passing a point in a conductor every second. expressed in amperes

$$1 \text{ Amp.} = 1 \text{ coulomb/second}$$

voltage : the difference in electrical charge between two points in a circuit expressed in Volts

$$1 \text{ Volt} = 1 \text{ Joule / coulomb}$$

قوة

electrical power ; is the rate at which electrical energy is converted to another form, such as motion, heat, light or an electromagnetic field.

$$P = U \times I \quad \frac{\text{J}}{\text{C}} \times \frac{\text{C}}{\text{s}} = \frac{\text{J}}{\text{s}} = \text{watt}$$

one watt is the power resulting from an energy dissipation, conversion, or storage process equivalent to one joule per second

in the resistance the energy absorbed is dissipated by the resistor in the form of heat.

$$P = V \times I \quad \text{power supplied by the sources.}$$

$$P = \frac{V^2}{R} \quad \left. \vphantom{P = \frac{V^2}{R}} \right\} \text{power dissipated}$$

OR

$$P = I^2 \times R \quad \left. \vphantom{P = I^2 \times R} \right\} \text{by the resistor.}$$

"Ohm's Law"

"قانون اوم"


Ohm's law is named for the German physicist Georg Simon ohm, who is credited with establishing the voltage - current relationship for resistance. As a result of his pioneering work, the unit of resistance bears his name.

Ohm's law states that the voltage across a resistance is directly proportional to the current flowing through it.

The resistance, measured in ohms, is the constant of proportionality between the voltage and current.

$$R = \frac{V}{I} \quad (\Omega)$$

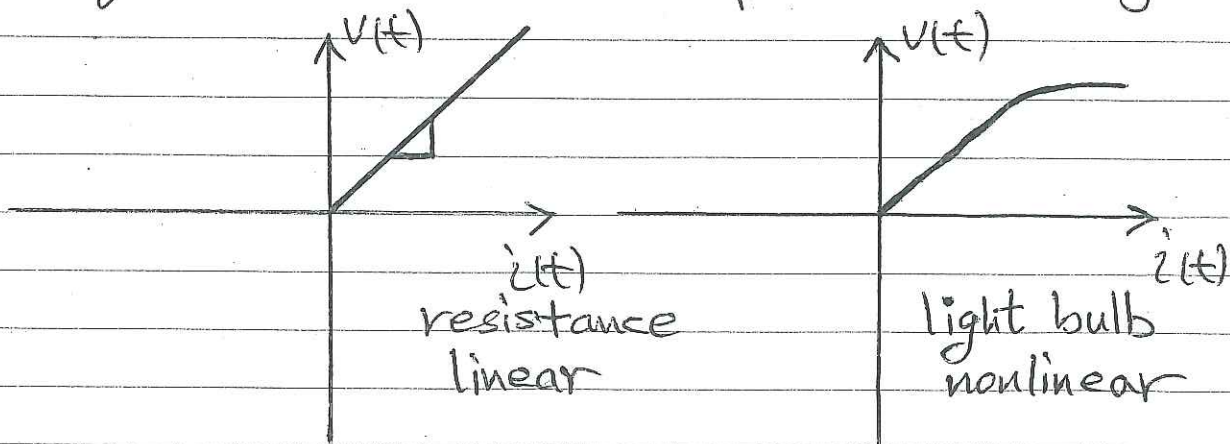In our analysis we will always assume that the resistor are linear and are thus described by a straight-line characteristic that passes through the origin, it is important that readers realize that some very useful and practical elements do exist that exhibit a nonlinear resistance characteristic; that is, the voltage - current relationship is not a straight line.



Since a resistor is a passive element, the proper current-voltage relationship is illustrated in above Fig.

The power supply to the terminals is absorbed by the resistor. Note that the charges move from higher to the lower potential as it passes through the resistor and the energy absorbed is dissipated by the resistor in the form of heat.

The instantaneous power

$$P(t) = V(t) \times i(t) \quad \text{Watt}$$

and can be written as

$$P(t) = R \times i^2(t) = \frac{V^2(t)}{R}$$

Conductance, represented by the symbol G , is another quantity with wide application in circuit analysis.

$$G = \frac{1}{R} \quad (\text{Siemens})$$

$$G = \frac{I}{V} \quad (\text{Siemens})$$

$$P(t) = \frac{i^2(t)}{G} = G V^2(t)$$

G التوصيل
Conductance


EX:- For the circuit as shown in fig., find the current in the resistance (2Ω).
 ①

Sol

$$R = \frac{V}{I}$$

$$I_R = \frac{V}{R}$$

$$I_R = \frac{12}{2} = \underline{6A}$$

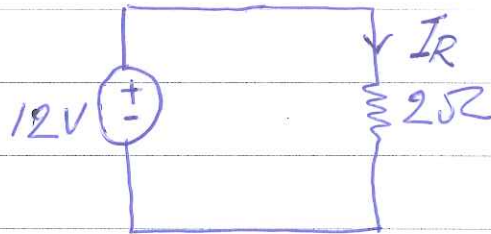


single loop circuit

EX: for the circuit as shown in fig., find the voltage across the resistance (5Ω).
 ②

Sol

$$R = \frac{V}{I}$$
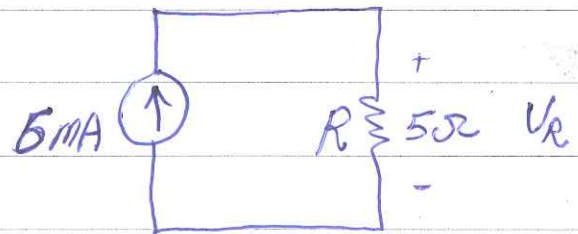
$$V_R = 6 \times 10^{-3} \times 5 = \underline{30mV}$$




EX: if $V_0 = 3$ Volt in the circuit in fig., find V_S .
 ③

Sol


$$I = \frac{V}{R} \Rightarrow I = \frac{3}{9k\Omega} = \frac{1}{3} mA$$

$$V_S = I \times (12k + 9k)$$
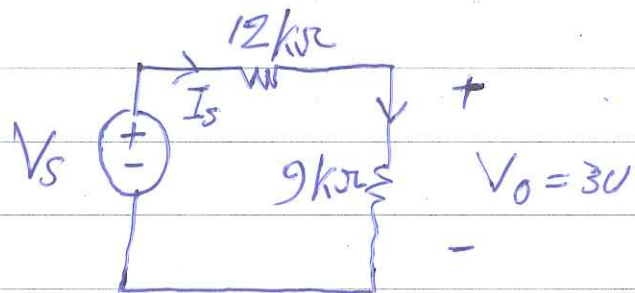
$$V_S = \frac{1}{3} \times 10^{-3} \times 21 \times 10^3 = \underline{7 \text{ Volt}}$$



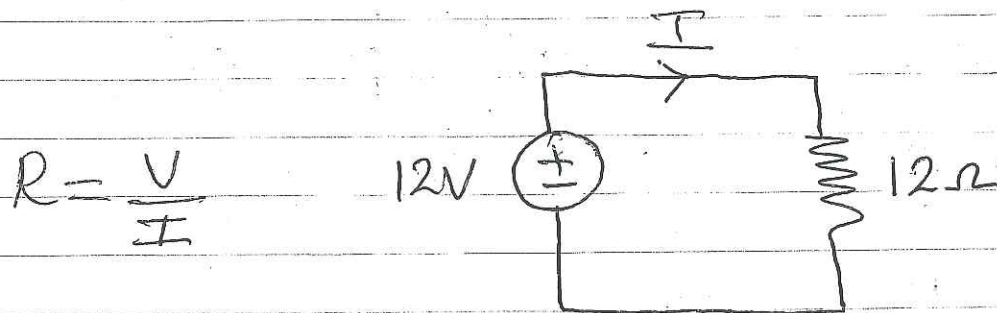~~Ex:~~ For the circuit as shown in fig., find the power absorbed in the resistance.



$$R = \frac{V}{I}$$

$$I = \frac{V}{R} = \frac{12}{12} = 1 \text{ (A)}$$

$$P = V * I = 12 * 1 = 12 \text{ watt}$$

$$P = I^2 * R = (1)^2 * 12 = 12 \text{ watt}$$

OR

$$P = \frac{V^2}{R} = \frac{(12)^2}{12} = 12 \text{ watt}$$

OR


$$P = V * I = (I * R) * I = I^2 R$$

$$P = V * \frac{V}{R} = \frac{V^2}{R}$$

~~Ex:~~ if $V_0 = 3$ volt in the circuit in fig., find V_s


$$I = \frac{3}{9k\Omega} = \frac{1}{3} \text{ mA}$$
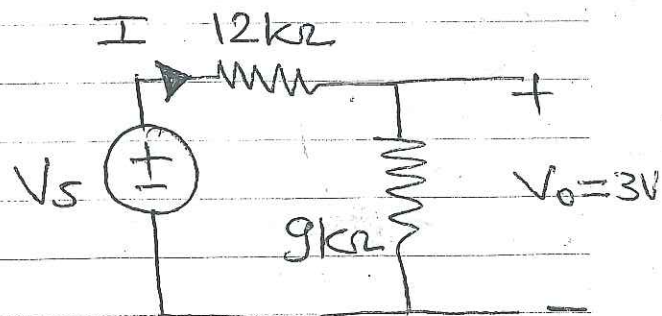
$$I = \frac{V_s}{12k\Omega + 9k\Omega} = \frac{1}{3} \text{ mA}$$



$$V_s = \frac{21k\Omega}{3} \text{ mA} = 7 \text{ Volt}$$



"Combination of Sources"

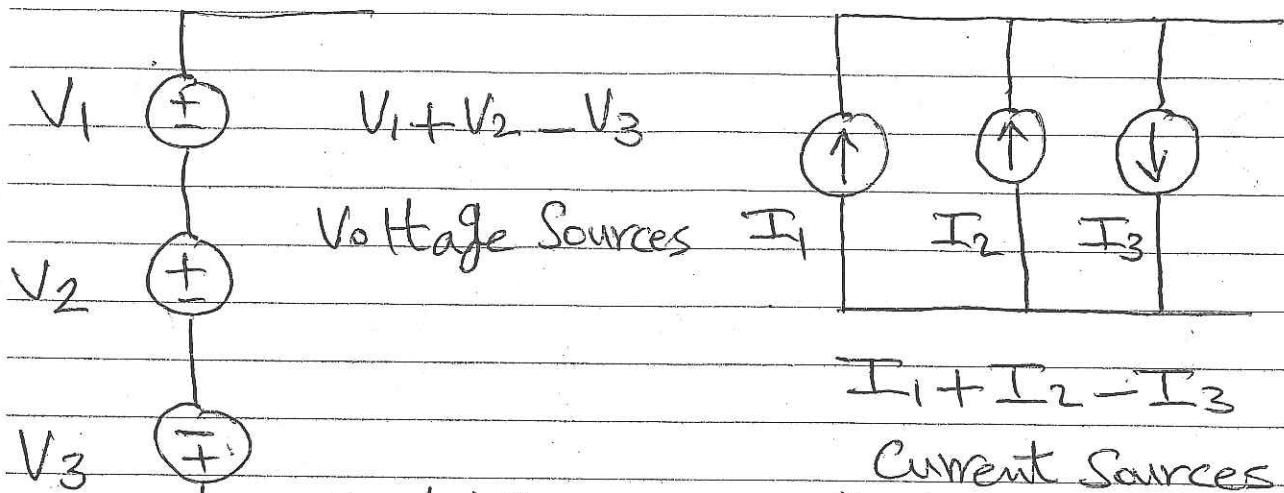

* at the same method, we can be applied the combination to the dependent sources.

("Voltage Source")

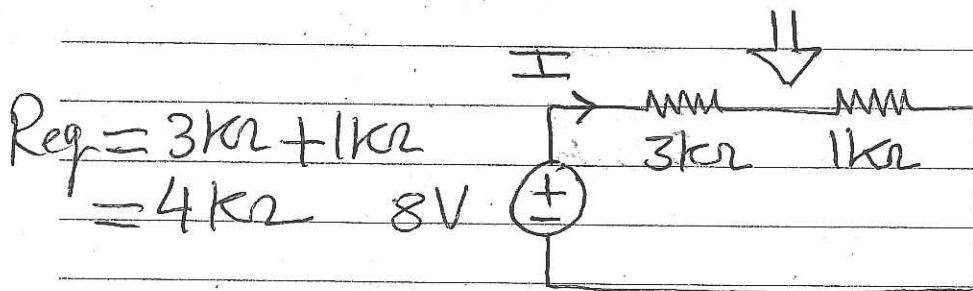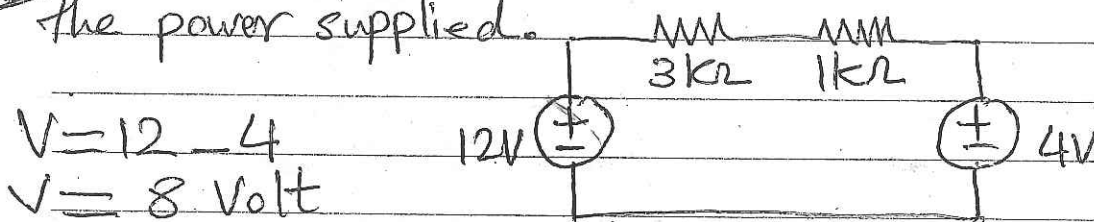Ex: - Find the current in the network in Fig., and the power supplied.



$$I = \frac{8}{4k\Omega} = 2 \text{ mA}$$

$$P = V \times I = 2 \times 10^{-3} \times 8 = 16 \text{ mwatt}$$