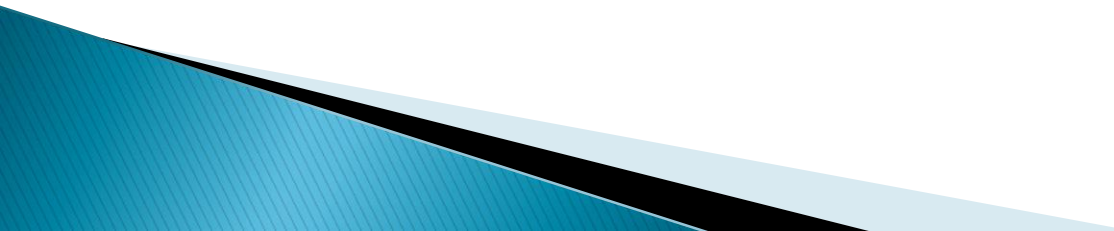




جامعة الموصل / كلية الهندسة قسم الهندسة الكهربائية


Subject Title : Electronic Circuits
Subject Code: ELCI214
Class : 2nd level
Instructor: Marwan Ahmed

Course Description Outlines


- ▶ Diode Application (clipper and clamper).
 - ▶ Rectifier and Filters
 - ▶ Voltage Multipliers.
 - ▶ LED Applications.
 - ▶ Zener Diode Application (Regulation)
 - ▶ Transistor Operation Principle.
 - ▶ Transistor Application (Amplifier).
 - ▶ Thyristor Applications.
 - ▶ Silicon –Controlled Rectifier (SCR).
- 

The diode rectifier


1-Half-wave rectifier

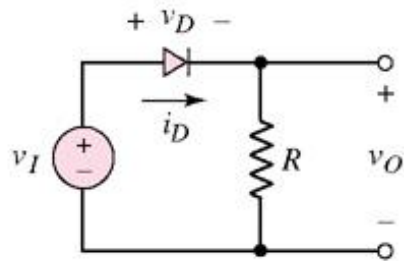


(a)

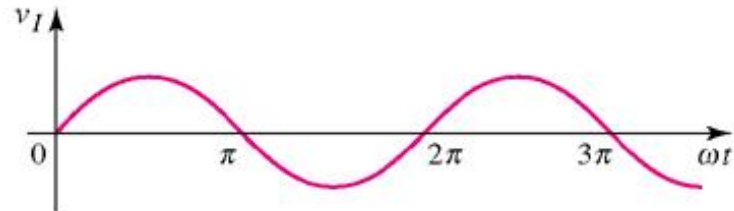

(b)

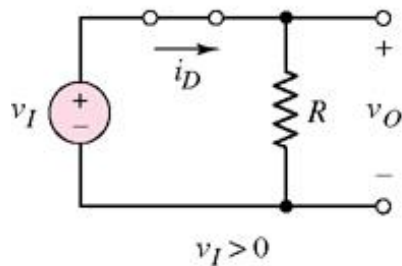

(c)

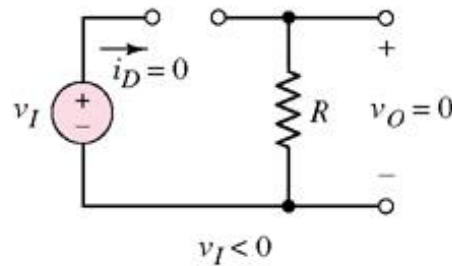


(d)




(e)

- (a) Diode half-wave rectifier circuit,
- (b) sinusoidal input signal,
- (c) equivalent circuit for $v_I > 0$.
- (d) equivalent circuit for $v_I < 0$.
- (e) rectified output signal.


Full-wave rectifier

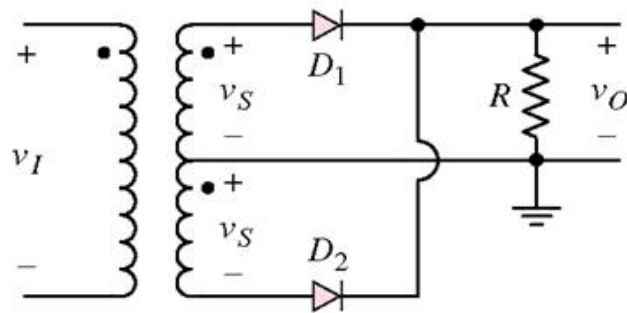

(a)

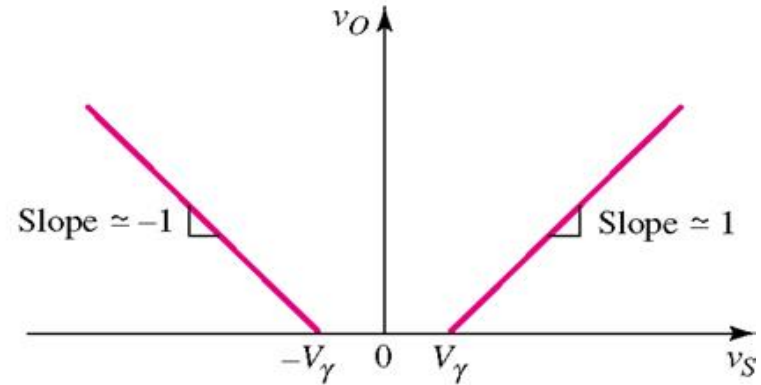


(b)

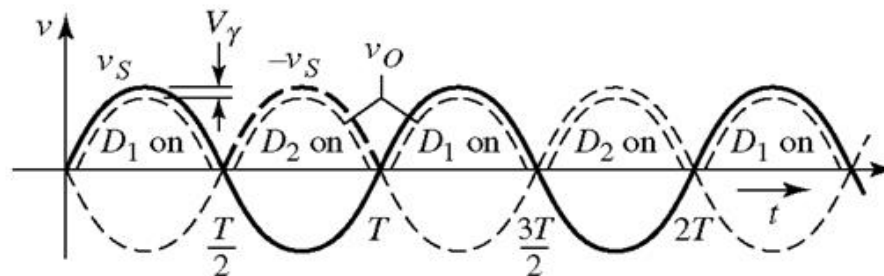

(c)


- (a) circuit with center-tapped transformer
- (b) voltage transfer characteristics
- (c) input and output waveforms

3-A full-wave bridge rectifier

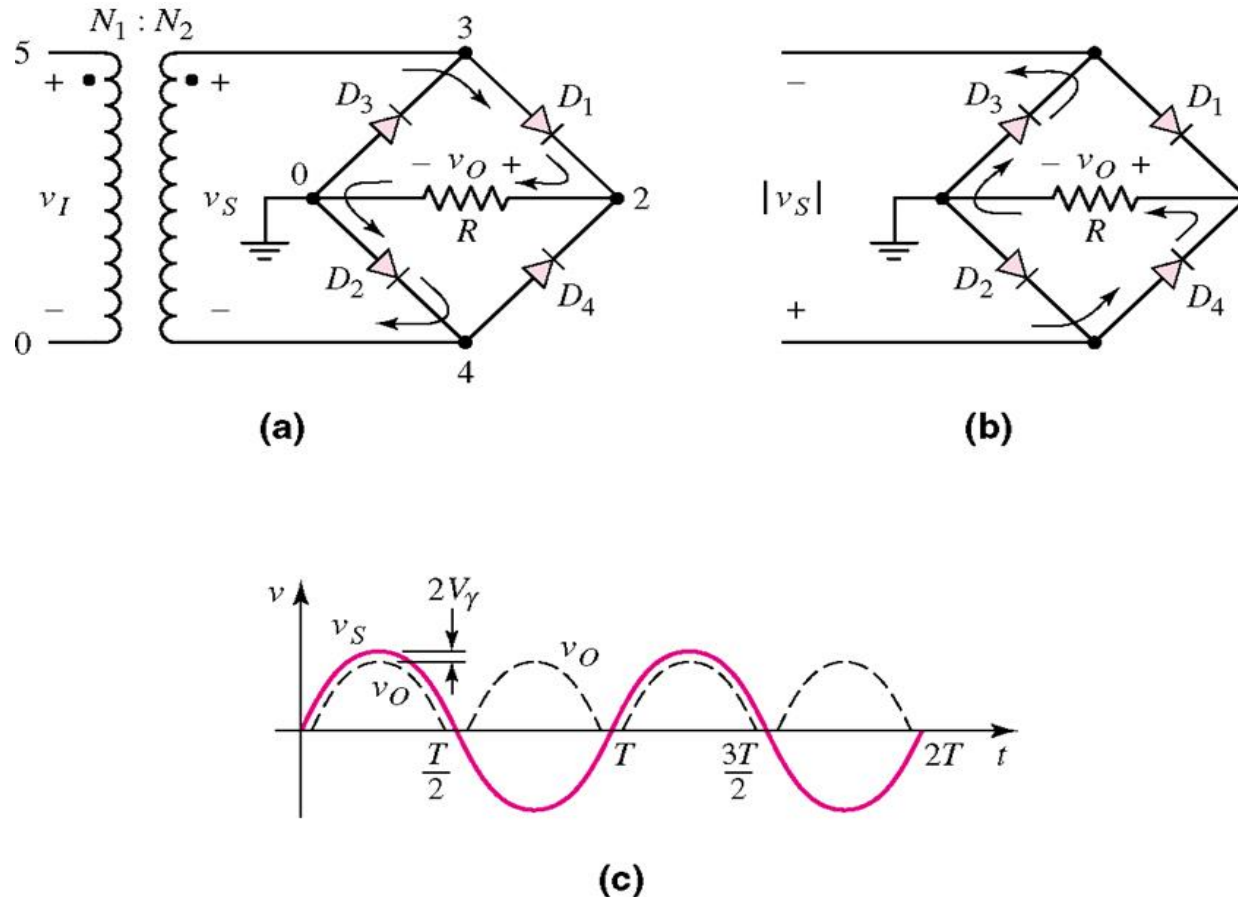


- (a) circuit showing the current direction for a positive input cycle
- (b) current direction for a negative input cycle
- (c) input and output voltage waveforms

Single-diode clipper

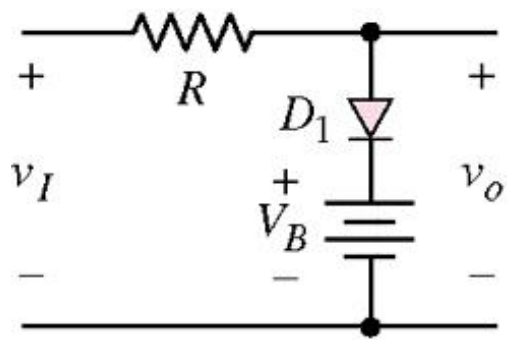

(a)

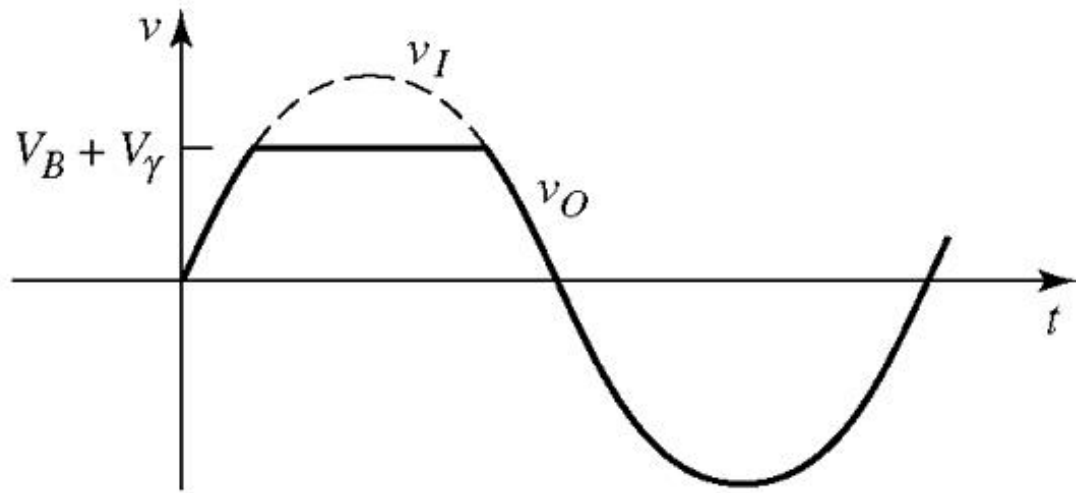


(b)


(a) circuit

(b) output response


A Diode clamper circuit

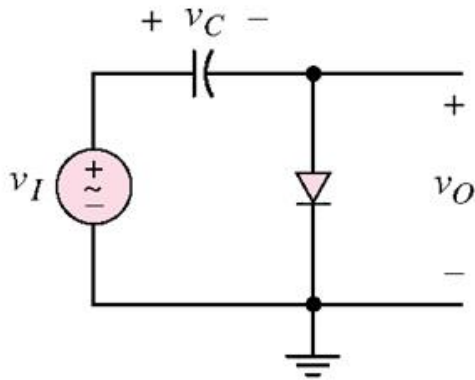


(a)

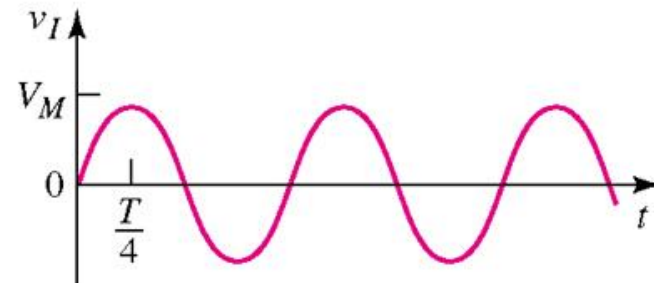

(b)

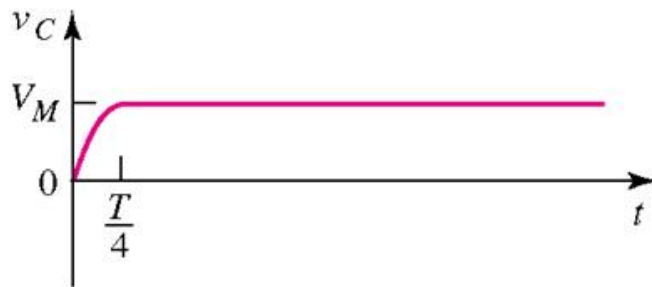

(c)

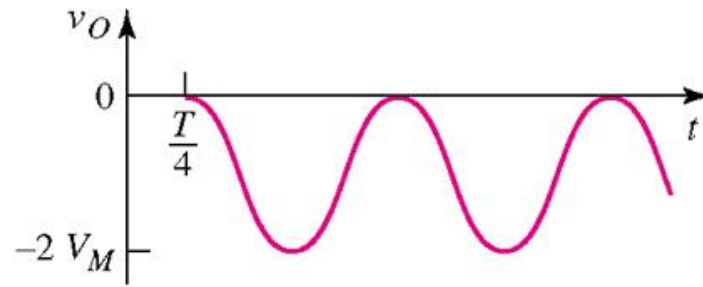


(d)

(a) a typical diode clamper circuit


(b) the sinusoidal input signal

(c) the capacitor voltage, and (d) the output voltage

A Zener diode voltage regulator circuit

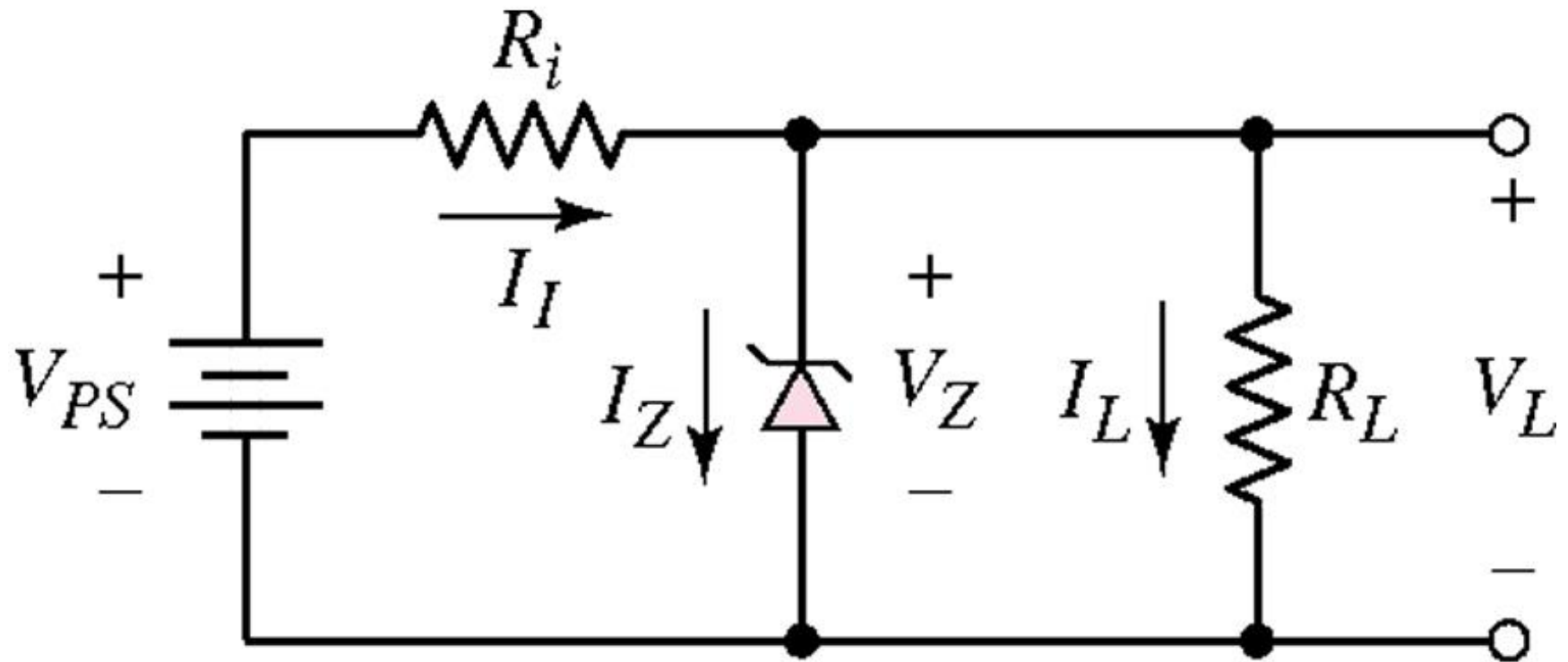

The Bipolar Junction Transistor

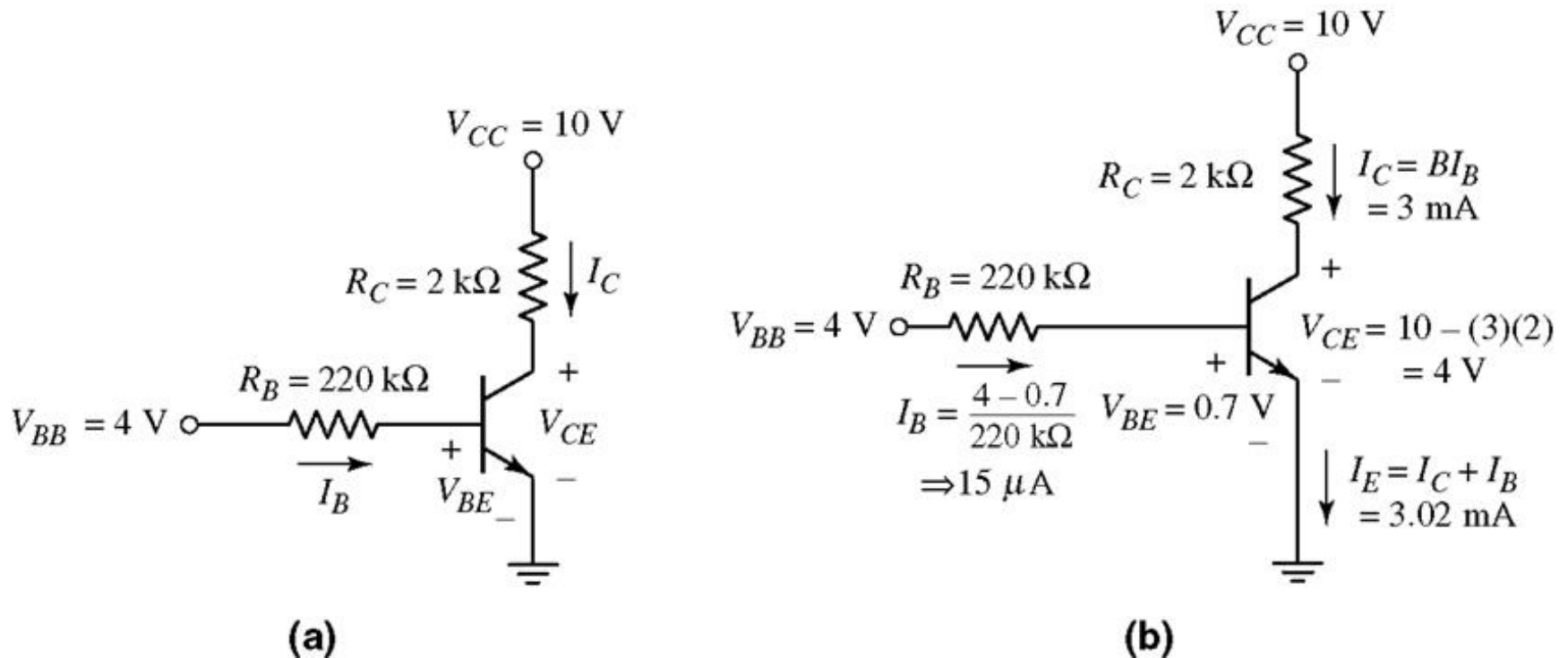

References

- ▶ Electronic Devices by Thomas L. Floyd
 - ▶ Electronic Devices and Circuit Theory by Robert Boylestad and Louis Nashelsky
 - ▶ Electronic Circuit Analysis and Design by Neamen
- 