

### dc Analysis

Consider  $V_{BE} = 0.7V$  ,

We can obtain transistor input characteristic as:

$$V_{BB} = I_B R_B + V_{BE} \quad \text{So,}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} \quad \text{IV Input Characteristic Curve Equation}$$

As for the output characteristics,


$$V_{CC} = I_C R_C + V_{CE}$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} \quad \text{Output characteristic equation}$$

As for the voltage between base and collector:

$$V_{CB} = V_{CE} - V_{BE}$$

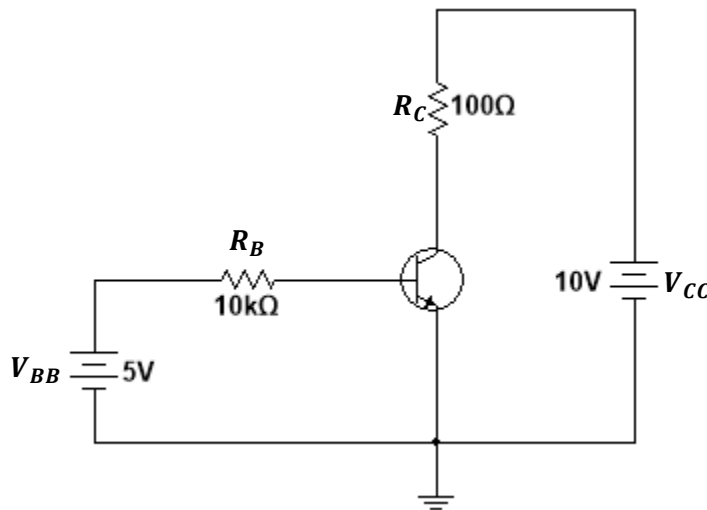Example: Determine  $I_B$ ,  $I_C$  ,  $V_{CE}$  and  $V_{CB}$  in the circuit below. Transistor has  $\beta_{dc} = 150$  .



$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 - 0.7V}{10k\Omega} = 430 \mu A$$


$$I_C = \beta_{dc} I_B = (150)(430 \mu A) = 64.5 mA$$

$$V_{CE} = V_{CC} - I_C R_C = 10V - (64.5mA)(100\Omega)$$


$$= 10V - 6.45V = 3.55V$$

$$V_{CB} = V_{CE} - V_{BE} = 3.55V - 0.7V = 2.85V$$

Collector Curves:

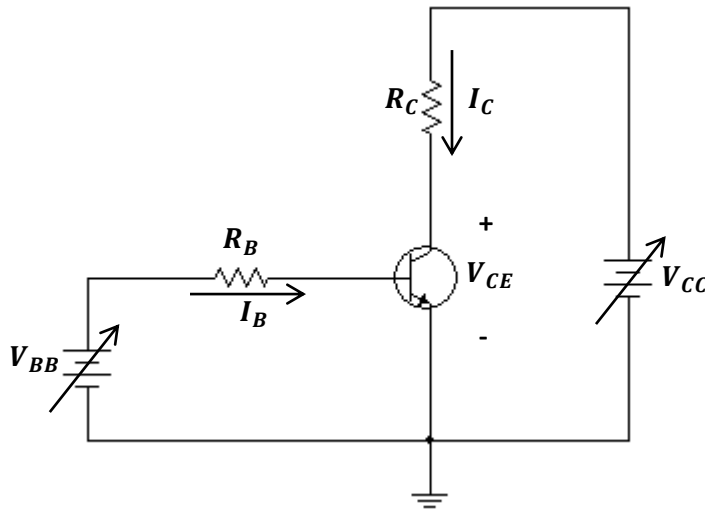


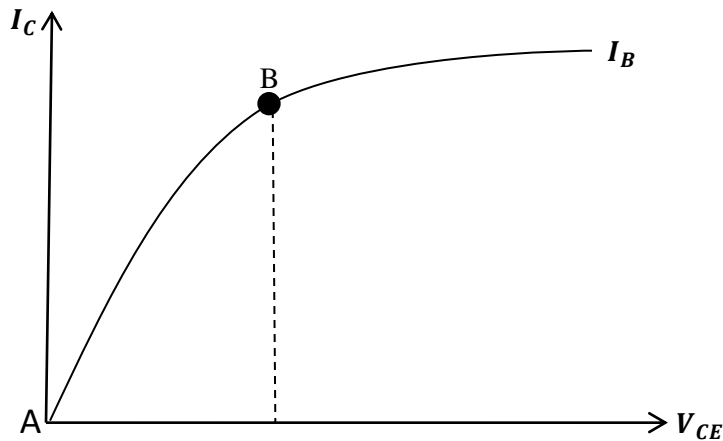- Notice that both  $V_{BB}$  and  $V_{CC}$  are adjustable.




- If  $V_{BB}$  is set to produce a specific value of  $I_B$  and  $V_{CC}$  is zero, the  $I_C = 0$  and  $V_{CE} = 0$ .
- As  $V_{CC}$  is gradually increased,  $V_{CE}$  will increase and so will  $I_C$  (from point A to point B).

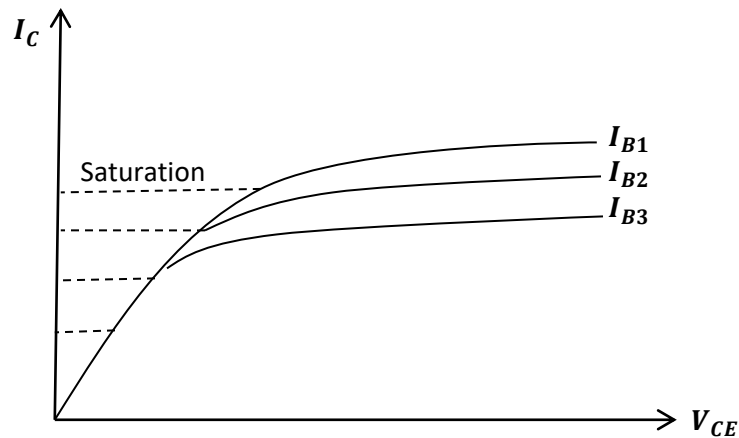- When  $V_{CE}$  reaches approximately 0.7V, the BC junction becomes reverse biased and  $I_C$  reaches its full value (almost constant) determined by the relationship  $I_C = \beta_{dc} I_B$  as  $V_{CE}$  continues to increase.
- Actually  $I_C$  increases slightly as  $V_{CE}$  increases due to widening the BC depletion layer which results in fewer holes for recombination in the base region.


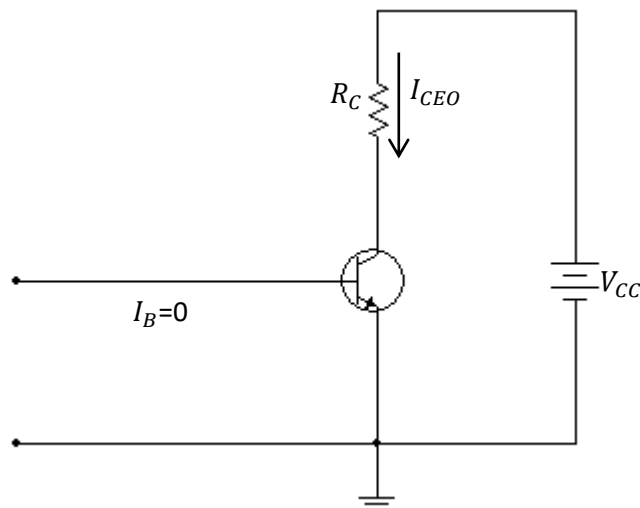
### Cut off and Saturation

- When  $I_B = 0$ , the transistor is cutoff. There is only very small amount of collector leakage current  $I_{CEO}$ , due mainly to thermally produced carriers.




- In cutoff, both BE and BC junctions are reverse-biased.
- As for saturation, when  $I_B$  is increased,  $I_C$  also increases,  $V_{CE}$  decreases (more voltage drop across  $R_C$ )

$$V_{CC} = I_C R_C + V_{CE}$$

- When  $V_{CE}$  reaches a value called  $V_{CE(sat)}$ , BC becomes forward-biased and  $I_C$  can increase no further even with continued increase in  $I_B$ . At this point of saturation,  $I_C = \beta_{dc} I_B$  is no longer valid.

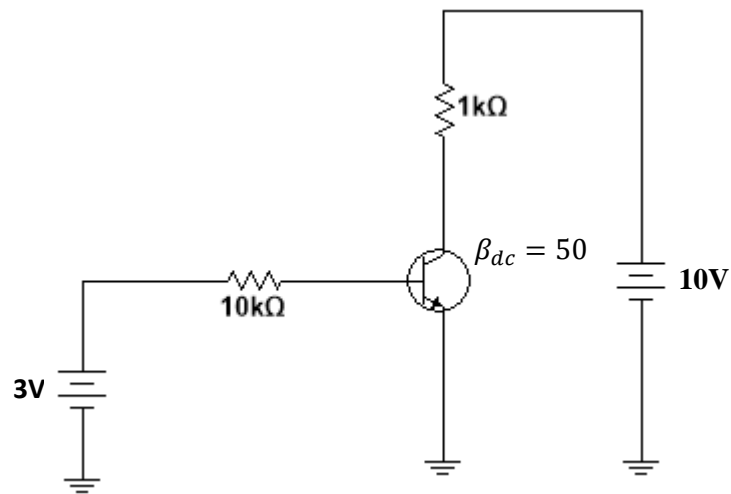Example: Determine whether or not the transistor in figure below is in saturation. Assume  $V_{CE(sat)}$  is small enough to neglect.



$$I_{C(sat)} = \frac{V_{CC} - V_{CE(sat)}}{R_C} = \frac{10V}{1k\Omega} = 10mA$$

Now, let's see if  $I_B$  is large enough to produce  $I_{C(sat)}$ .

$$I_B = \frac{V_{BB} - 0.7V}{R_B} = \frac{3V - 0.7V}{10k\Omega} = \frac{2.3V}{10k\Omega} = 0.23mA$$

$$I_C = \beta_{dc} I_B = (50)(0.23mA) = 11.5mA$$

This shows that with the specified  $\beta_{dc}$ , this base current is capable of producing an  $I_C$  greater than  $I_{C(sat)}$ , therefore the transistor is saturated, and the  $I_C = 11.5mA$  is never reached.