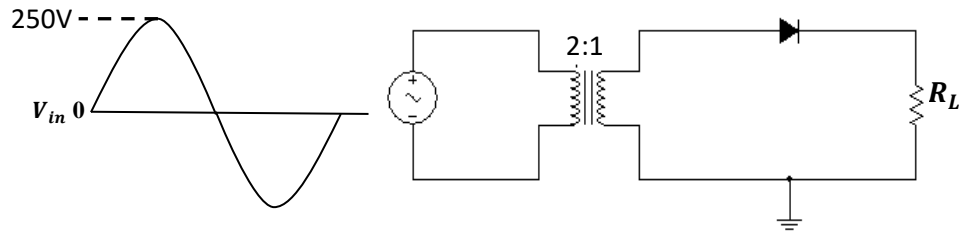


**Example:** Determine the peak value of the output voltage of figure below:



$$V_2 = \left(\frac{N_2}{N_1}\right) V_1$$

$$= \left(\frac{1}{2}\right) (250V)$$

$$= 125V$$


Peak Value of Output Voltage

$$V_{p(out)} = V_{p(in)} - 0.7V$$

$$= 125V - 0.7V$$

$$= 124.3V$$


### 2-3 Full-Wave Rectifier

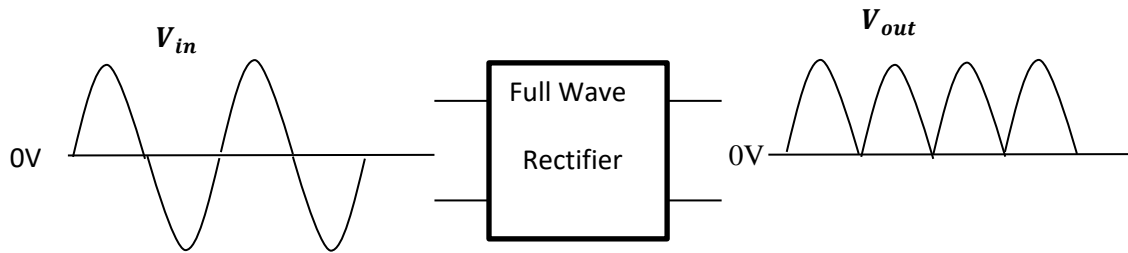

- The average value for a full-wave rectified voltage is twice that of the half-wave.

$$V_{AVG} = \frac{2V_p}{\pi}$$

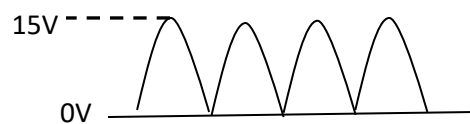**Example:** Find the average value of the full-wave rectified voltage in Figure below:




$$V_{AVG} = \frac{2V_p}{\pi} = \frac{2(15V)}{\pi} = 9.55V$$

### 2-3.1 Center-Tapped Full-Wave Rectifier


Full-Wave Bridge rectifier is discussed below instead of Center-Tapped rectifier.
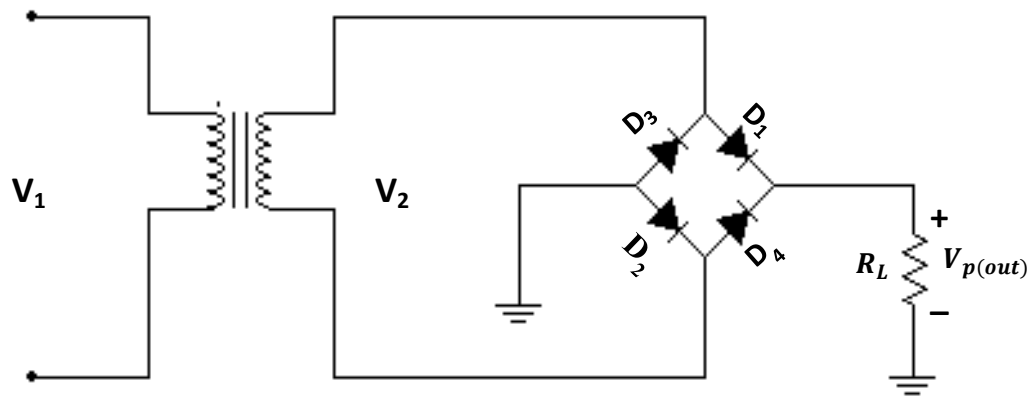
### 2-3.2 Full-Wave Bridge Rectifier


This type of full-wave rectifier uses four diodes as shown:



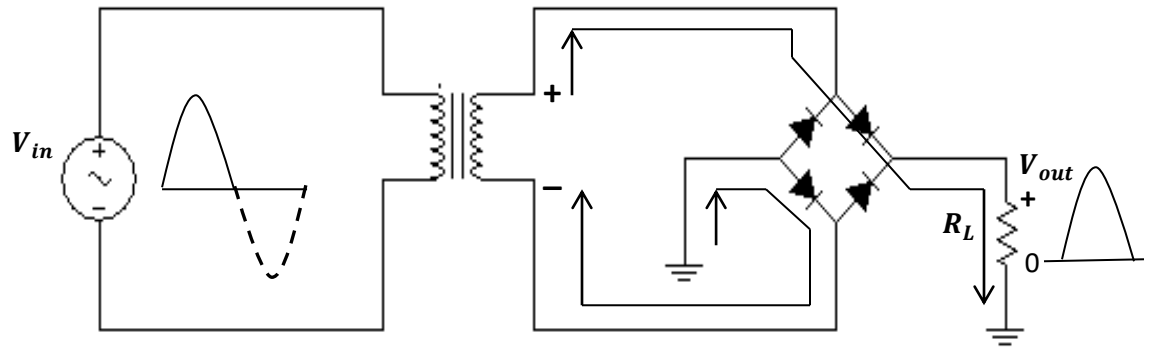When the input cycle is positive, Diodes  $D_1$  and  $D_2$  are forward biased, while  $D_3$  and  $D_4$  are reverse biased.




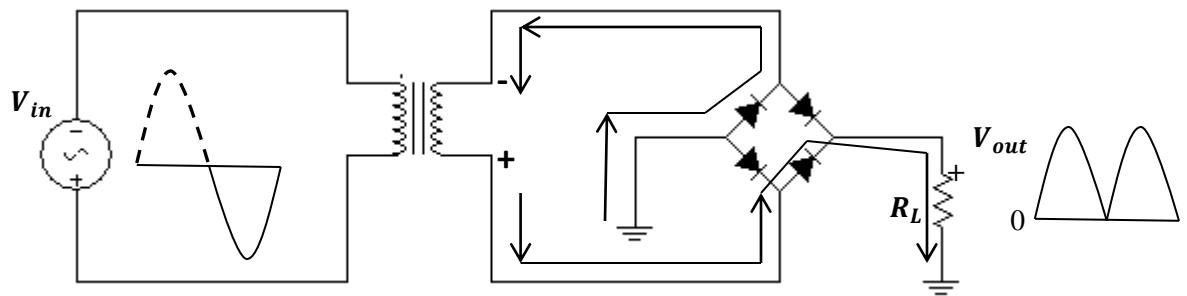- When the input cycle is negative, Diodes  $D_3$  and  $D_4$  are forward biased, while  $D_1$  and  $D_2$  are reverse biased.


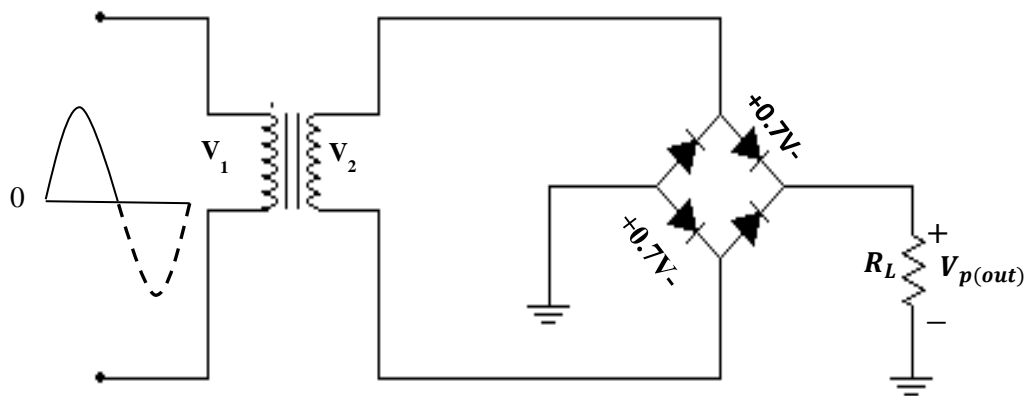
### Bridge Output Voltage

A bridge rectifier with transformer-coupled input is shown, during the positive half-cycle of the secondary voltage.



$$V_{p(out)} = V_2 - 2V_B$$

### Peak Inverse Voltage

Let us assume  $D_1$  and  $D_2$  are forward biased,  $D_3$  and  $D_4$  are reverse biased,

$$PIV = V_{p(out)}$$

